

CP2 ELECTROMAGNETISM

<https://users.physics.ox.ac.uk/~harnew/lectures/>

LECTURE 18: TRANSFORMER, MAGNETIC ENERGY



Neville Harnew¹
University of Oxford
HT 2022

$$\begin{aligned}\nabla \cdot \mathbf{E} &= \frac{\rho}{\epsilon_0} \\ \nabla \cdot \mathbf{B} &= 0 \\ \nabla \times \mathbf{E} &= -\frac{\partial \mathbf{B}}{\partial t} \\ \frac{1}{\mu_0} \nabla \times \mathbf{B} &= \mathbf{J} + \epsilon_0 \frac{\partial \mathbf{E}}{\partial t}\end{aligned}$$

OUTLINE : 18. TRANSFORMER, MAGNETIC ENERGY

18.1 Coaxial solenoids sharing the same area



18.2 Inductors in series and parallel

18.3 The transformer

18.4 Energy of the magnetic field

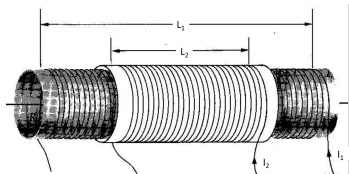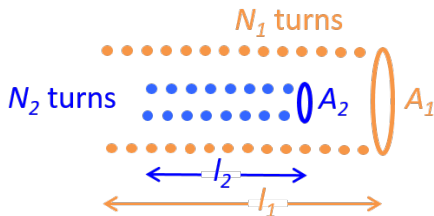18.1 Coaxial solenoids sharing the same area



From before : mutual inductance between coils :




In general circuits may not be tightly coupled, hence

$M = k\sqrt{(L_1 L_2)}$ where $k < 1$. k is the *coefficient of coupling*.

18.2 Inductors in series and parallel

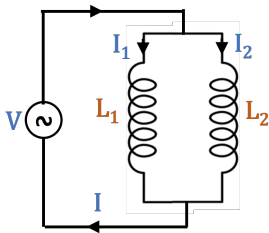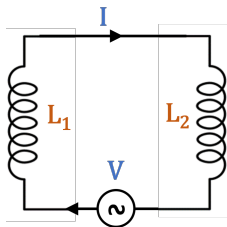


18.3 The transformer

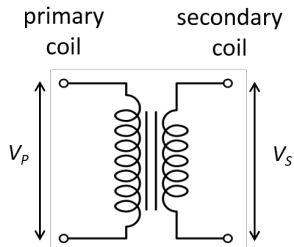

- ▶ Transformer will step up or step down applied voltage V_p by the winding ratio
- ▶ Ideally there is no power dissipated in the transformer if coils have zero resistance

Transformer summary

primary coil secondary coil

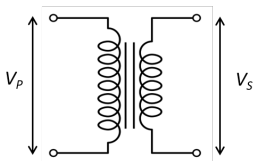

Primary coil creates flux which permeates secondary coil, coupling their voltages:

Voltage
Ratio:

$$\frac{V_S}{V_P} = \frac{d\Phi_S N_S}{d\Phi_P N_P}$$

Current
Ratio:

$$\frac{I_S}{I_P} = \frac{d\Phi_P N_P}{d\Phi_S N_S}$$

18.4 Energy of the magnetic field

Consider the energy stored in an inductor L :

- ▶ Change in current results in a back EMF \mathcal{E}

Summary of energy in E and B fields

Electric field energy

Magnetic field energy