

# CP2 ELECTROMAGNETISM

<https://users.physics.ox.ac.uk/~harnew/lectures/>

## LECTURE 18: TRANSFORMER, MAGNETIC ENERGY



Neville Harnew<sup>1</sup>  
University of Oxford  
HT 2022

$$\begin{aligned}\nabla \cdot \mathbf{E} &= \frac{\rho}{\epsilon_0} \\ \nabla \cdot \mathbf{B} &= 0 \\ \nabla \times \mathbf{E} &= -\frac{\partial \mathbf{B}}{\partial t} \\ \frac{1}{\mu_0} \nabla \times \mathbf{B} &= \mathbf{J} + \epsilon_0 \frac{\partial \mathbf{E}}{\partial t}\end{aligned}$$

## *OUTLINE : 18. TRANSFORMER, MAGNETIC ENERGY*

*18.1 Coaxial solenoids sharing the same area*

*18.2 Inductors in series and parallel*

*18.3 The transformer*

*18.4 Energy of the magnetic field*

## 18.1 Coaxial solenoids sharing the same area

From before : mutual inductance between coils :

$$M_{21} = M_{12} = \mu_0 \frac{N_1 N_2}{\ell_1} A_2 (= M)$$

- ▶ Self inductance of coils 1 & 2

$$L_1 = \mu_0 \frac{N_1^2}{\ell_1} A_1 \quad \text{and}$$

$$L_2 = \mu_0 \frac{N_2^2}{\ell_2} A_2$$

- ▶ If  $A_1 = A_2$



$$M = \left( \sqrt{\frac{\ell_2}{\ell_1}} \right) \sqrt{(L_1 L_2)}$$

If  $\ell_1 = \ell_2$  then  $M = \sqrt{(L_1 L_2)}$

- ▶ Hence the mutual inductance is proportional to the geometrical mean of the self inductances.

In general circuits may not be tightly coupled, hence

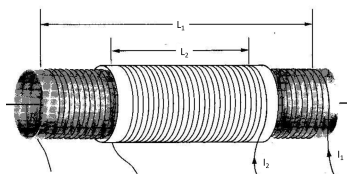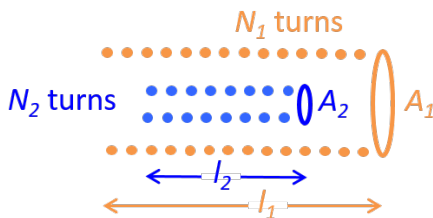$M = k \sqrt{(L_1 L_2)}$  where  $k < 1$ .  $k$  is the *coefficient of coupling*.



## 18.2 Inductors in series and parallel

- 1. In series with no mutual inductance between coils :

$$V = L_1 \frac{dI}{dt} + L_2 \frac{dI}{dt} = (L_1 + L_2) \frac{dI}{dt}$$

$$L = L_1 + L_2$$

- 2. In series with mutual inductance between coils :

$$V = (L_1 + M) \frac{dI}{dt} + (L_2 + M) \frac{dI}{dt}$$
$$= (L_1 + L_2 + 2M) \frac{dI}{dt}$$

$$L = L_1 + L_2 + 2M$$



- 3. In parallel, no mutual inductance :

$$V = L_1 \frac{dI_1}{dt} = L_2 \frac{dI_2}{dt} \quad \text{where } I = I_1 + I_2$$

$$\text{Write } V = L \frac{dI}{dt} \rightarrow V = L \left( \frac{dI_1}{dt} + \frac{dI_2}{dt} \right) = L \left( \frac{V}{L_1} + \frac{V}{L_2} \right)$$

$$\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2}$$
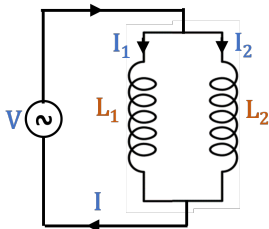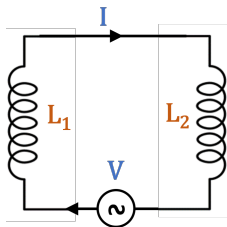
$$\text{(with mutual inductance } L = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} \text{)}$$




## 18.3 The transformer

- ▶ Primary coil creates flux  $\Phi_p = A_p B_p$  per winding  $\rightarrow$  secondary coil gives EMF per winding  $\mathcal{E}_S = -\frac{d\Phi_S}{dt}$
- ▶ The coils are coupled :  $\Phi_S = k\Phi_P$  where  $k = 1$  for an ideal transformer ( $k$  depends on geometry, coupling etc.)
- ▶ Ratio of EMFs :

$$\mathcal{E}_P = -N_P \frac{d\Phi_P}{dt} \rightarrow \frac{V_S}{V_P} = \underbrace{\frac{d\Phi_S}{d\Phi_P}}_k \times \underbrace{\frac{N_S}{N_P}}_{\text{winding ratio}}$$
$$\mathcal{E}_S = -N_S \frac{d\Phi_S}{dt}$$


- ▶ Transformer will step up or step down applied voltage  $V_P$  by the winding ratio
- ▶ Ideally there is no power dissipated in the transformer if coils have zero resistance
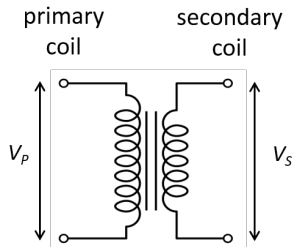
$$\rightarrow V_S I_S = V_P I_P \rightarrow \frac{I_S}{I_P} = \frac{V_P}{V_S} = \frac{1}{k} \frac{N_P}{N_S}$$



## Transformer summary

primary coil      secondary coil

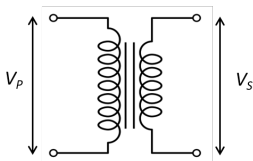

Primary coil creates flux which permeates secondary coil, coupling their voltages:

Voltage  
Ratio:

$$\frac{V_S}{V_P} = \frac{d\Phi_S N_S}{d\Phi_P N_P}$$

Current  
Ratio:

$$\frac{I_S}{I_P} = \frac{d\Phi_P N_P}{d\Phi_S N_S}$$

## 18.4 Energy of the magnetic field

Consider the energy stored in an inductor  $L$  :

- ▶ Change in current results in a back EMF  $\mathcal{E}$
- ▶ We need to do work to change the current :  $dW = VdQ$

$$\text{Power} = \text{work per unit time} = V \frac{dQ}{dt} = VI$$

$$\text{Energy expended } U = \int \underbrace{VI}_{\text{power}} dt = \int \underbrace{L \frac{dI}{dt}}_{\text{Back EMF}} I dt$$

- ▶  $U = \frac{1}{2} LI^2 = \frac{1}{2} \Phi I$  ( $L = \frac{\Phi}{I}$ )

regardless of circuit / current geometry

- ▶ For a coil :  $L = \mu_0 \frac{N^2}{\ell} A$  and  $B = \mu_0 \frac{N}{\ell} I$  (Ampere Law)

$$\rightarrow U = \frac{1}{2} \left( \mu_0 \frac{N^2}{\ell} A \right) \left( \frac{B^2}{\mu_0^2 \frac{N^2}{\ell^2}} \right) = \frac{1}{2} \frac{B^2}{\mu_0} A \ell = \frac{1}{2} \frac{B^2}{\mu_0} \mathcal{V} \leftarrow \text{volume}$$

- ▶ In the general case :  $U = \frac{1}{2\mu_0} \int B^2 d\mathcal{V}$  over all space

## Summary of energy in $E$ and $B$ fields

### Electric field energy

- ▶ In terms of circuits :

$$U_e = \frac{1}{2} C V^2$$
$$= \frac{1}{2} Q V$$

- ▶ In terms of fields :

$$U_e = \frac{\epsilon_0}{2} \int_{all\ space} E^2 dV$$

### Magnetic field energy

- ▶ In terms of circuits :

$$U_m = \frac{1}{2} L I^2$$
$$= \frac{1}{2} \Phi I$$

- ▶ In terms of fields :

$$U_m = \frac{1}{2\mu_0} \int_{all\ space} B^2 dV$$