




CP2 Circuit Theory

Prof. Todd Huffman todd.huffman@physics.ox.ac.uk
<http://www-pnp.physics.ox.ac.uk/~huffman/>

Aims of this course:

Understand basic circuit components (resistors, capacitors, inductors, voltage and current sources, op-amps)

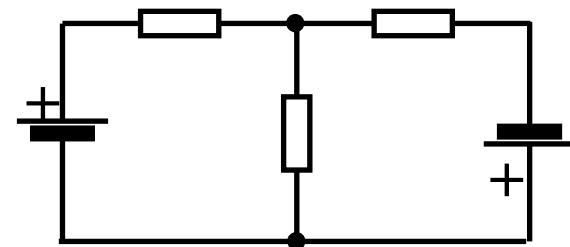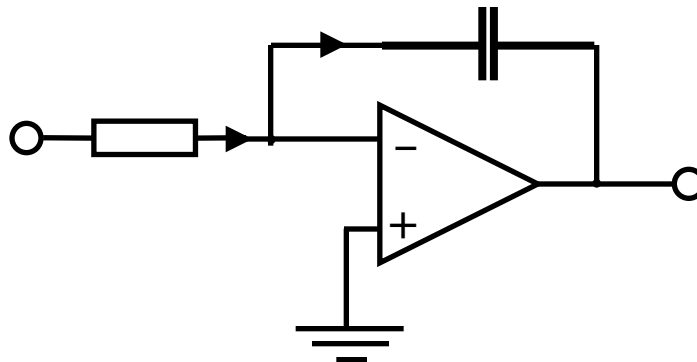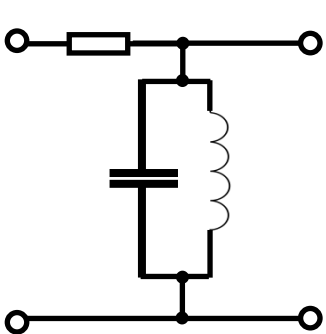Analyse and design simple linear circuits



Circuit Theory: Synopsis

Basics: voltage, current, Ohm's law...

Kirchoff's laws: mesh currents, node voltages...

Thevenin and Norton's theorem: ideal voltage and current sources...

Capacitors: } Stored energy, RC and RL transient
Inductors: } circuits

AC theory: complex notation, phasor diagrams, RC, RL, LCR circuits, resonance, bridges...

Op amps: ideal operational amplifier circuits...

Op-amps are on the exam syllabus

Reading List

- *Electronics: Circuits, Amplifiers and Gates, D V Bugg, Taylor and Francis*
Chapters 1-7
- *Basic Electronics for Scientists and Engineers, D L Eggleston, CUP*
Chapters 1,2,6
- *Electromagnetism Principles and Applications, Lorrain and Corson, Freeman*
Chapters 5,16,17,18
- *Practical Course Electronics Manual*
http://www-teaching.physics.ox.ac.uk/practical_course/EIManToc.html
Chapters 1-3
- *Elementary Linear Circuit Analysis, L S Bobrow, HRW*
Chapters 1-6
- *The Art of Electronics, Horowitz and Hill, CUP*

Why study circuit theory?

- Foundations of electronics: analogue circuits, digital circuits, computing, communications...
- Scientific instruments: readout, measurement, data acquisition...
- Physics of electrical circuits, electromagnetism, transmission lines, particle accelerators, thunderstorms...
- Not just electrical systems, also thermal, pneumatic, hydraulic circuits, control theory

Mathematics required

- Differential equations $\frac{d^2I}{dt^2} + \frac{R}{L} \frac{dI}{dt} + \frac{1}{LC} I = 0$

- Complex numbers $V(t) = V_0 e^{j\omega t}$

$$I = \frac{V}{Z} \quad Z = R + jX$$

- Linear equations

$$V_0 - I_1 R_1 - (I_1 - I_2) R_3 = 0$$

$$(I_1 - I_2) R_3 - I_2 R_2 + 2 = 0$$

Covered by Complex Nos & ODEs /
Vectors & Matrices lectures (but with fewer dimensions)

Charge, voltage, current

Charge: determines strength of electromagnetic force
quantised: $e = 1.62 \times 10^{-19} C$ [coulombs]

Potential difference: $V = V_A - V_B$ [volts]

Energy to move unit charge from A to B
in electric field

$$V = - \int_A^B \mathbf{E} \cdot d\mathbf{s} \quad \mathbf{E} = -\nabla V$$

$$W = - \int_A^B Q \mathbf{E} \cdot d\mathbf{s}$$

Current: rate of flow of charge

$$I = \frac{dQ}{dt} = nAve$$

Charge $Q=e$

No. electrons/unit vol

Cross-section area of conductor

Drift velocity

[amps]

Power: rate of change of work



$$P = \frac{dW}{dt} = \frac{d}{dt}(QV) = Q \frac{dV}{dt} + V \frac{dQ}{dt}$$
$$= IV$$

[watts]

Ohm's law

Voltage difference \propto current

Resistor symbols:

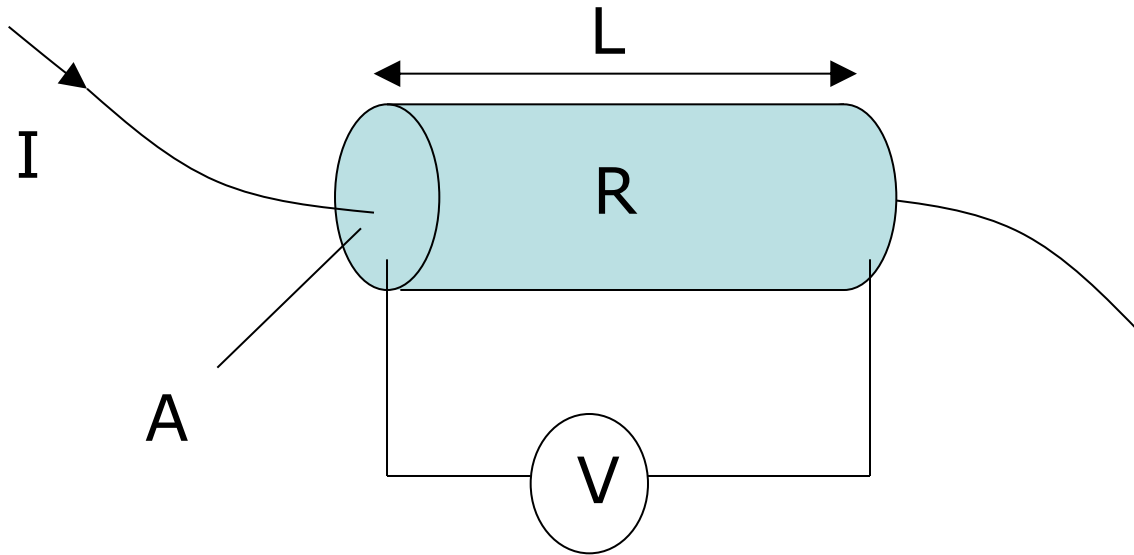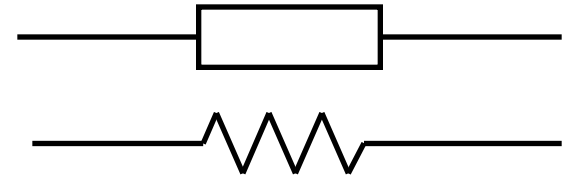

$$V = IR$$

R = Resistance Ω [ohms]

$$R = \frac{\rho L}{A}$$

ρ = Resistivity Ωm


Resistivities

Silver	$1.6 \times 10^{-8} \Omega\text{m}$
Copper	$1.7 \times 10^{-8} \Omega\text{m}$
Manganin	$42 \times 10^{-8} \Omega\text{m}$
Distilled water	$5.0 \times 10^3 \Omega\text{m}$
PTFE (Teflon)	$\sim 10^{19} \Omega\text{m}$


Conductance [seimens]	$g = \frac{1}{R}$	conductivity [seimens/m]	$\sigma = \frac{1}{\rho}$
--------------------------	-------------------	-----------------------------	---------------------------

Power dissipation by resistor: $P = IV = I^2R = \frac{V^2}{R}$

Voltage source

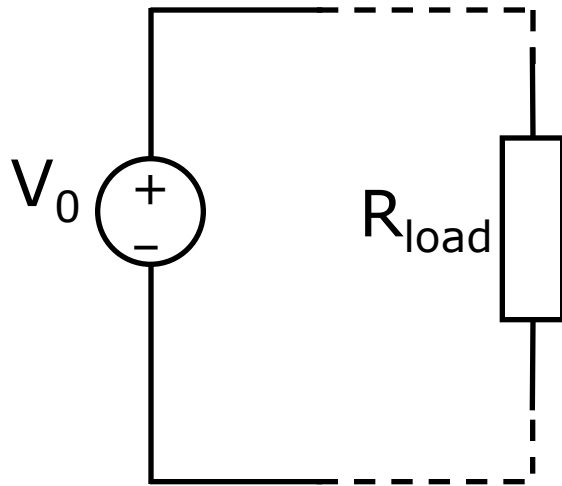

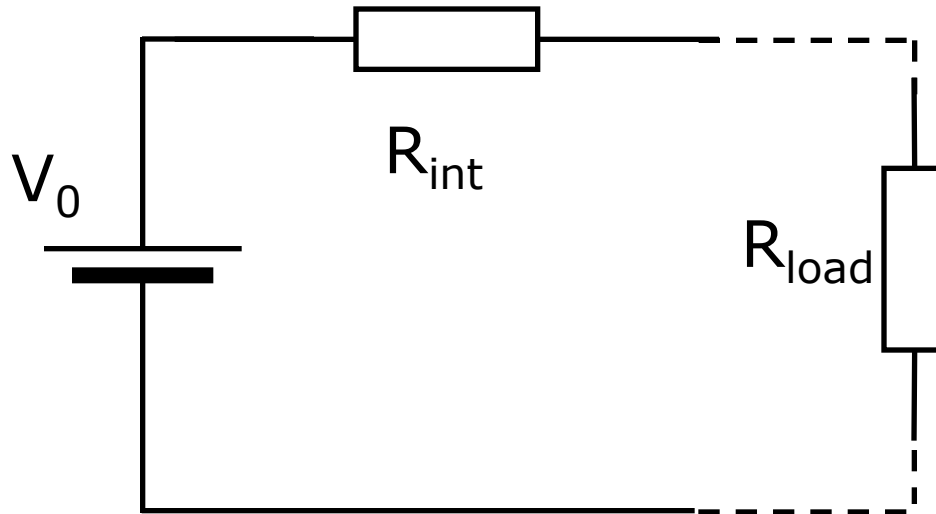Ideal voltage source: supplies V_0
independent of current




Real voltage source:



$$V_{\text{load}} = V_0 - IR_{\text{int}}$$

battery cell

Constant current source

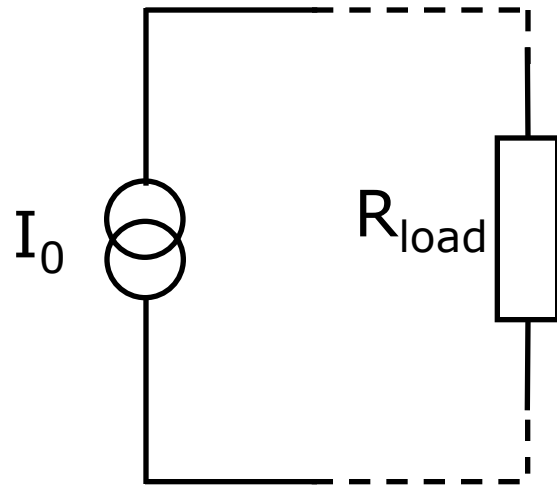

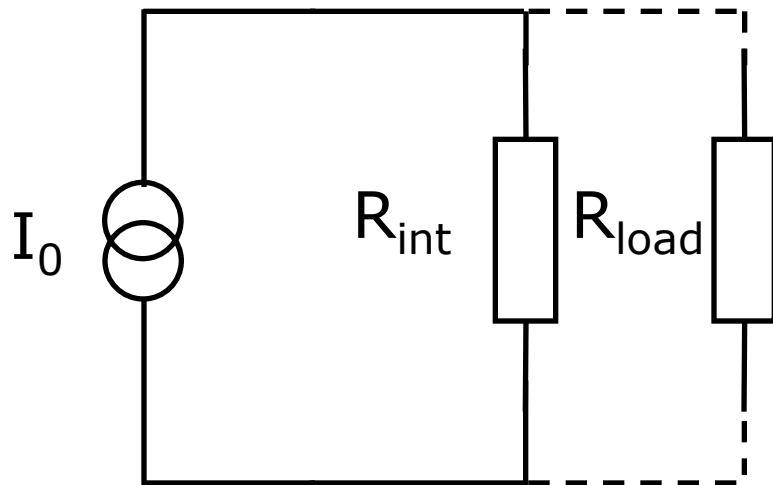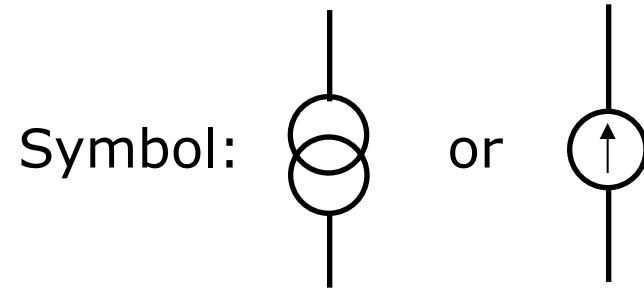Ideal current source: supplies I_0 amps independent of voltage




Real current source:

$$I_{load} = I_0 - \frac{V}{R_{int}}$$

AC and DC

DC (Direct Current):

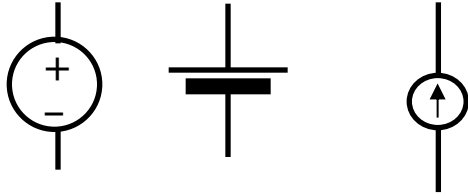


Constant voltage or current

Time independent

$$V = V_0$$

AC (Alternating Current):

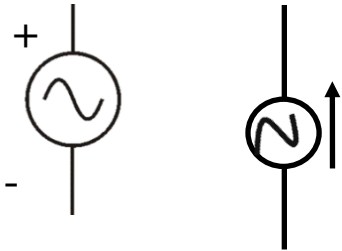


Time dependent

Periodic

$$I(t) = I_0 \sin(\omega t)$$

$$\omega = 2\pi f = \frac{2\pi}{T}$$

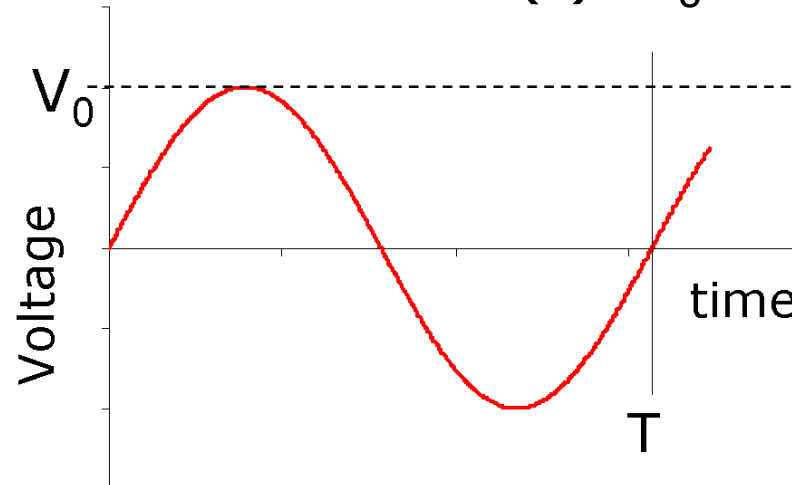


50Hz power, audio, radio...

RMS values

AC Power dissipation $\bar{P} = I_{\text{RMS}} V_{\text{RMS}} = \frac{V_{\text{RMS}}^2}{R}$

$$V_{\text{RMS}} = \frac{V_0}{\sqrt{2}}$$

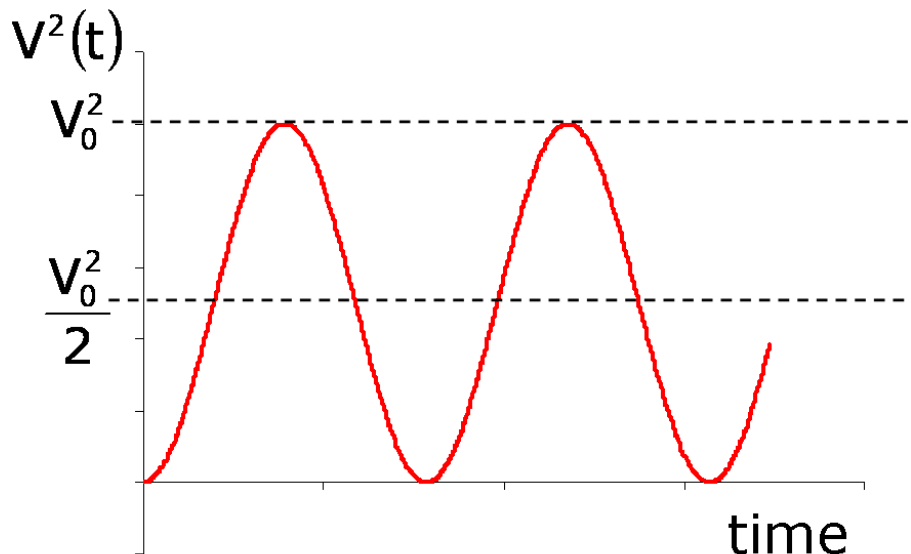Why $\sqrt{2}$? Square root of mean of $V(t)^2$



$$V_{\text{RMS}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

Passive Sign Convention

Passive devices ONLY - **Learn it; Live it; Love it!**

$R = \text{Resistance } \Omega[\text{ohms}]$



$$V = IR$$

Two seemingly Simple questions:


Which way does the current flow, left or right?

Voltage has a '+' side and a '-' side (you can see it on a battery)
on which side should we put the '+'? On the left or the right?

Given $V=IR$, does it matter which sides for V or which direction for I ?

Kirchoff's Laws

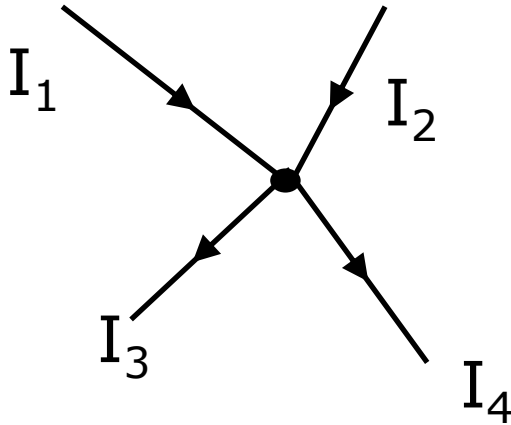I Kirchoff's current law: Sum of all currents at a node is zero



$$I_1 + I_2 - I_3 - I_4 = 0$$

$$\sum I_n = 0$$


(conservation of charge)

Here is a cute trick:

It does not matter whether you pick “entering” or “leaving” currents as positive.

BUT keep the same convention for all currents on one node!

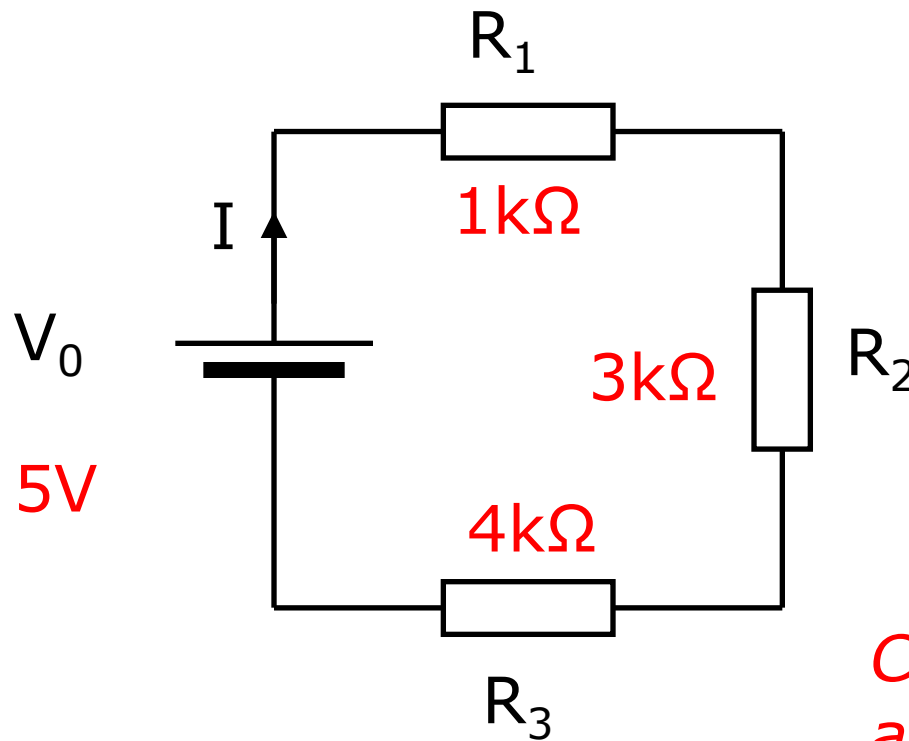II Kirchhoff's voltage law: Around a closed loop the net change of potential is zero (Conservation of Energy)




$$\sum V_n = 0$$

Calculate the voltage across R_2

Kirchoff's voltage law:

$$\sum V_n = 0$$

$$-V_0 + IR_1 + IR_2 + IR_3 = 0$$

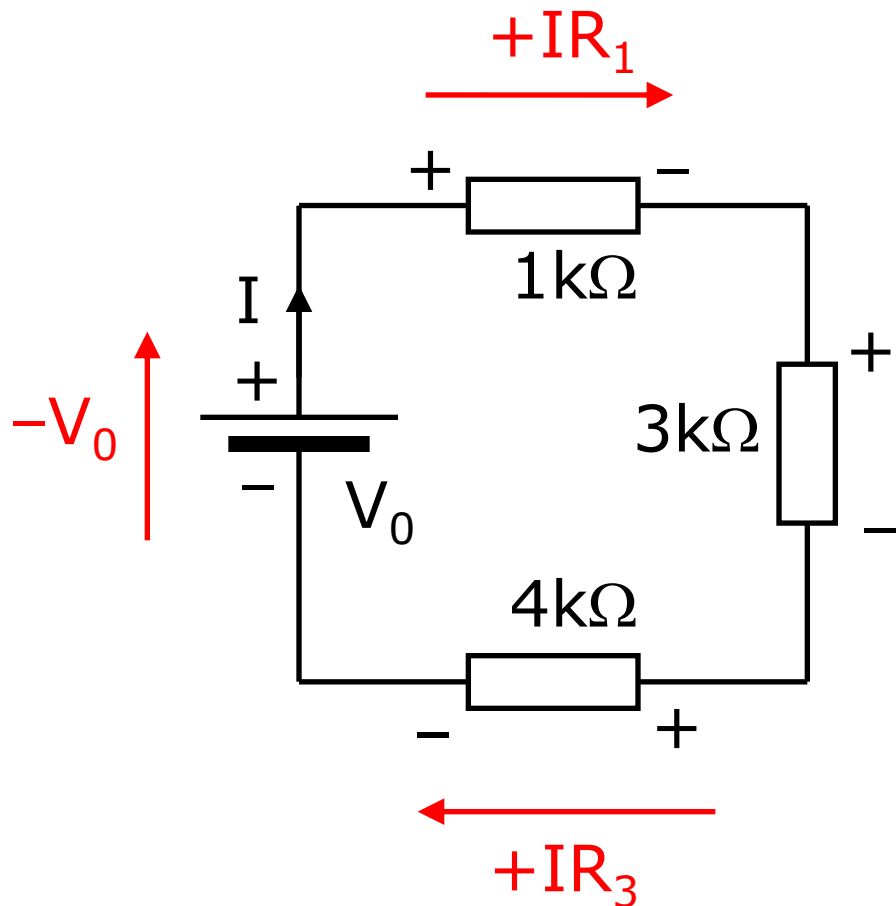


$$5\text{V} = I(1 + 3 + 4)\text{k}\Omega$$

$$I = \frac{5\text{V}}{8000\Omega} = 0.625\text{mA}$$


$$V_{R2} = 0.625\text{mA} \times 3\text{k}\Omega = 1.9\text{V}$$

Series / parallel circuits

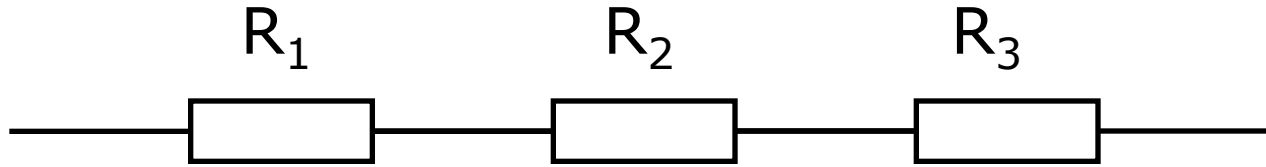

$$R_T = \sum_n R_n$$

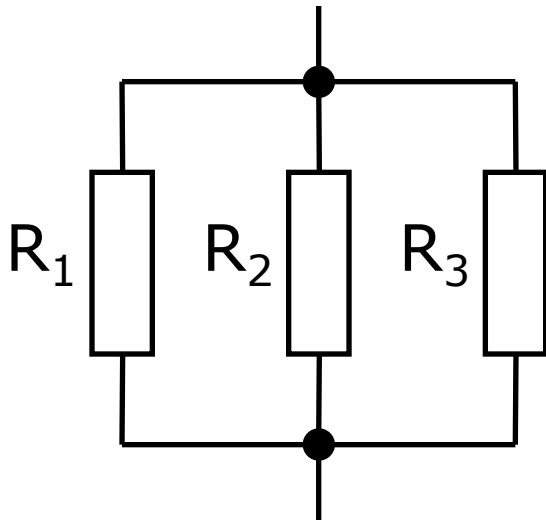
Resistors in series: $R_{\text{Total}} = R_1 + R_2 + R_3 \dots$



Resistors in parallel


$$\begin{aligned} \frac{1}{R_T} &= \sum_n \frac{1}{R_n} \\ &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots \end{aligned}$$

Two parallel resistors:

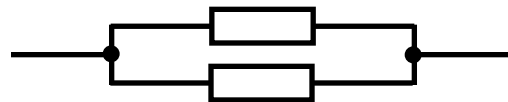

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

Potential divider

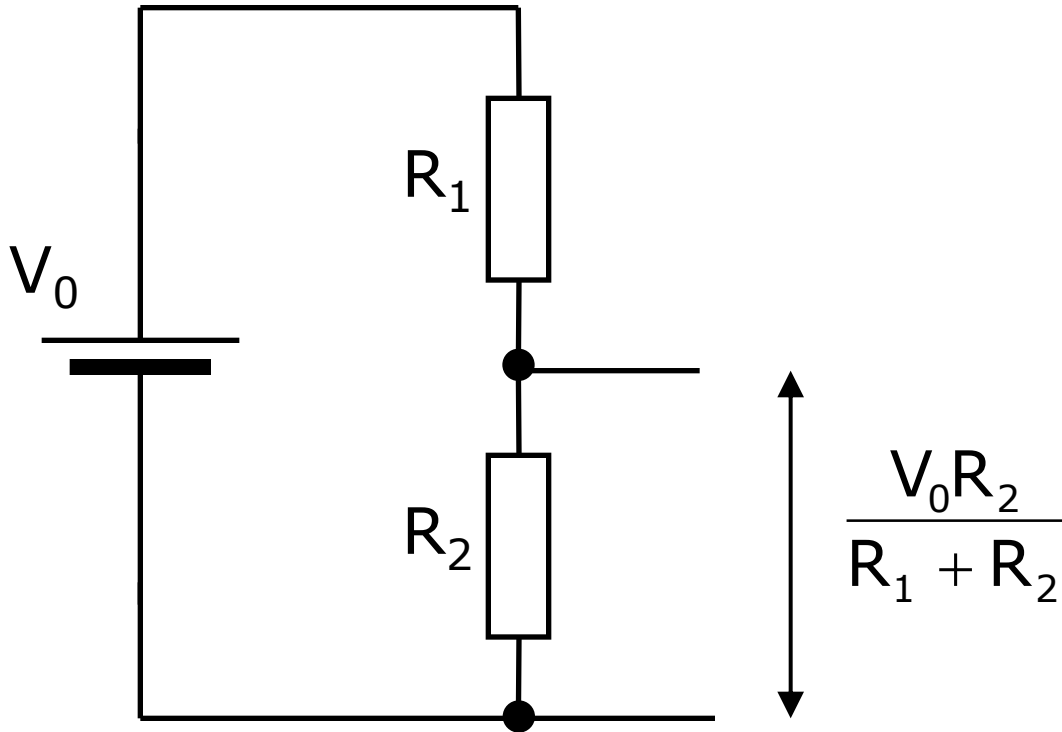


USE PASSIVE SIGN CONVENTION!!!

Show on blackboard

Mesh currents
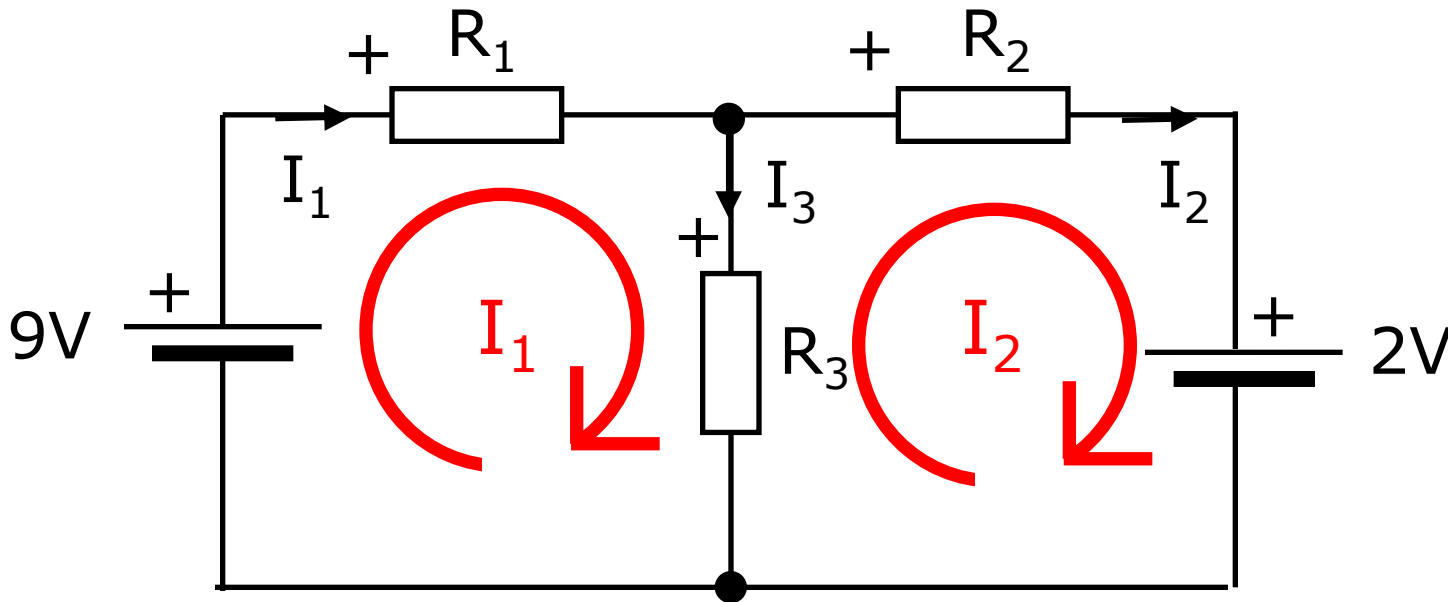
$$\begin{aligned} R_1 &= 3\text{k}\Omega \\ R_2 &= 2\text{k}\Omega \\ R_3 &= 6\text{k}\Omega \end{aligned}$$



First job: Label loop currents in all **interior** loops

Second job: **USE PASSIVE SIGN CONVENTION!!!**


Third job: Apply KCL to nodes sharing loop currents

Define: Currents Entering Node are positive

$$I_1 - I_2 - I_3 = 0 \rightarrow I_3 = I_1 - I_2$$

Mesh currents
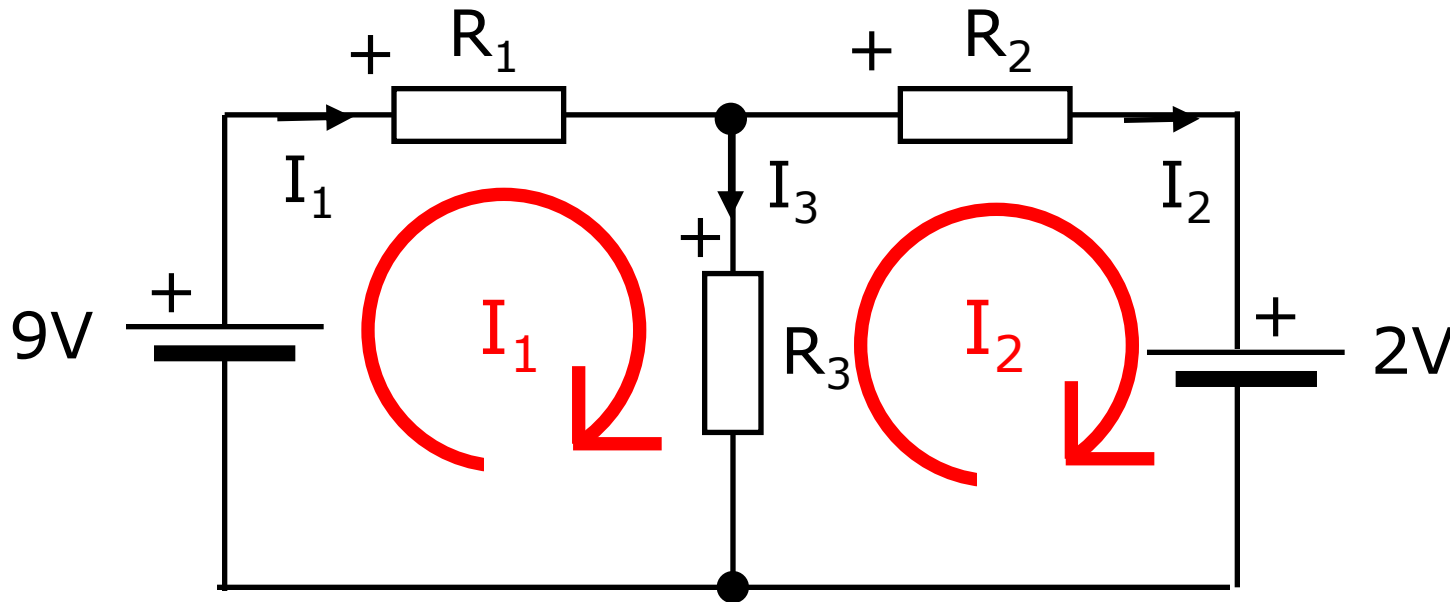
$$\begin{aligned}R_1 &= 3\text{k}\Omega \\ R_2 &= 2\text{k}\Omega \\ R_3 &= 6\text{k}\Omega\end{aligned}$$




Fourth job: Apply Kirchhoff's Voltage law around each loop.

Last job: USE Ohm's law and solve equations.

Mesh currents
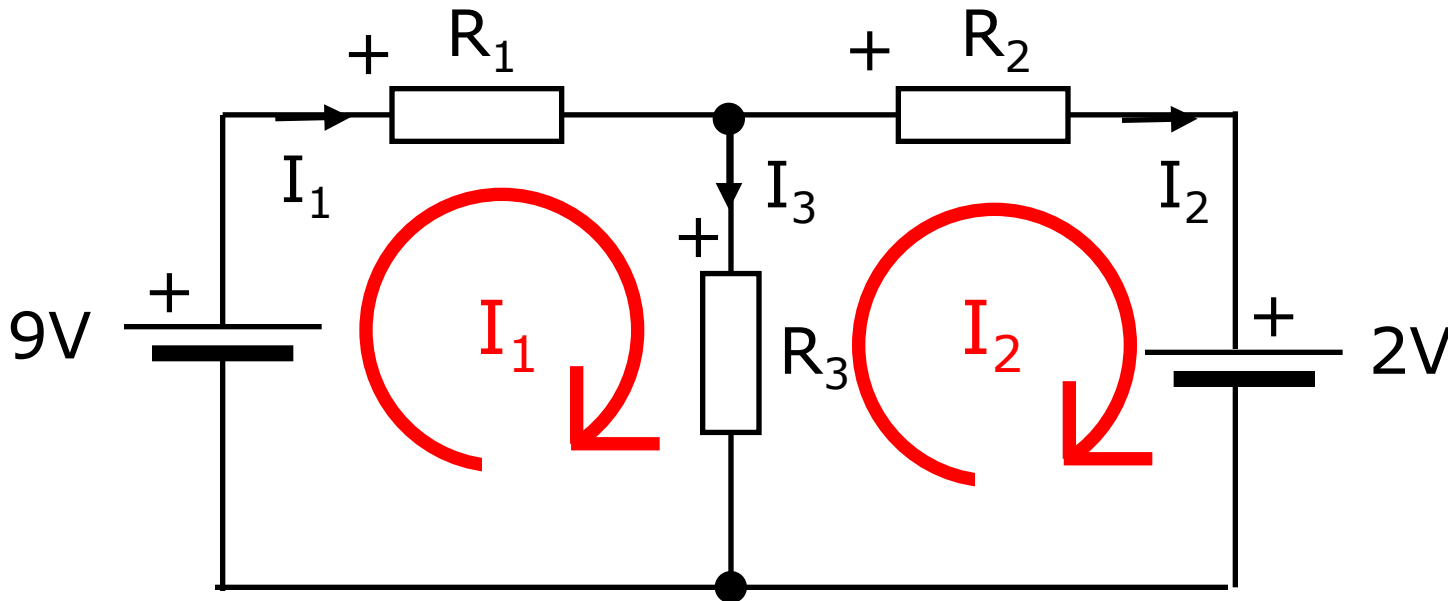
$$\begin{aligned}R_1 &= 3\text{k}\Omega \\ R_2 &= 2\text{k}\Omega \\ R_3 &= 6\text{k}\Omega\end{aligned}$$



$$-9V + I_1 R_1 + I_3 R_3 = 0 \quad I_3 = I_1 - I_2$$

$$-I_3 R_3 + I_2 R_2 + 2V = 0$$

Solve simultaneous equations

$$9V/\text{k}\Omega = 9I_1 - 6I_2$$

$$-2V/\text{k}\Omega = -6I_1 + 8I_2$$


$$\rightarrow I_2 = 1 \text{ mA}$$

$$I_1 = \frac{5}{3} \text{ mA} \quad I_3 = \frac{2}{3} \text{ mA}$$

$$V_3 = R_3 I_3 = 4 \text{ V}$$

Node voltages
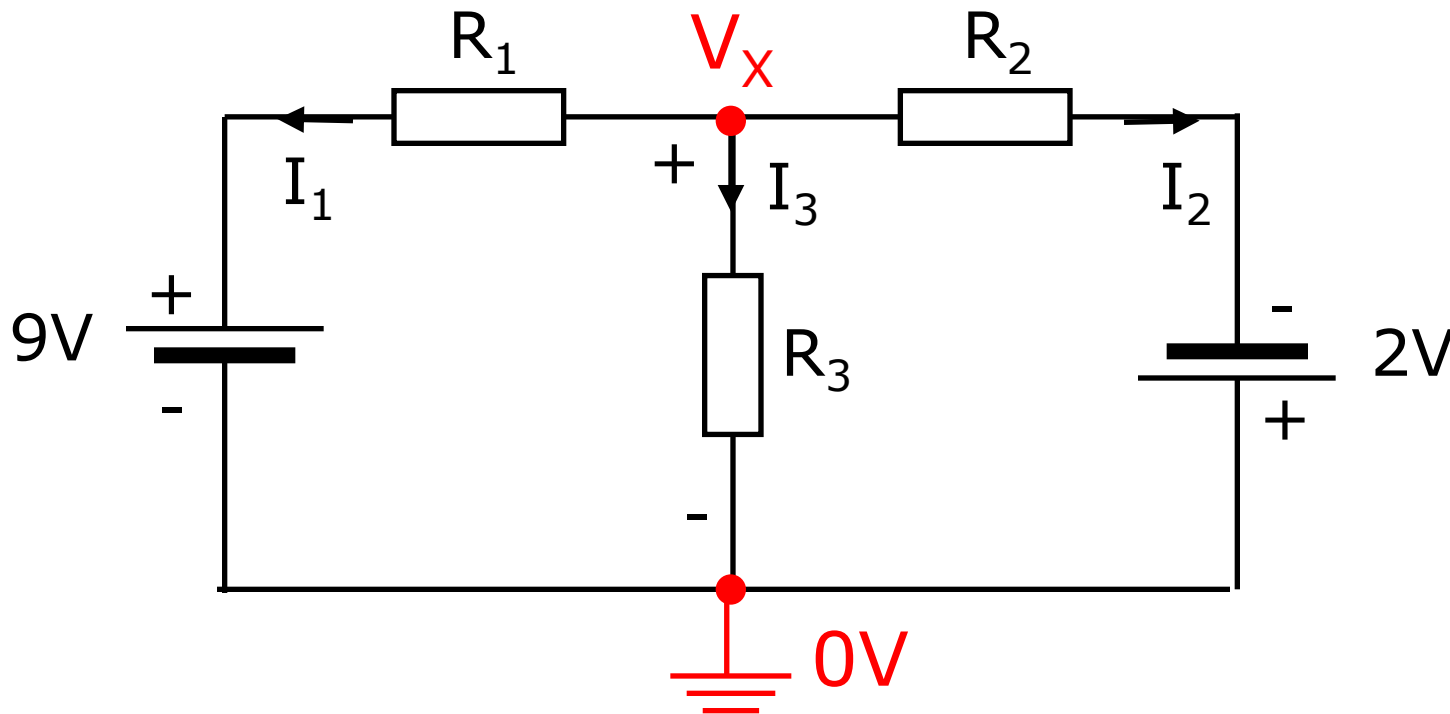
$$\begin{aligned}R_1 &= 3\text{k}\Omega \\ R_2 &= 2\text{k}\Omega \\ R_3 &= 6\text{k}\Omega\end{aligned}$$



Step 1: Choose a ground node!


Step 2: Label V's and I's on all nodes

Step 3: Apply KVL to find ΔV across resistors

Step 4: Apply KCL and ohms law using the tricks

Node voltages

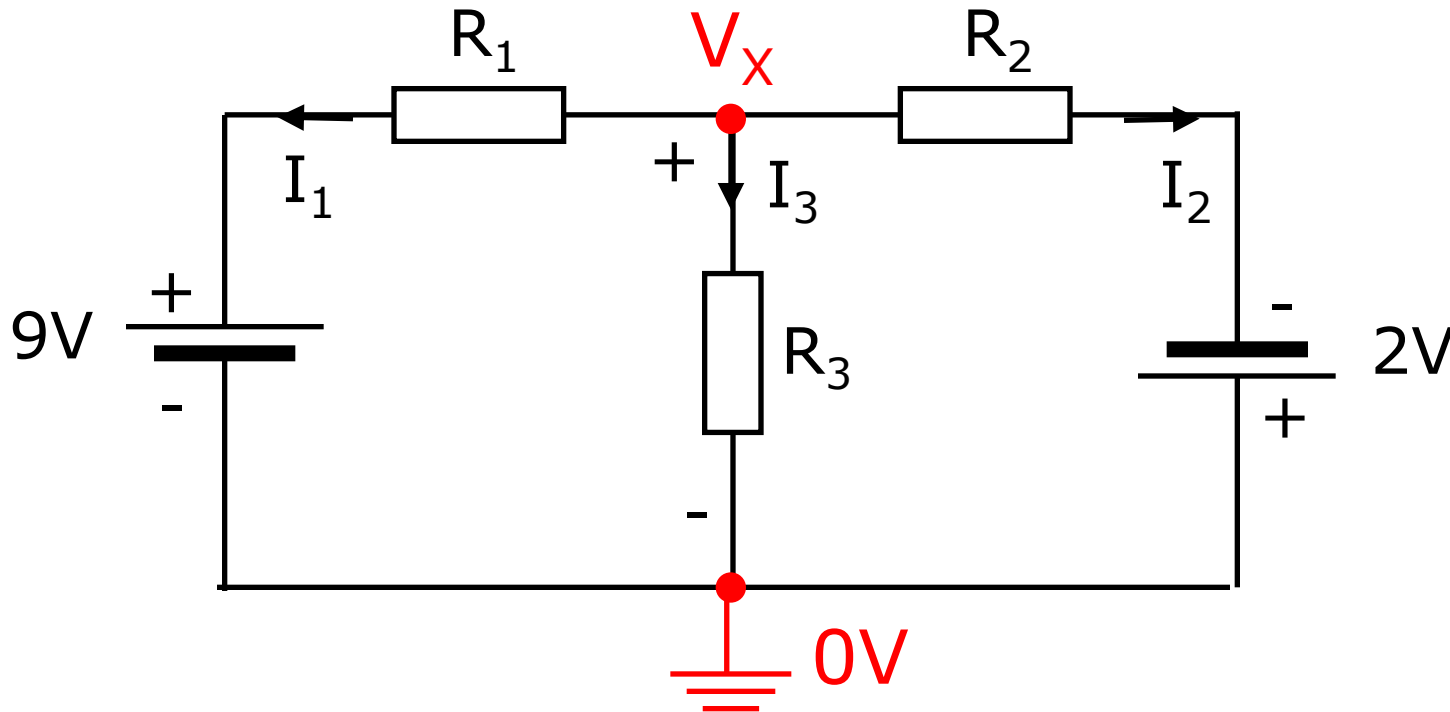
$$\begin{aligned} R_1 &= 3\text{k}\Omega \\ R_2 &= 2\text{k}\Omega \\ R_3 &= 6\text{k}\Omega \end{aligned}$$



$$\begin{aligned} 0 &= I_2 + I_3 + I_1 \\ 0 &= \frac{V_x - (-2V)}{R_2} + \frac{V_x}{R_3} + \frac{V_x - 9V}{R_1} \end{aligned}$$

*All currents leave all labeled nodes
And apply $\Delta V/R$ to each current.
Only one equation,
Mesh analysis would give two.*

USE PASSIVE SIGN CONVENTION!!!

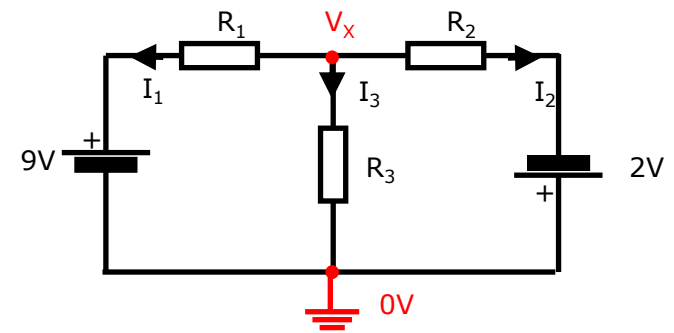

$$0 = I_2 + I_3 + I_1$$

$$0 = \frac{V_x - (-2V)}{R_2} + \frac{V_x}{R_3} + \frac{V_x - 9V}{R_1}$$

$$V_x \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_1} \right) = \frac{9V}{R_1} - \frac{2V}{R_2} = 3\text{mA} - 1\text{mA} = 2\text{mA}$$

$$V_x \left(\frac{1}{2} + \frac{1}{6} + \frac{1}{3} \right) \frac{1}{\text{k}\Omega} = 2\text{mA}$$


$$\frac{V_x}{1\text{k}\Omega} = 2\text{mA} \rightarrow V_x = 2V$$

$$I_1 = \frac{2V - 9V}{3\text{k}\Omega} = -\frac{7}{3}\text{mA} \quad I_2 = \frac{2V + 2V}{2\text{k}\Omega} = 2\text{mA}$$


$$I_3 = \frac{2V}{6\text{k}\Omega} = \frac{1}{3}\text{mA}$$

Thevenin's theorem

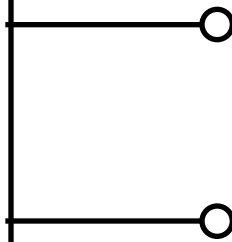Any **linear** network
of voltage/current
sources and
resistors



≡

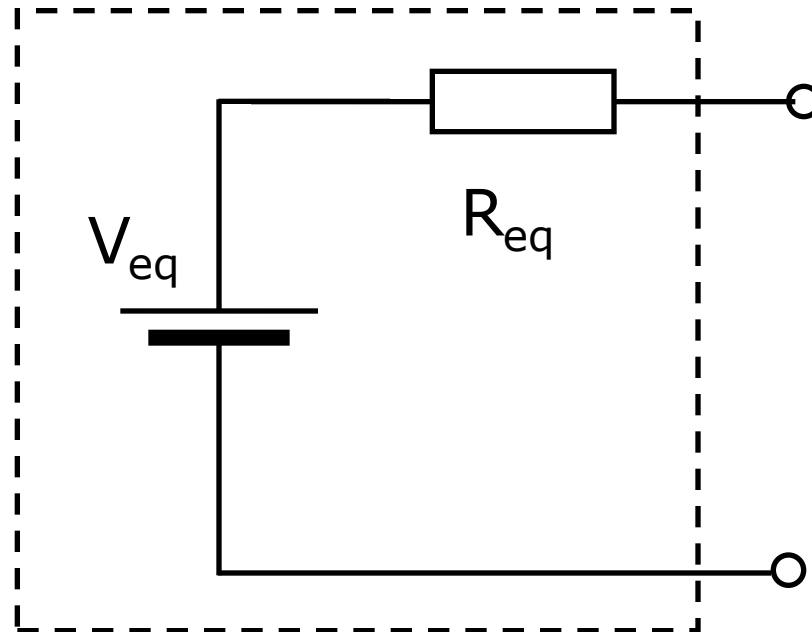


Equivalent circuit

In Practice, to find V_{eq} , R_{eq} ...

$$R_L \rightarrow \infty \text{ (open circuit)} \quad I_L \rightarrow 0 \quad V_{eq} = V_{OS}$$

$$R_L \rightarrow 0 \text{ (short circuit)} \quad V_L \rightarrow 0 \quad R_{eq} = \frac{V_{OS}}{I_{SS}}$$

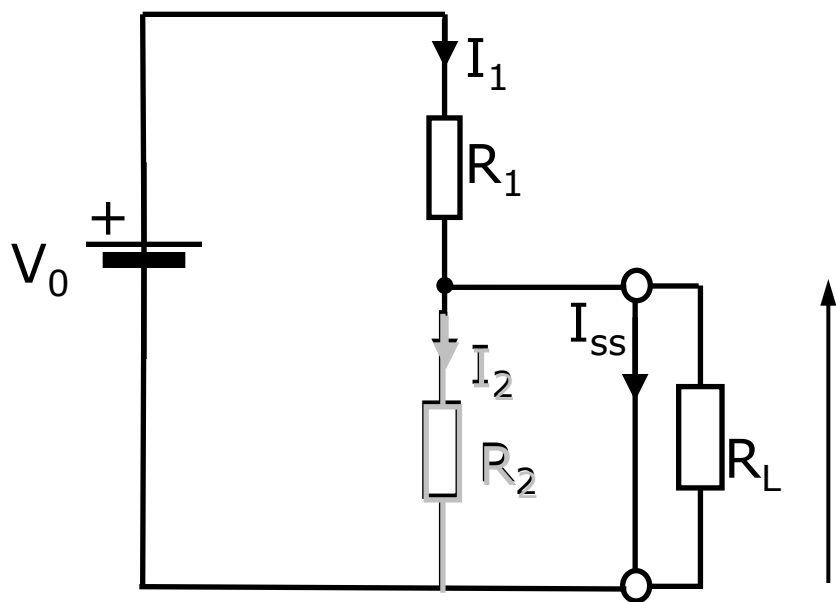R_{eq} = resistance between terminals when all voltages sources shorted – **Warning! This is not always obvious!**



$$V_{os} = V_0 \frac{R_2}{R_1 + R_2}$$


$$I_{ss} = \frac{V_0}{R_1}$$

$$R_{eq} = \frac{V_0 \frac{R_2}{R_1 + R_2}}{\frac{V_0}{R_1}} = \frac{R_1 R_2}{R_1 + R_2}$$


Norton's theorem

Any linear network
of voltage/current
sources and
resistors

≡

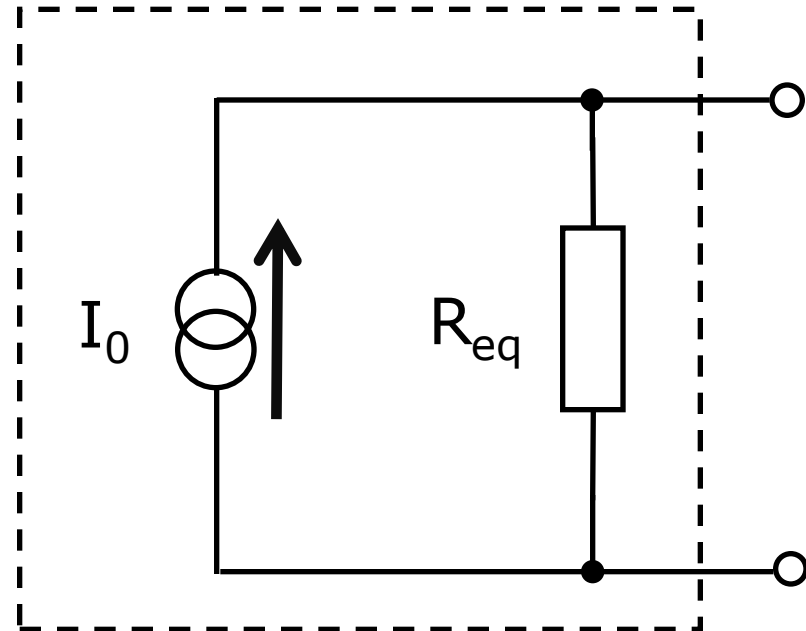


Equivalent circuit

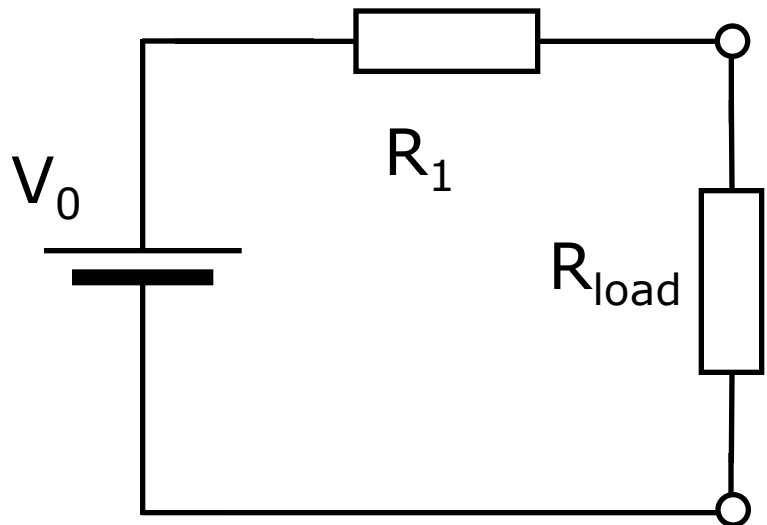

$$V_L = V_0 - I_L R_1$$



$$\therefore I_{eq} = \frac{V_0}{R_{eq}}$$



$$R_{eq} = R_1$$

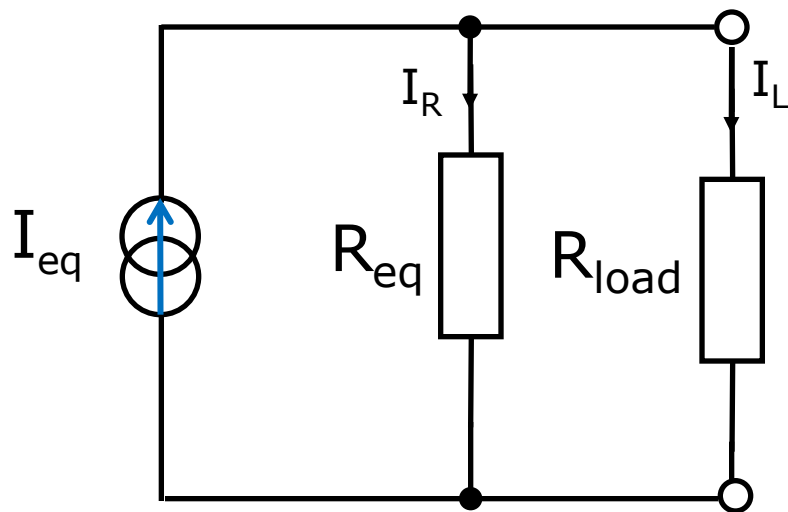

$$I_{eq} = I_R + I_L = \frac{V_L}{R_{eq}} + I_L$$


$$R_{eq} I_{eq} - R_{eq} I_L = V_L$$

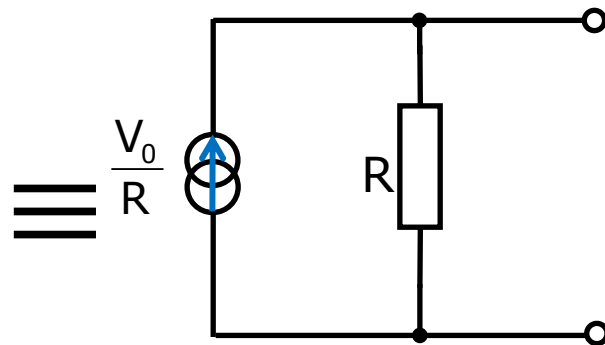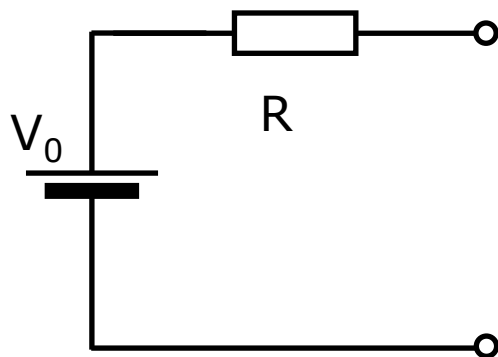

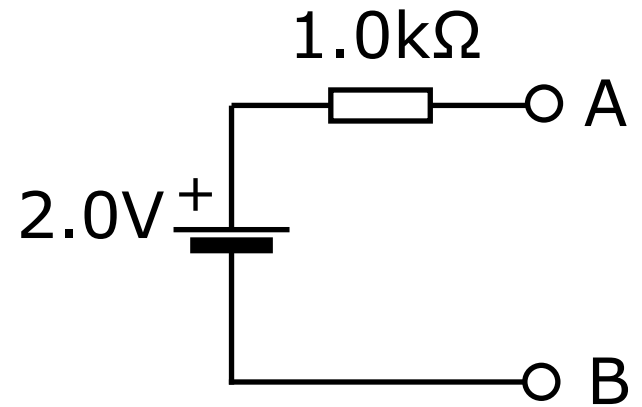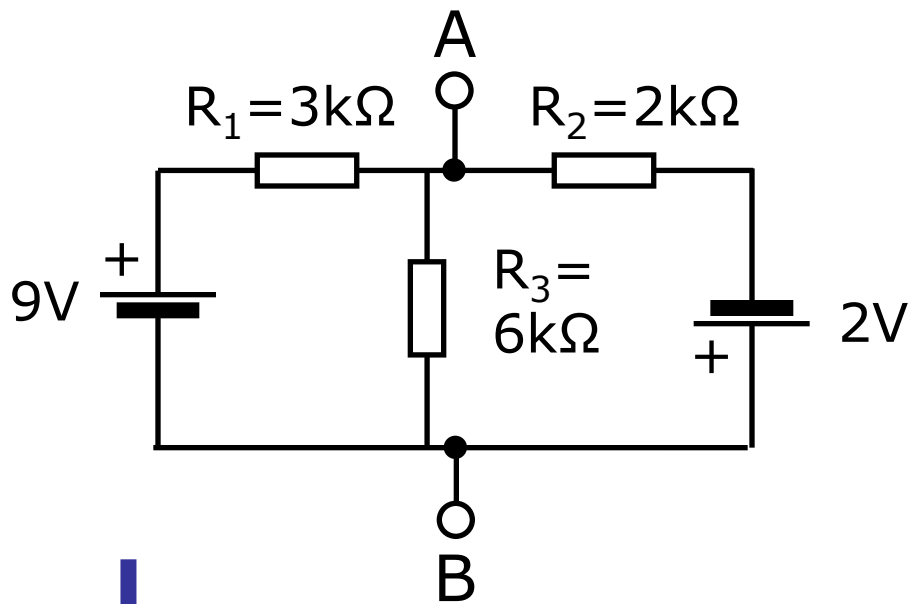

using Thevenin's theorem:

$$V_{OC} = V_{eq} = 2.0V$$


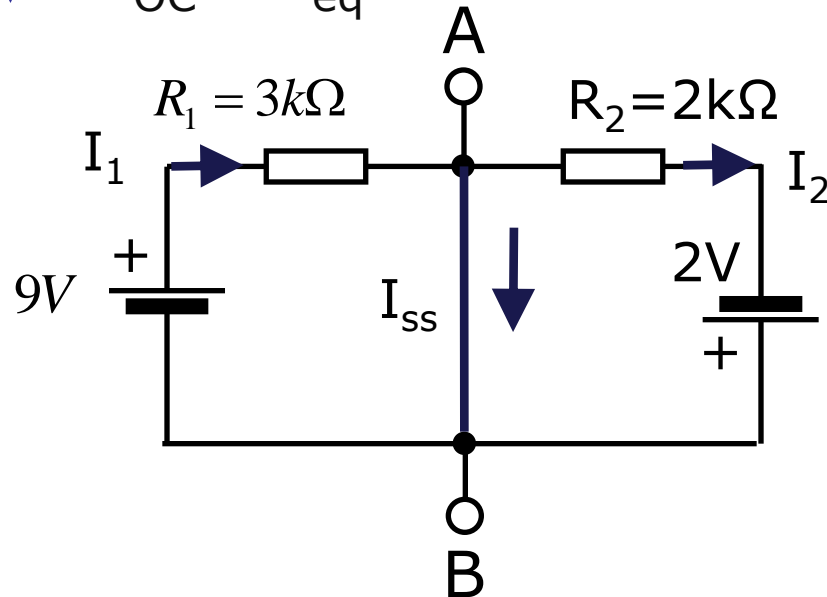


$$I_1 = \frac{9V}{3k\Omega} = 3ma$$

$$I_2 = \frac{2V}{2k\Omega} = 1ma$$

$$I_{ss} = I_1 - I_2 = 2ma$$
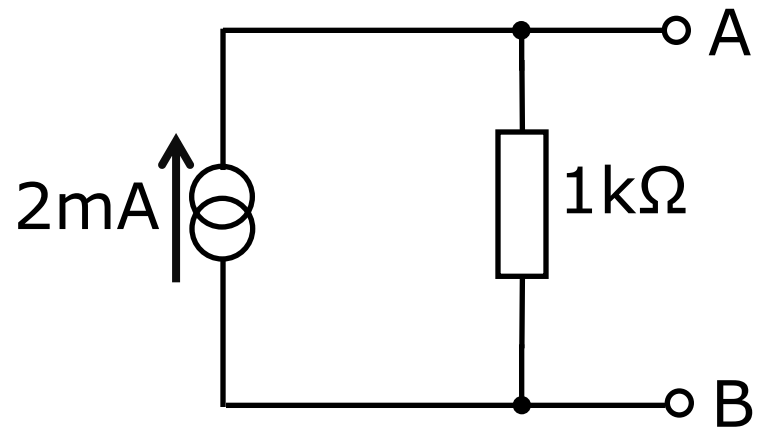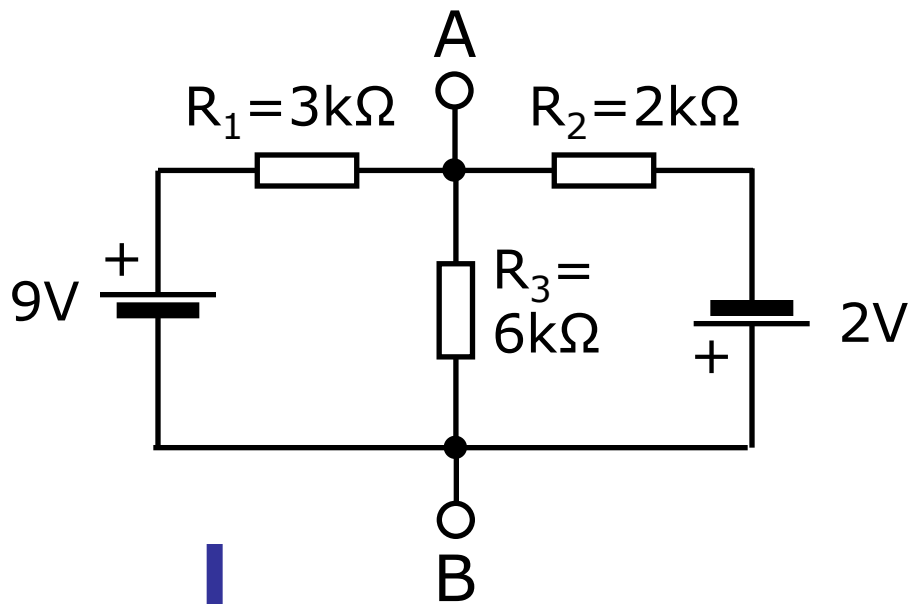
$$R_{eq} = \frac{V_{oc}}{I_{ss}} = 1.0k\Omega$$




using Norton's theorem:


Same procedure: Find I_{SS} and V_{OC}

$$I_{EQ} = I_{SS} \text{ and } R_{EQ} = V_{OC}/I_{SS}$$


Superposition

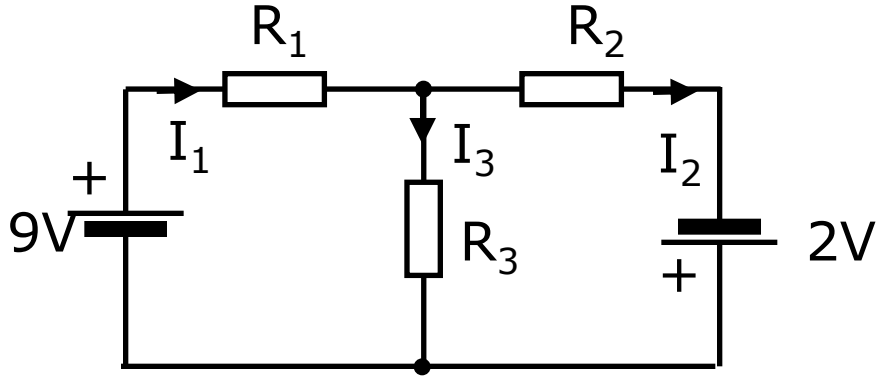

=

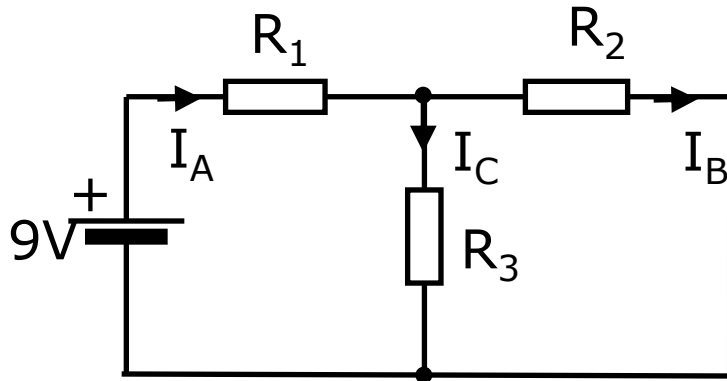

+

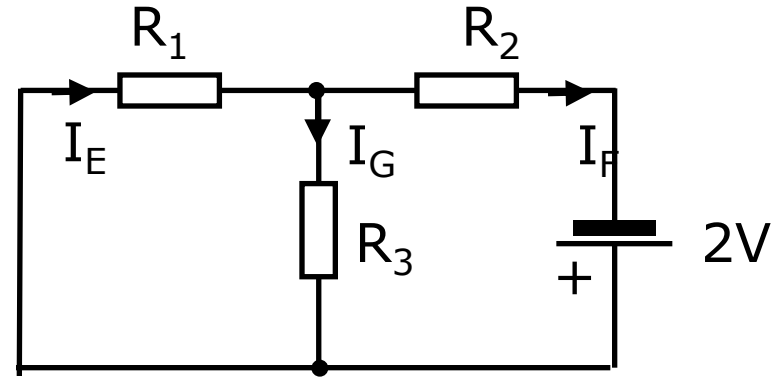


$$I_1 = I_A + I_E$$

$$I_2 = I_B + I_F$$

$$I_3 = I_C + I_G$$

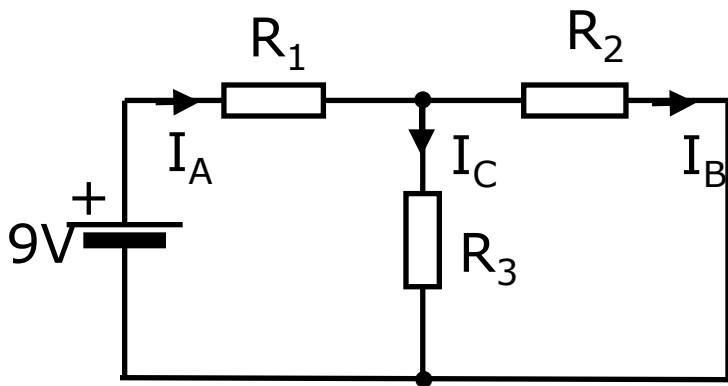Important: label *Everything* the same directions!




Example:
Superposition

$$R_1 = 3\text{k}\Omega$$

$$R_2 = 2\text{k}\Omega$$

$$R_3 = 6\text{k}\Omega$$

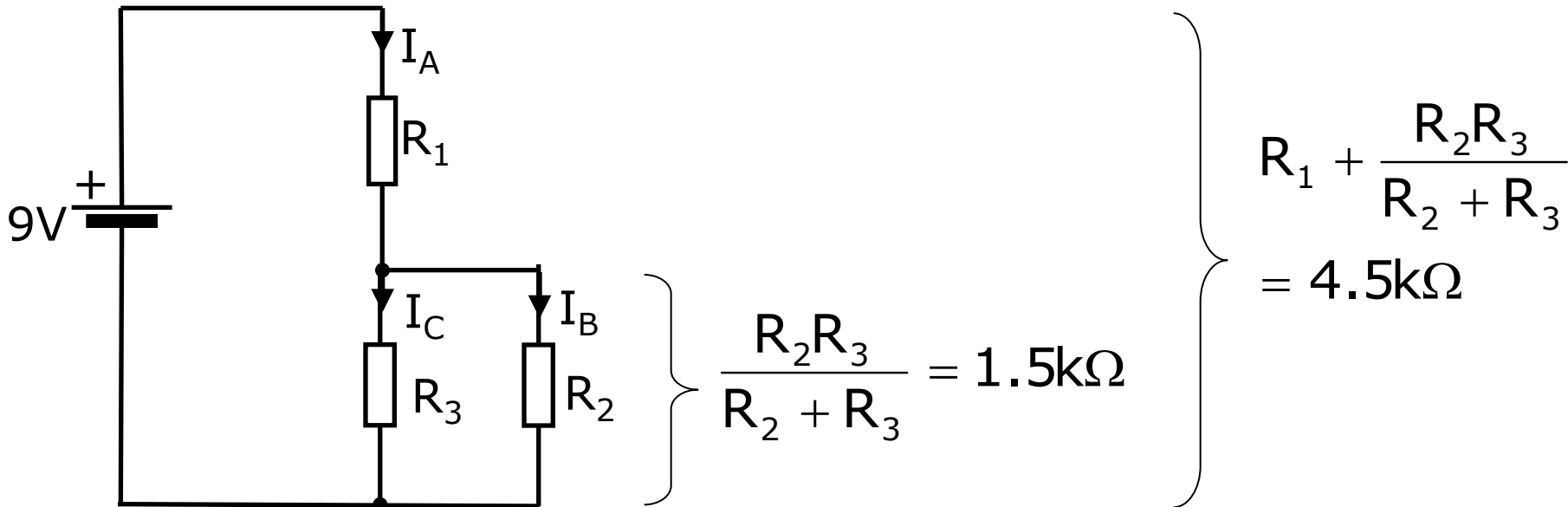


$$I_A = \frac{9\text{V}}{4.5\text{k}\Omega} = 2\text{mA}$$

$$I_C R_3 = I_B R_2 = 9\text{V} \frac{1.5}{4.5} = 3\text{V}$$

$$I_C = 0.5\text{mA}$$


$$I_B = 1.5\text{mA}$$

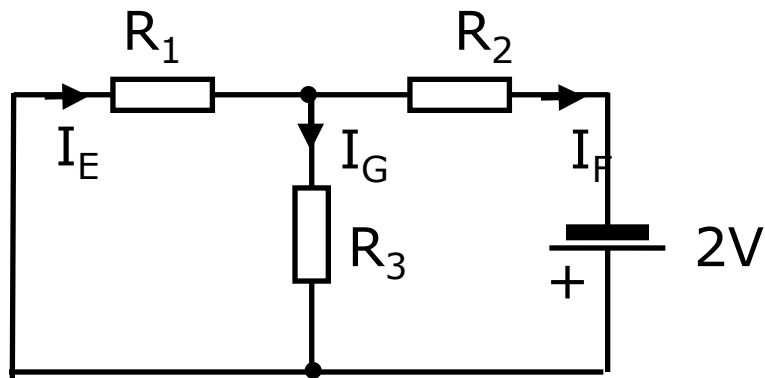

$$R_1 = 3k\Omega$$

$$R_2 = 2k\Omega$$

$$R_3 = 6k\Omega$$

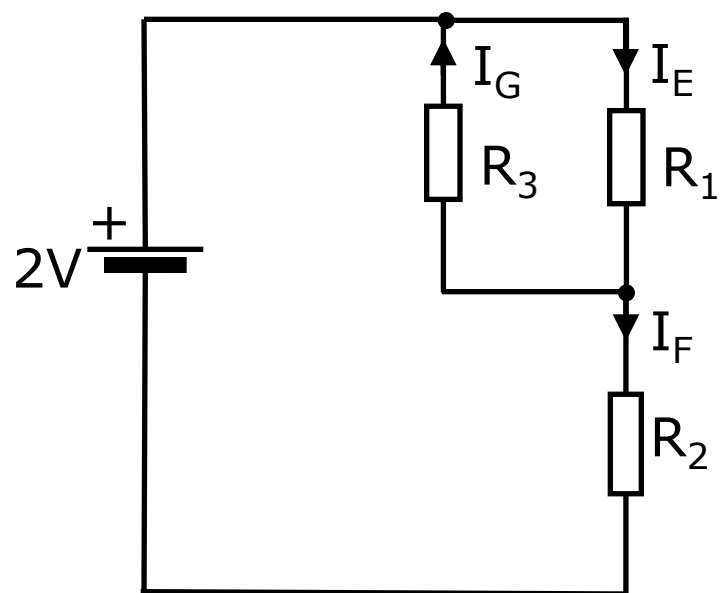

$$\frac{R_1 R_3}{R_1 + R_3} = 2k\Omega$$


$$R_2 + \frac{R_1 R_3}{R_1 + R_3} = 4k\Omega$$

$$I_F = \frac{2V}{4k\Omega} = 0.5mA$$


$$-I_G R_3 = I_E R_1 = 2V \frac{2}{4} = 1V$$

$$I_G = -\frac{1}{6}mA$$


$$I_E = \frac{1}{3}mA$$

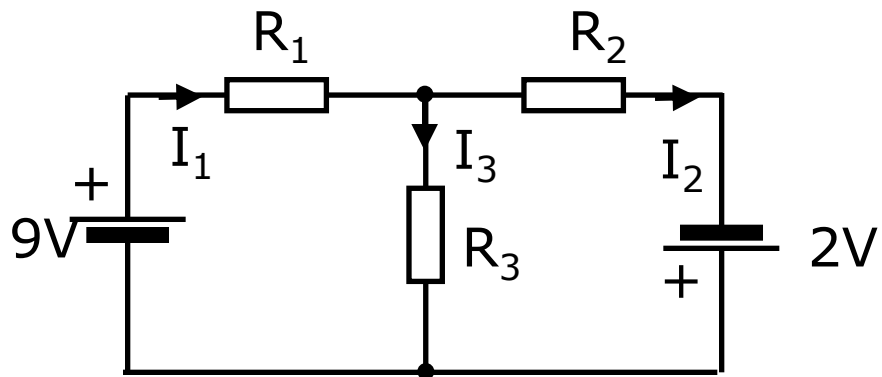

=

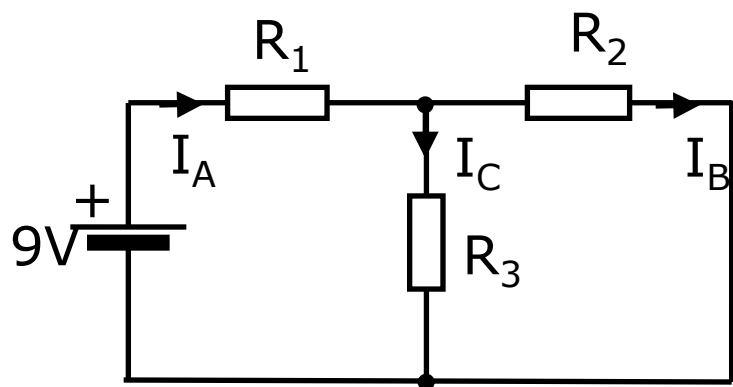

+

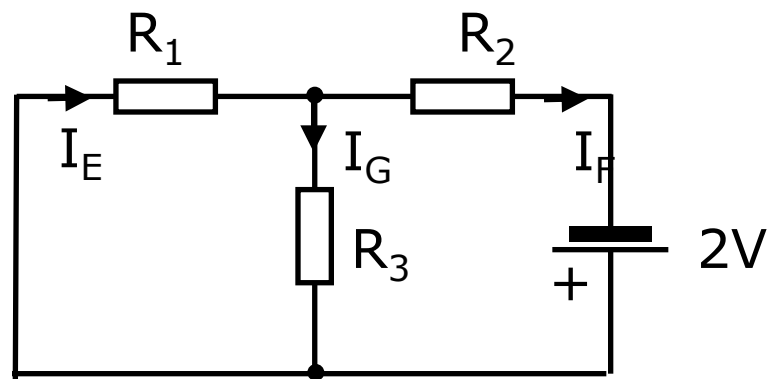

$$I_1 = I_A + I_E$$

$$I_1 = \left(2 + \frac{1}{3}\right) \text{mA}$$

$$= \frac{7}{3} \text{mA}$$

$$I_2 = I_B + I_F$$

$$I_2 = (1.5 + 0.5) \text{mA}$$


$$= 2 \text{mA}$$

$$I_3 = I_C + I_G$$

$$I_3 = \left(0.5 - \frac{1}{6}\right) \text{mA}$$

$$= \frac{1}{3} \text{mA}$$

Matching: maximum power transfer

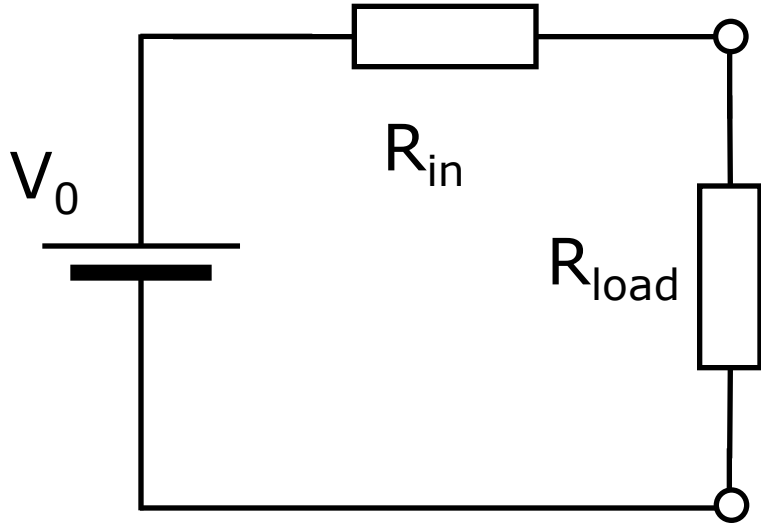

Find R_L to give maximum power in load

$$P = \frac{V_L^2}{R_L} = V_0^2 \frac{R_L^2}{(R_{in} + R_L)^2} \frac{1}{R_L}$$

$$\frac{dP}{dR_L} = V_0^2 \frac{(R_{in} + R_L)^2 - 2R_L(R_{in} + R_L)}{(R_{in} + R_L)^4} = 0$$

$$R_{in} + R_L - 2R_L = 0$$

$$\therefore R_{in} = R_L$$

Maximum power transfer when $R_L = R_{in}$

Note – power dissipated half in R_L and half in R_{in}

Circuits have Consequences

- Problem:
 - My old speakers are 60W speakers.
 - Special 2-4-1 deal at El-Cheap-0 Acoustics on 120W speakers!!
 - (“Offer not seen on TV!”)
 - Do I buy them?
- Depends! 4 Ω , 8 Ω , or 16 Ω speakers?
- **Why does this matter?**





And Now for Something Completely Different