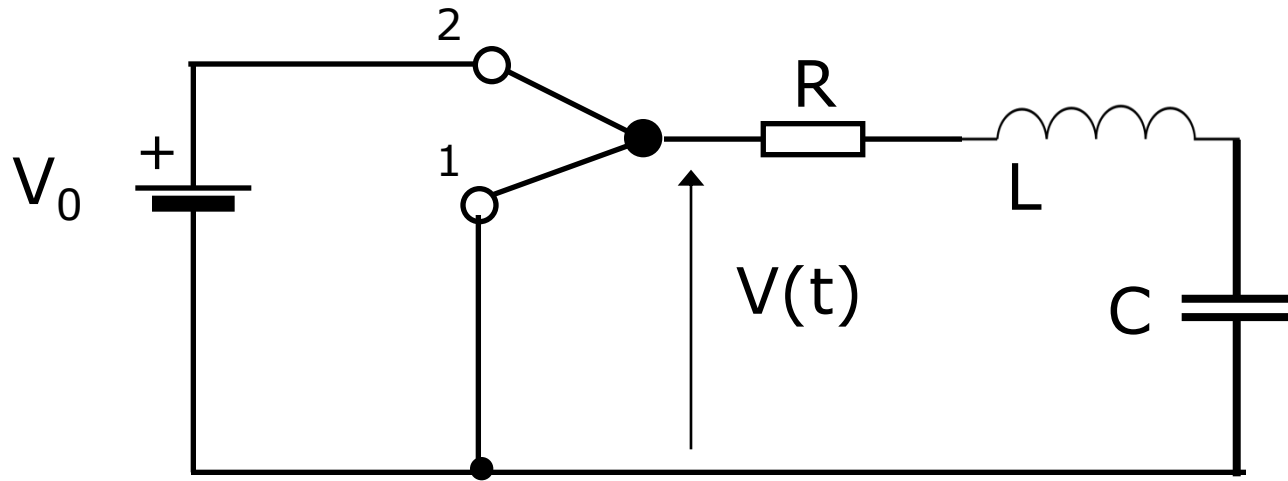


LCR circuit



$$V(t) = \begin{cases} 0 & \text{for } t < 0 \\ V_0 & \text{for } t \geq 0 \end{cases}$$

$$I(t) = 0 \text{ for } t < 0$$

$$t \geq 0$$

$$V_R + V_L + V_C = V_0$$

$$IR + L \frac{dI}{dt} + \frac{Q}{C} = V_0$$

$$\frac{d^2 I}{dt^2} + \frac{R}{L} \frac{dI}{dt} + \frac{1}{LC} I = 0$$

$$I = ke^{\lambda t} \quad \text{trial solution}$$

$$\lambda^2 + \lambda \frac{R}{L} + \frac{1}{LC} = 0 \quad \text{characteristic equation}$$


$$\begin{aligned} \lambda &= -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} \\ &= -\gamma \pm \sqrt{\gamma^2 - \omega_0^2} \end{aligned}$$

$$\gamma = \frac{R}{2L}$$

$$\omega_0^2 = \frac{1}{LC}$$

$$I = k_1 e^{\lambda_1 t} + k_2 e^{\lambda_2 t} \quad \text{general solution}$$

LCR circuit – initial conditions

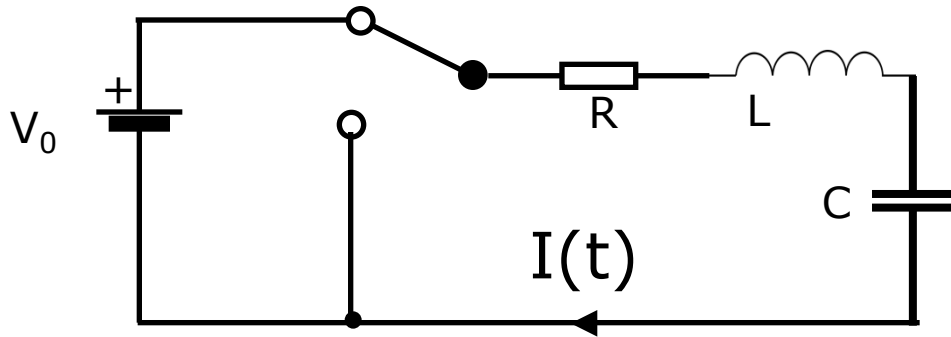

Initial conditions $I(0)$, $\frac{dI}{dt}(0)$?

No energy stored $W_L = \frac{1}{2} LI^2 = 0 \rightarrow I(0) = 0$

$W_C = \frac{1}{2} CV^2 = 0 \rightarrow V_C(0) = 0$

$$I(0)R + L \frac{dI}{dt}(0) + V_C = V_0$$

$$L \frac{dI}{dt}(0) = V_0$$

$$\frac{dI}{dt}(0) = \frac{V_0}{L}$$

LCR circuit

$$I = k_1 e^{\lambda_1 t} + k_2 e^{\lambda_2 t}$$

$$\lambda = -\gamma \pm \sqrt{\gamma^2 - \omega_0^2}$$

$$\gamma^2 > \omega_0^2$$

$$\lambda_{1,2} = -\gamma \pm \beta$$

$$\beta = \sqrt{\gamma^2 - \omega_0^2}$$

$$\gamma = \frac{R}{2L}$$

$$\omega_0^2 = \frac{1}{LC}$$


$$I(t \geq 0) = k_1 e^{(-\gamma + \beta)t} + k_2 e^{(-\gamma - \beta)t}$$

$$I(0) = k_1 + k_2 = 0 \rightarrow k_1 = -k_2$$

$$\frac{dI}{dt}(0) = k_1(-\gamma + \beta) - k_2(\gamma + \beta) = \frac{V_0}{L}$$

$$k_1 = \frac{V_0}{2\beta L}$$
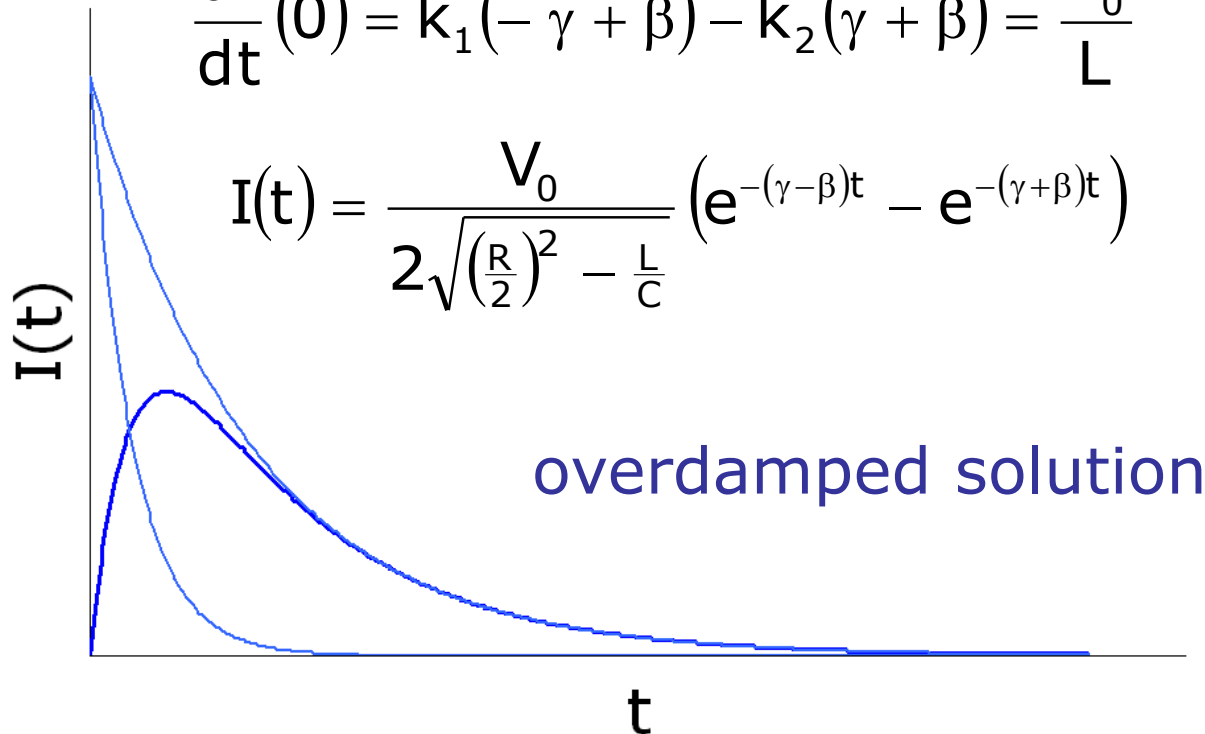
$$I(t) = \frac{V_0}{2\sqrt{\left(\frac{R}{2}\right)^2 - \frac{L}{C}}} \left(e^{-(\gamma - \beta)t} - e^{-(\gamma + \beta)t} \right)$$



LCR circuit

$$\lambda = -\gamma \pm \sqrt{\gamma^2 - \omega_0^2}$$

$$\gamma^2 = \omega_0^2$$


$$\lambda_1 = \lambda_2 = -\gamma$$

$$I = (k_1 + k_2 t)e^{\lambda t}$$

$$I(0) = 0 \rightarrow k_1 = 0$$

$$\frac{dI}{dt} = (-\gamma(k_1 + k_2 t) + k_2)e^{-\gamma t} \rightarrow k_2 = \left. \frac{dI}{dt} \right|_{t=0} = \frac{V_0}{L}$$
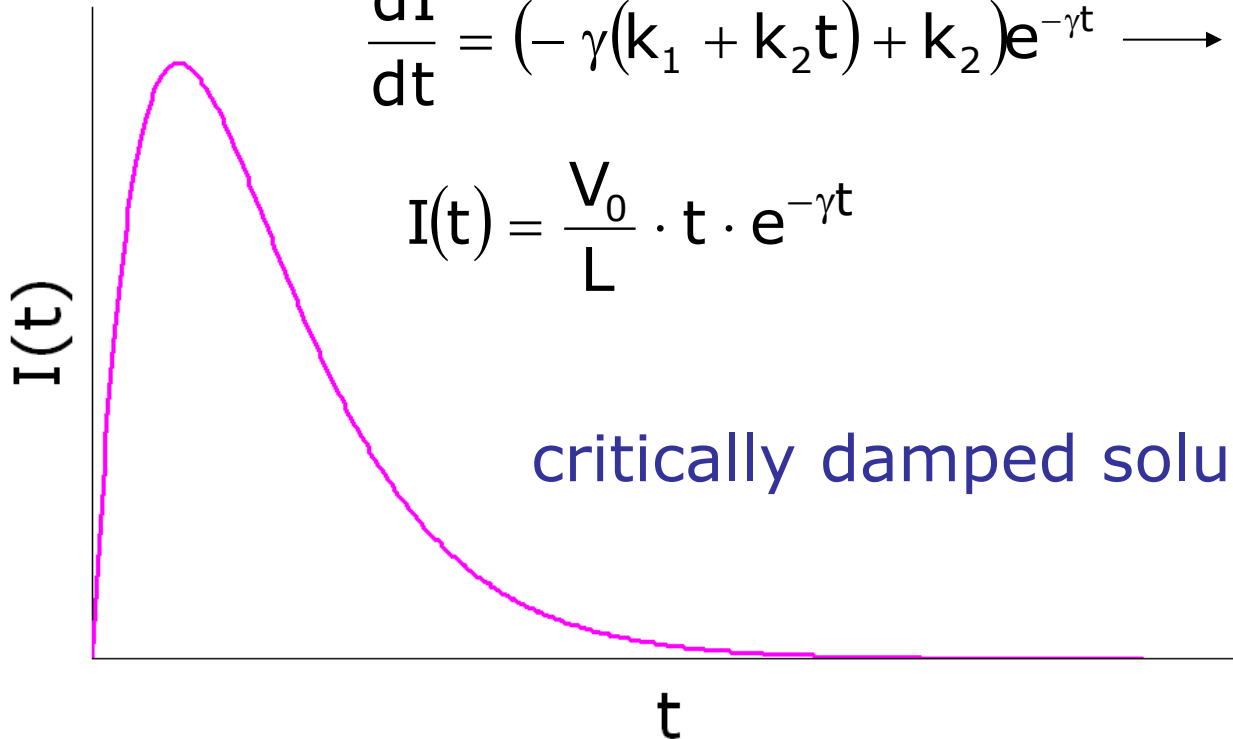
$$I(t) = \frac{V_0}{L} \cdot t \cdot e^{-\gamma t}$$




critically damped solution


LCR circuit

$$I = k_1 e^{\lambda_1 t} + k_2 e^{\lambda_2 t} \quad \lambda = -\gamma \pm \sqrt{\gamma^2 - \omega_0^2}$$

$$\gamma^2 < \omega_0^2$$

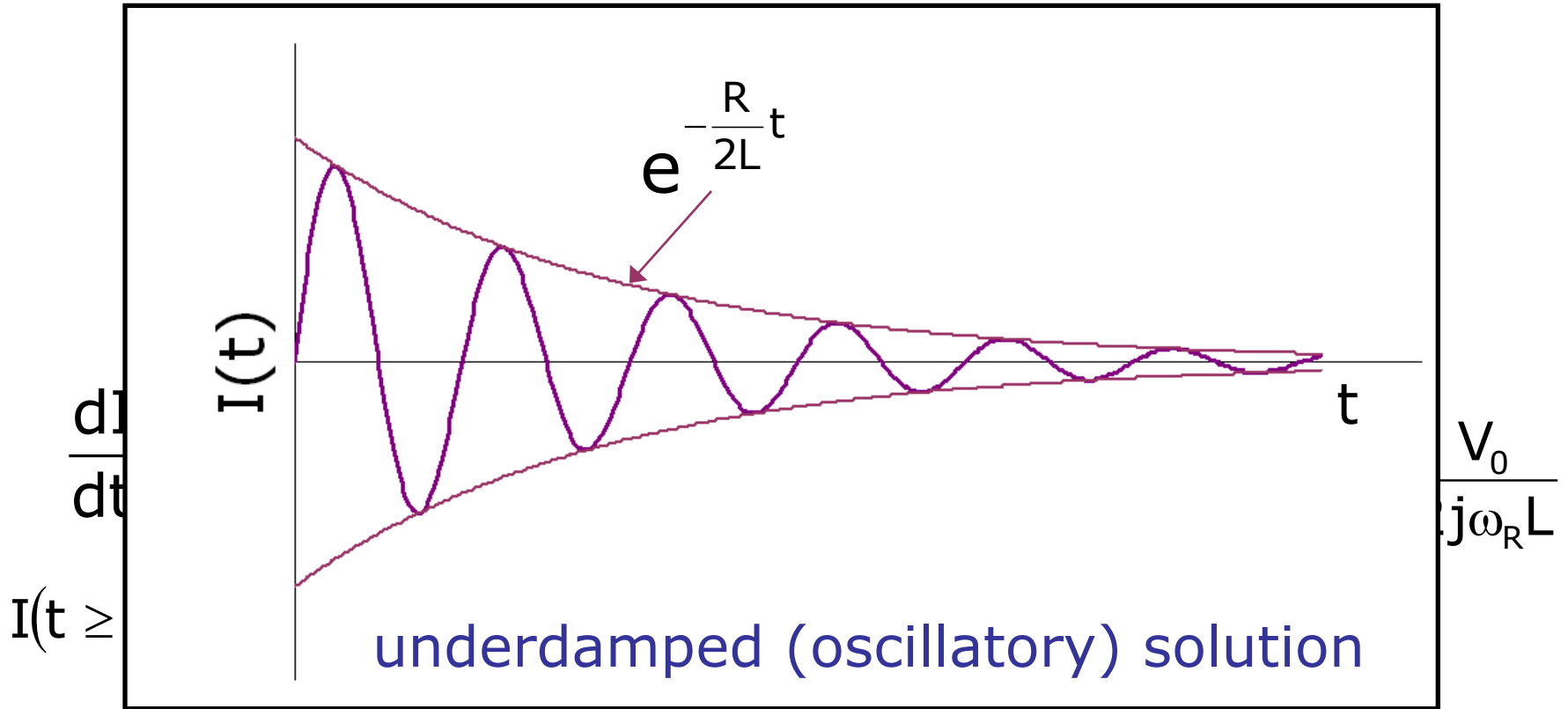
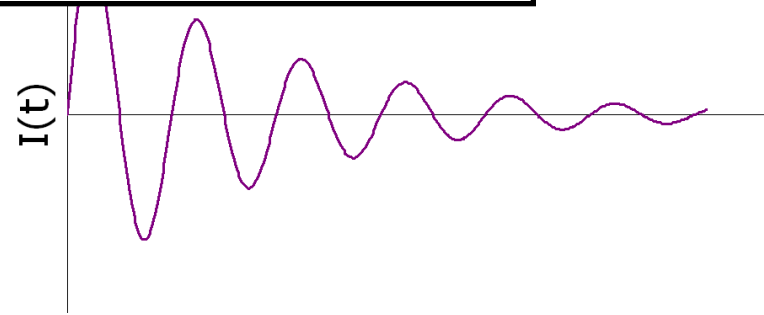
$$I(t \geq 0) = \frac{V_0}{\sqrt{\frac{L}{C} - \left(\frac{R}{2}\right)^2}} e^{-\gamma t} \cdot \sin(\omega_R t)$$



LCR circuit

$$\frac{d^2 I}{dt^2} + \frac{R}{L} \frac{dI}{dt} + \frac{1}{LC} I = 0$$

$$I = k_1 e^{\lambda_1 t} + k_2 e^{\lambda_2 t} \quad \lambda = -\gamma \pm \sqrt{\gamma^2 - \omega_0^2}$$

overdamped solution

$$\gamma = \frac{R}{2L}$$

$$\omega_0^2 = \frac{1}{LC}$$

$$\gamma^2 > \omega_0^2 \quad \lambda_{1,2} = -\gamma \pm \beta \quad \beta \text{ is real}$$

critically damped solution

$$\gamma^2 = \omega_0^2 \quad \lambda_1 = \lambda_2 = -\gamma \quad I = (k_1 + k_2 t) e^{\lambda t}$$

underdamped (oscillatory) solution

$$\begin{aligned} \gamma^2 < \omega_0^2 \quad \lambda_{1,2} &= -\gamma \pm \mathbf{j} \sqrt{\omega_0^2 - \gamma^2} \\ &= -\gamma \pm \mathbf{j} \omega_R \end{aligned}$$

LCR circuit

$$\frac{d^2 I}{dt^2} + \frac{R}{L} \frac{dI}{dt} + \frac{1}{LC} I = 0$$

$$\gamma = \frac{R}{2L}$$

$$\omega_0^2 = \frac{1}{LC}$$

$$I = k_1 e^{\lambda_1 t} + k_2 e^{\lambda_2 t} \quad \lambda = -\gamma \pm \sqrt{\gamma^2 - \omega_0^2}$$

overdamped solution

$$\gamma^2 > \omega_0^2 \quad I(t) = \frac{V_0}{2\sqrt{\left(\frac{R}{2}\right)^2 - \frac{1}{C}}} \left(e^{-(\gamma-\beta)t} - e^{-(\gamma+\beta)t} \right)$$

critically damped solution

$$\gamma^2 = \omega_0^2 \quad I(t) = \frac{V_0}{L} \cdot t \cdot e^{-\gamma t}$$

underdamped (oscillatory) solution

$$\gamma^2 < \omega_0^2 \quad I(t \geq 0) = \frac{V_0}{\sqrt{\frac{1}{C} - \left(\frac{R}{2}\right)^2}} e^{-\gamma t} \cdot \sin(\omega_R t)$$

CP2 September 2003

7. Consider a capacitor C , which has an initial charge Q_0 , in series with an inductor L , a resistance R and a switch. At time $t = 0$ the switch is closed and the capacitor starts to discharge through L and R . Show that the differential equation for the charge Q on the capacitor can be written as

$$\frac{d^2Q}{dt^2} + 2\alpha\frac{dQ}{dt} + \omega_0^2Q = 0.$$

Give expressions for α and ω_0 in terms of L , C and R .

[6]

By writing $Q = qe^{-\alpha t}$, where q is a function of t , show that


$$\frac{d^2q}{dt^2} + (\omega_0^2 - \alpha^2)q = 0,$$

and give the general solution for Q when $\omega_0^2 = \alpha^2$.

[5]

For $L = 10 \text{ mH}$, $R = 200 \Omega$ and $\omega_0^2 = \alpha^2$, find at what time the current reaches its maximum value after the switch is closed.

[9]

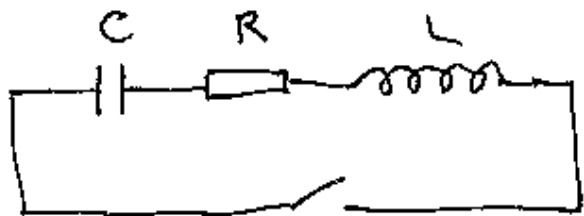

$$V_C + V_R + V_L = 0$$

$$\frac{Q}{C} + IR + L \frac{dI}{dt} = 0$$

$$\text{but } I = \frac{dQ}{dt}$$

so

$$\frac{Q}{C} + \frac{dQ}{dt} R + L \frac{d^2Q}{dt^2} = 0$$

$$\frac{d^2Q}{dt^2} + \underbrace{\frac{R}{L}}_{2\alpha} \frac{dQ}{dt} + \underbrace{\frac{1}{LC}}_{\omega_0^2} Q = 0$$

Try solution $Q = q e^{-\alpha t}$

$$\dot{Q} = \dot{q} e^{-\alpha t} - \alpha q e^{-\alpha t}$$

$$\begin{aligned}\ddot{Q} &= \dot{q} e^{-\alpha t} - \alpha \dot{q} e^{-\alpha t} - \alpha \dot{q} e^{-\alpha t} + \alpha^2 q e^{-\alpha t} \\ &= \dot{q} e^{-\alpha t} - 2\alpha \dot{q} e^{-\alpha t} + \alpha^2 q e^{-\alpha t}\end{aligned}$$

$$\underbrace{(\ddot{q} - 2\alpha \dot{q} + \alpha^2 q)}_{\frac{d^2 Q}{dt^2}} e^{-\alpha t} + 2\alpha \underbrace{(\dot{q} - \alpha q)}_{\frac{dQ}{dt}} e^{-\alpha t} + \omega_0^2 \underbrace{q}_{Q} e^{-\alpha t} = 0$$

$$\rightarrow [\ddot{q} + (\omega_0^2 - \alpha^2) q] e^{-\alpha t} = 0$$

$$\rightarrow \ddot{q} + (\omega_0^2 - \alpha^2) q = 0$$

Solve $\ddot{q} + (\omega_0^2 - \alpha^2)q = 0$ when $\omega_0^2 = \alpha^2$

$$\dot{q} = 0$$

$$\dot{q} = A$$

$$q = At + B$$

So $Q = (At + B)e^{-\alpha t}$

$$\dot{Q} = (A - \alpha At - \alpha B)e^{-\alpha t}$$

at $t=0$ $Q = Q_0$ $\dot{Q} = 0$ (thanks to inductor)


$$\rightarrow B = Q_0$$

$$A = \alpha Q_0$$

$$= \omega_0 Q_0$$

$$Q(t) = Q_0(\omega_0 t + 1)e^{-\omega_0 t}$$

"Critically damped" solution

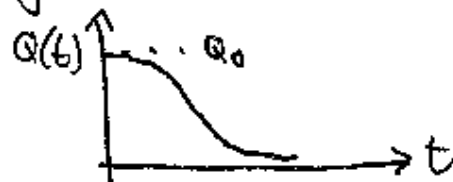

- [Recall 2 other solutions
- $\alpha^2 > \omega_0^2$ overdamped - slower return to baseline than above
 - $\alpha^2 < \omega_0^2$ underdamped - oscillatory solution within exponential fall-off]

Maximum current $L = 10 \text{ mH}$ $R = 200 \Omega$

$$I = \dot{Q} = -\omega_0^2 Q_0 t e^{-\omega_0 t}$$

$$\dot{I} = -\omega_0^2 Q_0 e^{-\omega_0 t} + \omega_0^3 Q_0 t e^{-\omega_0 t}$$

$$= 0 \text{ when } t = \frac{1}{\omega_0}$$

$$\omega_0 = \alpha = \frac{R}{2L} = \frac{200}{2 \times 10 \times 10^{-3}} = 10^4 \text{ s}^{-1}$$

$\rightarrow I$ maximal at $t = 0.1 \text{ ms}$

LCR circuit

$$\frac{d^2 I}{dt^2} + \frac{R}{L} \frac{dI}{dt} + \frac{1}{LC} I = 0$$

$$\gamma = \frac{R}{2L}$$

$$\omega_0^2 = \frac{1}{LC}$$

$$I = k_1 e^{\lambda_1 t} + k_2 e^{\lambda_2 t} \quad \lambda = -\gamma \pm \sqrt{\gamma^2 - \omega_0^2}$$

overdamped solution

$$\gamma^2 > \omega_0^2 \quad I(t) = \frac{V_0}{2\sqrt{\left(\frac{R}{2}\right)^2 - \frac{1}{C}}} \left(e^{-(\gamma-\beta)t} - e^{-(\gamma+\beta)t} \right)$$

critically damped solution

$$\gamma^2 = \omega_0^2 \quad I(t) = \frac{V_0}{L} \cdot t \cdot e^{-\gamma t}$$

underdamped (oscillatory) solution

$$\gamma^2 < \omega_0^2 \quad I(t \geq 0) = \frac{V_0}{\sqrt{\frac{1}{C} - \left(\frac{R}{2}\right)^2}} e^{-\gamma t} \cdot \sin(\omega_R t)$$