

AC Circuit Theory


Amplitude

Phase


$$V = V_0 \sin(\omega t)$$

$$V = V_0 \cos(\omega t)$$

$$V = V_0 \sin(\omega t + \phi)$$

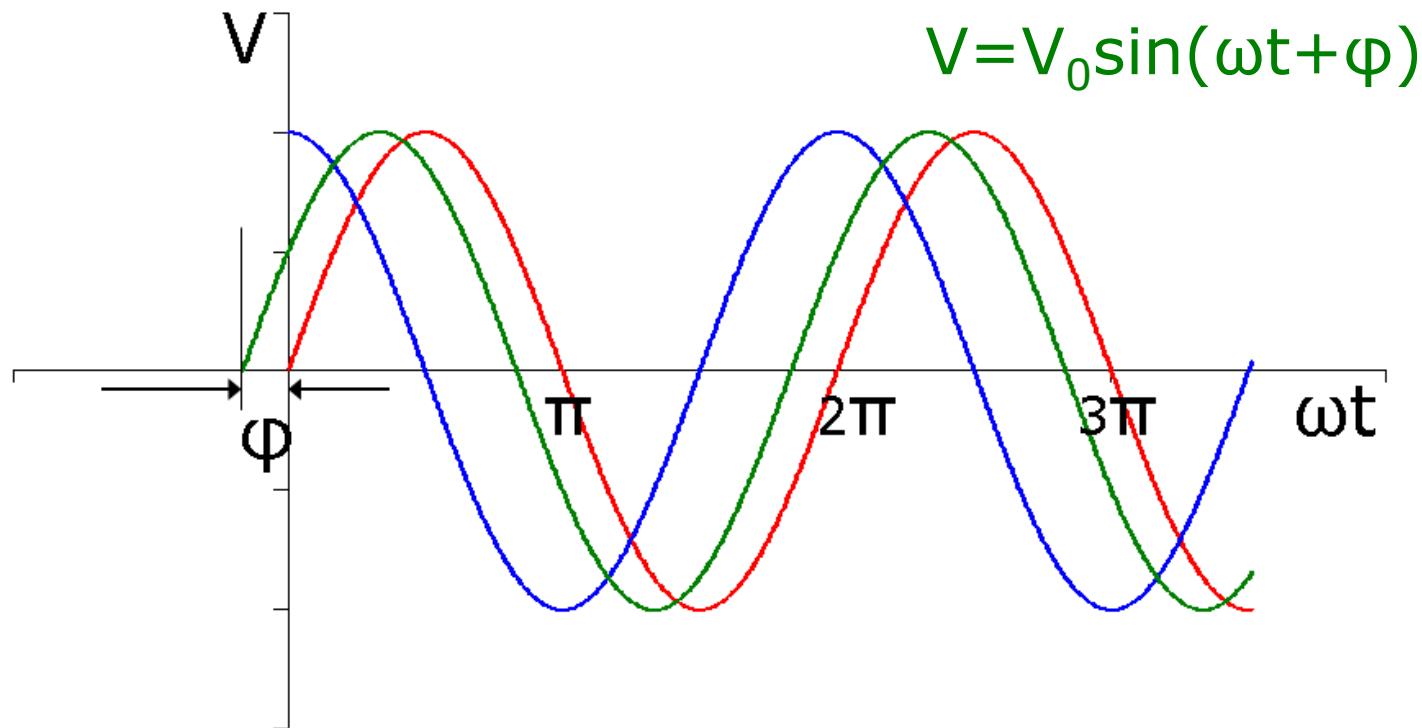


Apply AC current to a resistor...

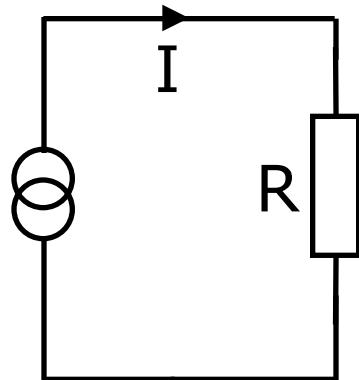

$$I = I_0 \sin(\omega t)$$

$$V_R = IR = I_0 R \sin(\omega t)$$

...capacitor...

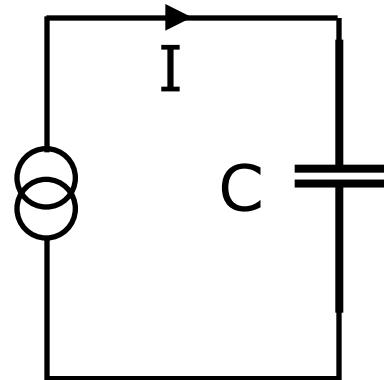


$$V_C = \frac{Q}{C} = \frac{1}{C} \int I_0 \sin(\omega t) dt$$

$$= -\frac{1}{\omega C} I_0 \cos(\omega t)$$

$$= \frac{1}{\omega C} I_0 \sin\left(\omega t - \frac{\pi}{2}\right)$$

...and inductor

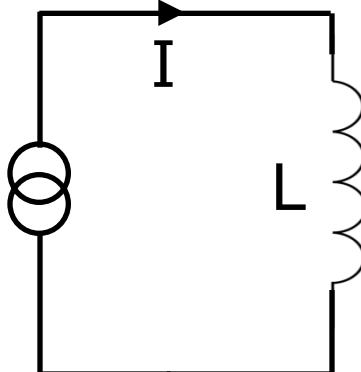

$$V_L = L \frac{dI}{dt} = \omega L I_0 \cos(\omega t) = \omega L I_0 \sin\left(\omega t + \frac{\pi}{2}\right)$$


Voltage leads current by $\frac{\pi}{2}$

Voltage lags current by $\pi/2$

Adding voltages


$V(t)?$

Kirchoff's Voltage Law
and
Ohm's law

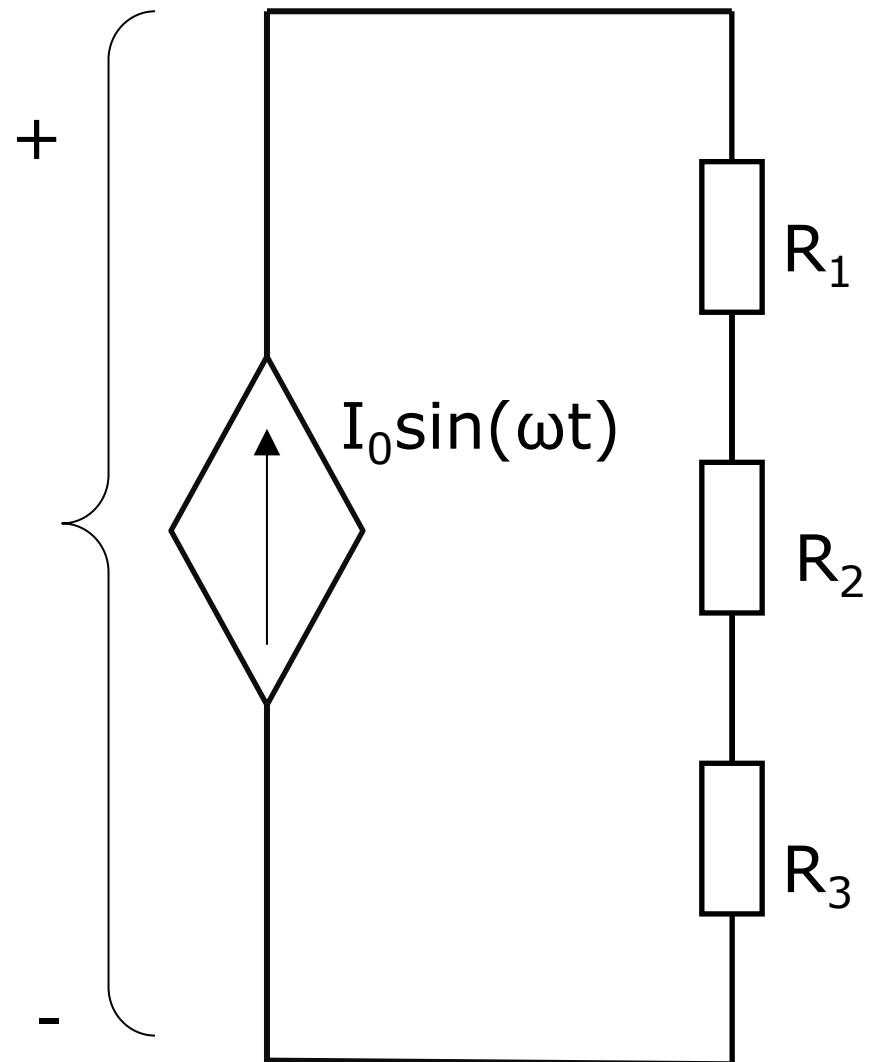


$$\begin{aligned}V &= I_0 R_1 \sin(\omega t) + I_0 R_2 \sin(\omega t) + I_0 R_3 \sin(\omega t) \\&= I_0 (R_1 + R_2 + R_3) \sin(\omega t)\end{aligned}$$

Adding voltages

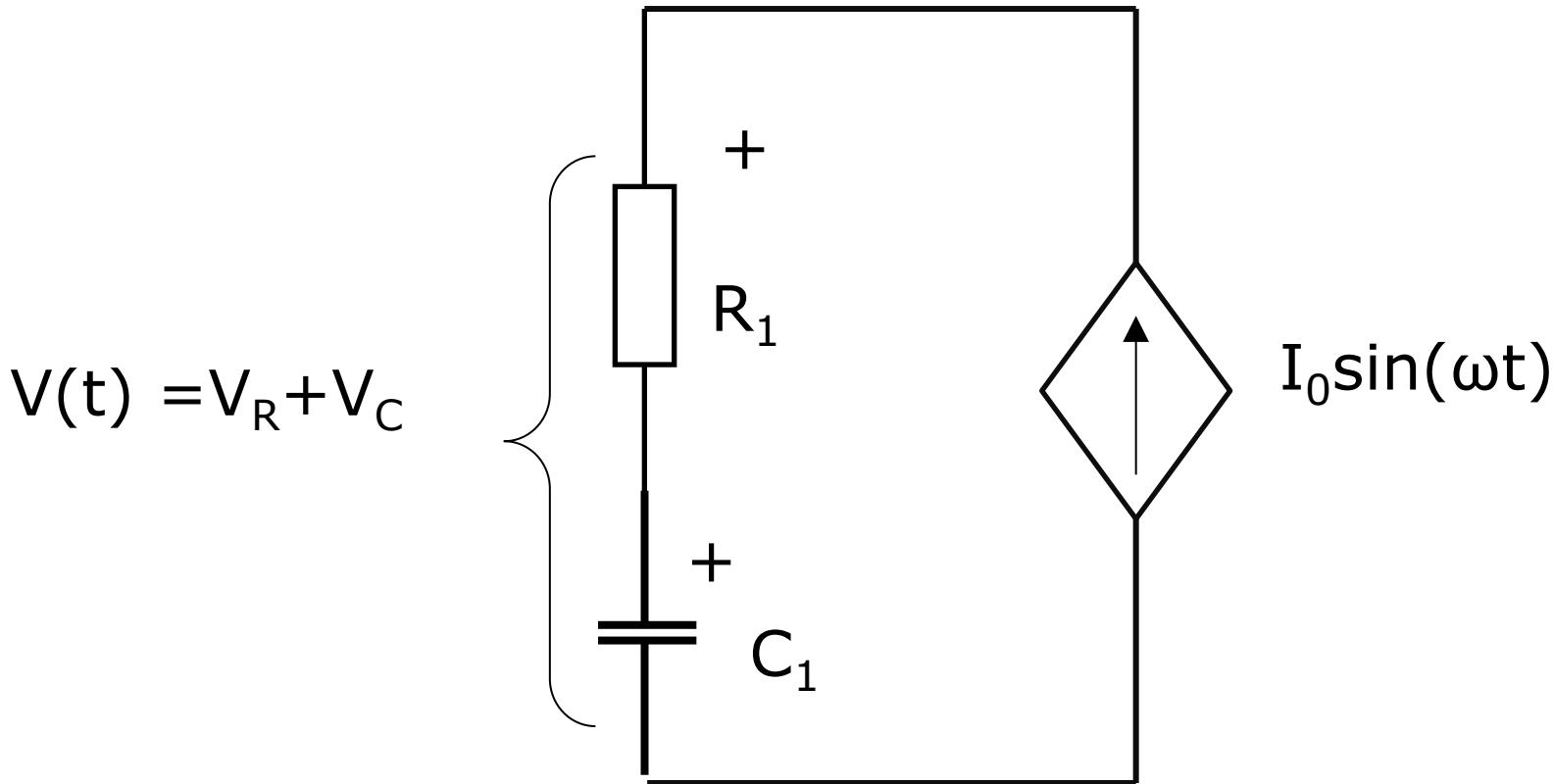

$$V = I_0 R_1 \sin(\omega t) - \frac{I_0}{\omega C} \cos(\omega t) \quad \text{voltages out of phase... } 4$$

Complex numbers in AC circuit theory

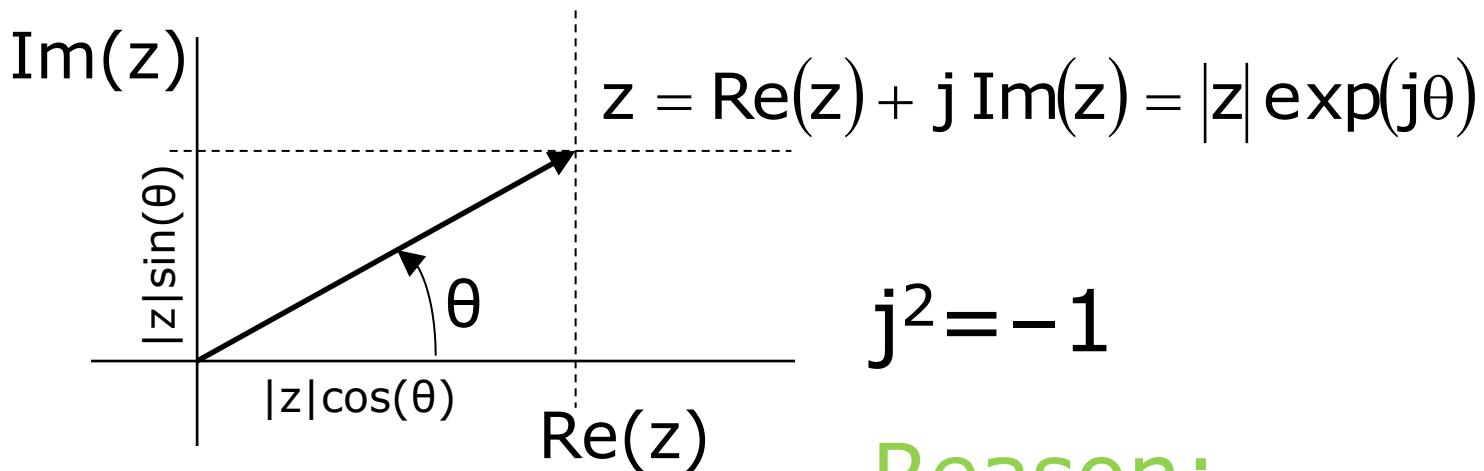

$$V(t) = V_0 \cos(\omega t) = \mathcal{R}e(V_0 e^{j\omega t})$$

$$V(t) = V_0 \sin(\omega t) = \mathcal{I}m(V_0 e^{j\omega t})$$

'i' is already taken

Complex Impedance

The ratio of the voltage across a component to the current through it when both are expressed in complex notation

$$I = I_0 \sin(\omega t) \rightarrow I = I_0 e^{j\omega t}$$

$$V_R = IR = I_0 R e^{j\omega t} \longrightarrow Z_R = R$$

$$V_C = \frac{1}{C} \int I dt = \frac{I_0}{j\omega C} e^{j\omega t} \longrightarrow Z_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$

$$V_L = L \frac{dI}{dt} = j\omega I_0 L e^{j\omega t} \longrightarrow Z_L = j\omega L$$

Complex Impedance


Real part: resistance (R)

Imaginary part: reactance $\left(\omega L - \frac{1}{\omega C} \right)$


Ohm's law $V = Z \cdot I$

$|V| = |Z| \cdot |I|$

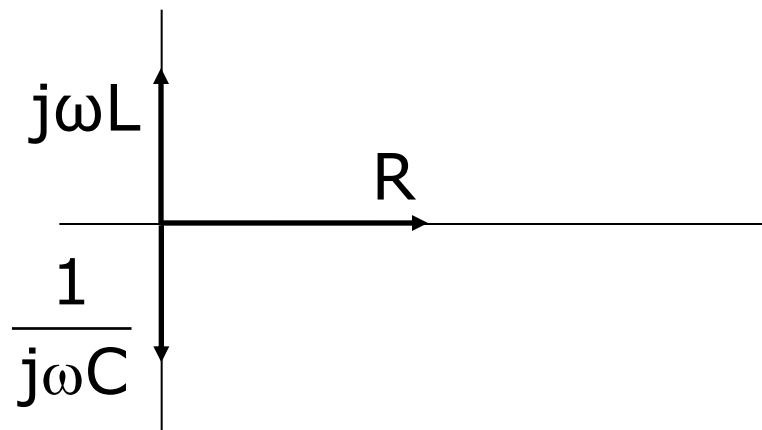
$\text{phase}(V) = \text{phase}(Z) + \text{phase}(I)$



Series / parallel impedances

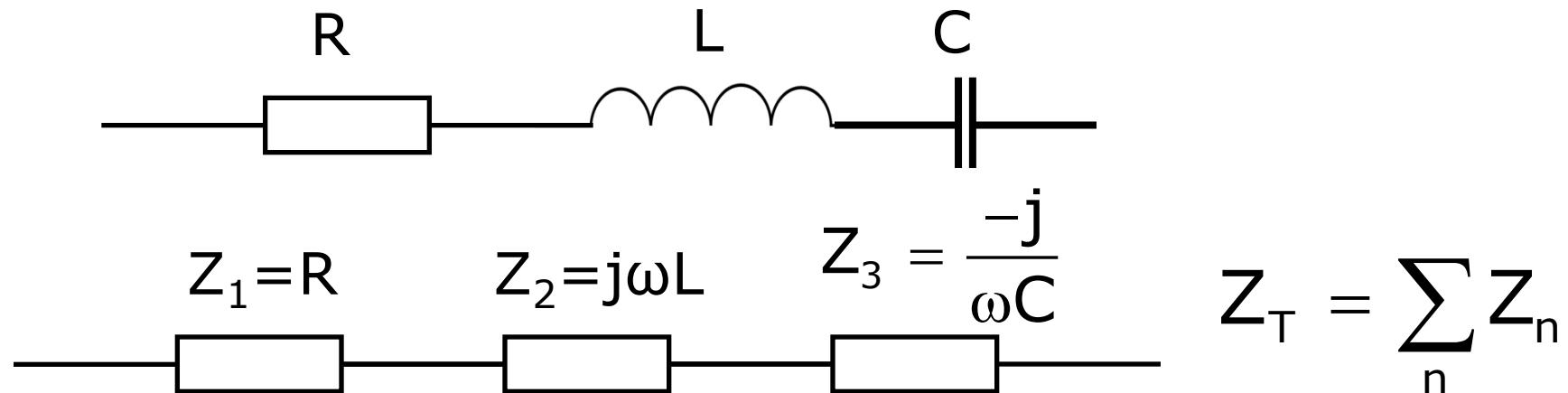

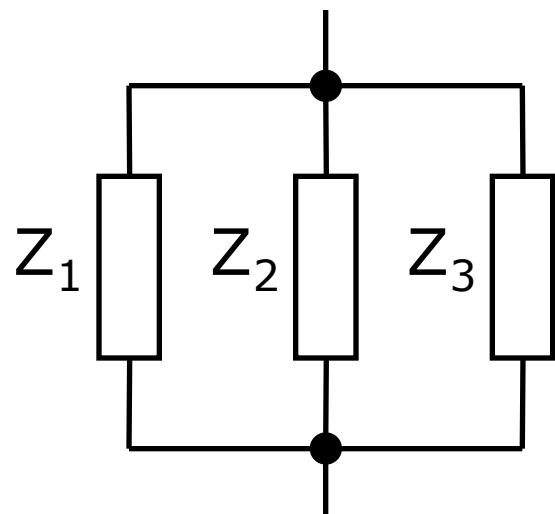Impedances in series: $Z_{\text{Total}} = Z_1 + Z_2 + Z_3 \dots$




Impedances in parallel

$$\frac{1}{Z_T} = \sum_n \frac{1}{Z_n}$$

$$= \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \dots$$


RC low pass filter

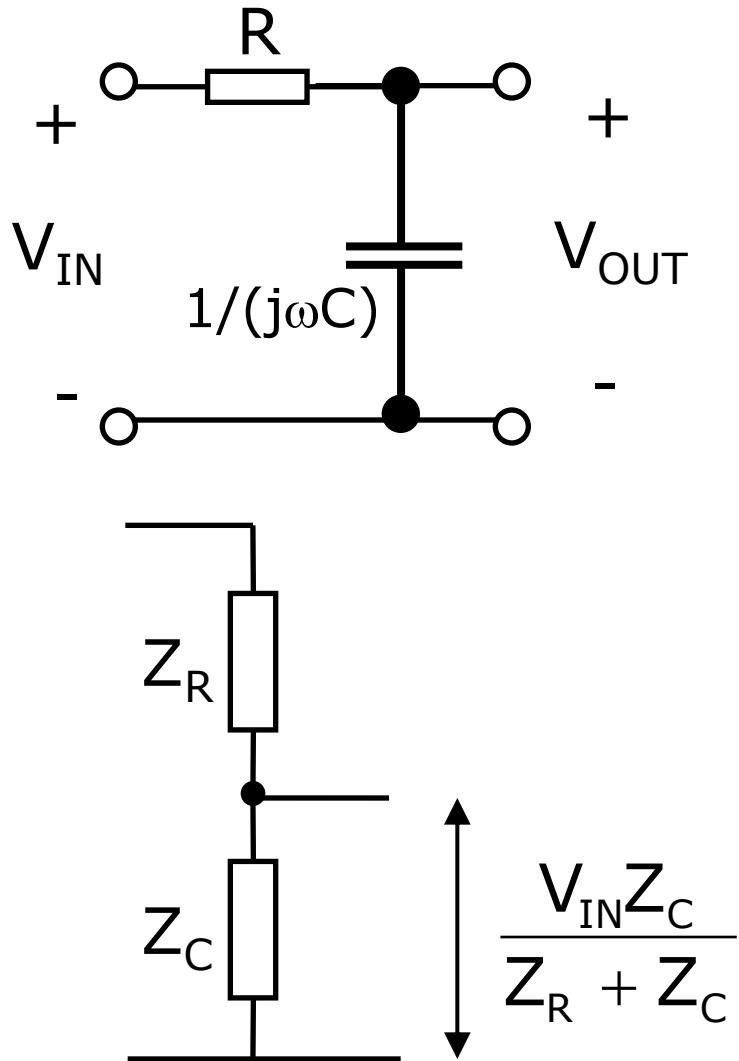

$$\begin{aligned}
 V_{OUT} &= \frac{V_{IN}Z_C}{Z_R + Z_C} = V_{IN} \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \\
 &= V_{IN} \frac{1}{1 + j\omega RC} \\
 &= V_{IN} \frac{1}{1 + j\omega RC} \frac{(1 - j\omega RC)}{(1 - j\omega RC)} \\
 &= V_{IN} \frac{1 - j\omega RC}{1 + (\omega RC)^2} \\
 &= V_{IN} \frac{1}{\sqrt{1 + (\omega RC)^2}} e^{j\varphi}
 \end{aligned}$$

$$\varphi = \tan^{-1}(-\omega RC)$$

RL high pass filter

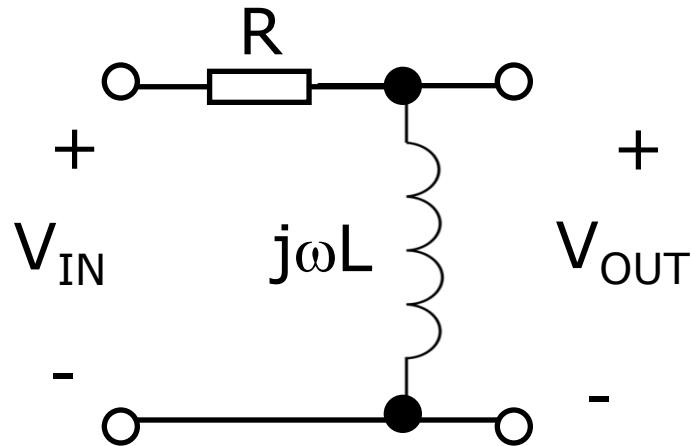

$$V_{OUT} = V_{IN} \frac{j\omega L}{R + j\omega L}$$


Here is a slight trick:
Get comfortable with
the **complex result**.

$$V_{OUT} = V_{IN} \frac{\omega \frac{L}{R}}{\sqrt{1 + (\omega \frac{L}{R})^2}} e^{j\varphi}$$

$$\varphi = \tan^{-1} \left(\frac{R_{10}}{\omega L} \right)$$

Bode plot
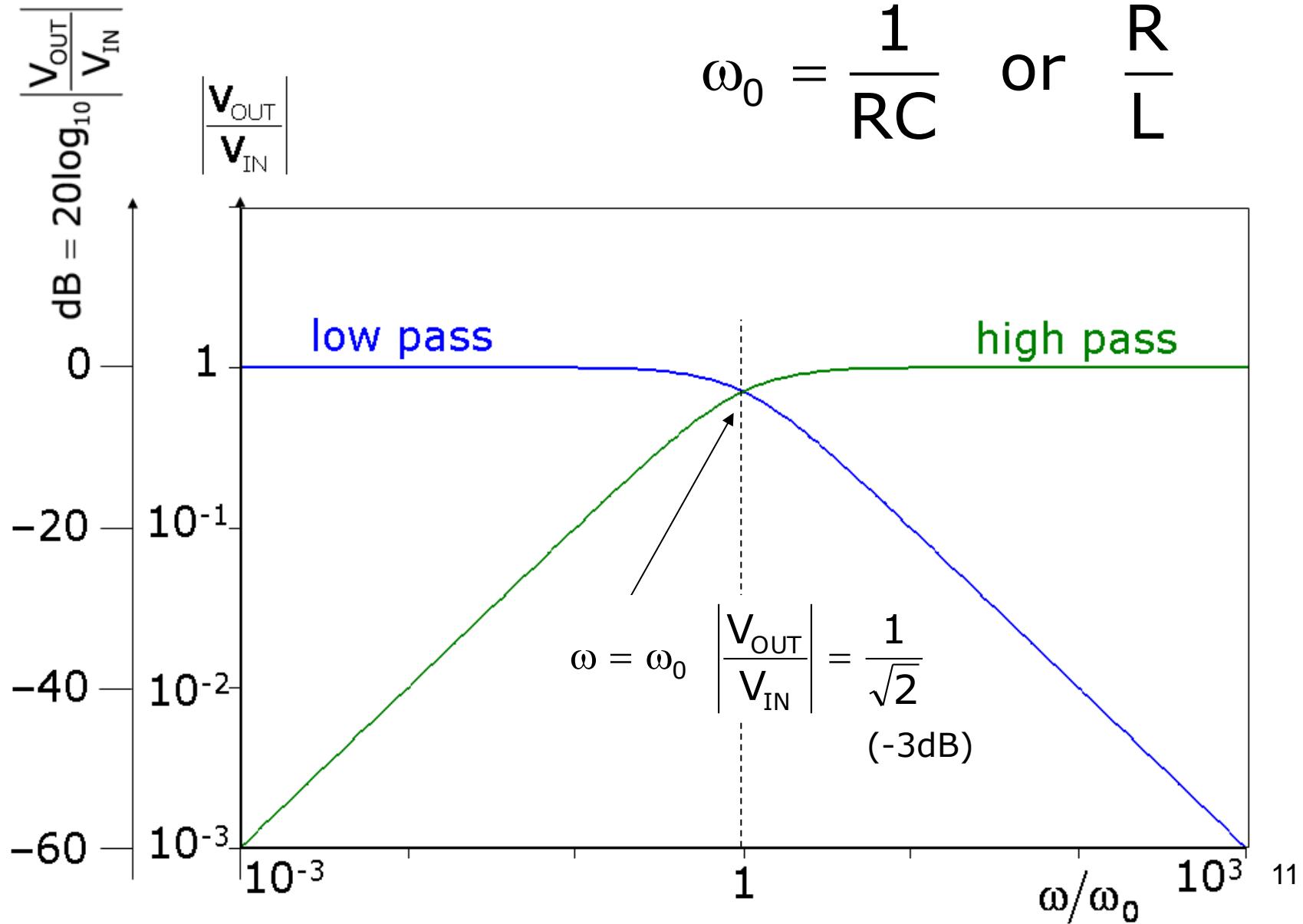
$$\omega_0 = \frac{1}{RC} \quad \text{or} \quad \frac{R}{L}$$




Decibels

Logarithm of power ratio

$$dB = 10 \log_{10} \left| \frac{V_{OUT}^2}{V_{IN}^2} \right| = 20 \log \left| \frac{V_{OUT}}{V_{IN}} \right|$$

V_{OUT}/V_{IN}	dB
10	20
1	0
0.1	-20
0.01	-40
0.001	-60

Bode plot

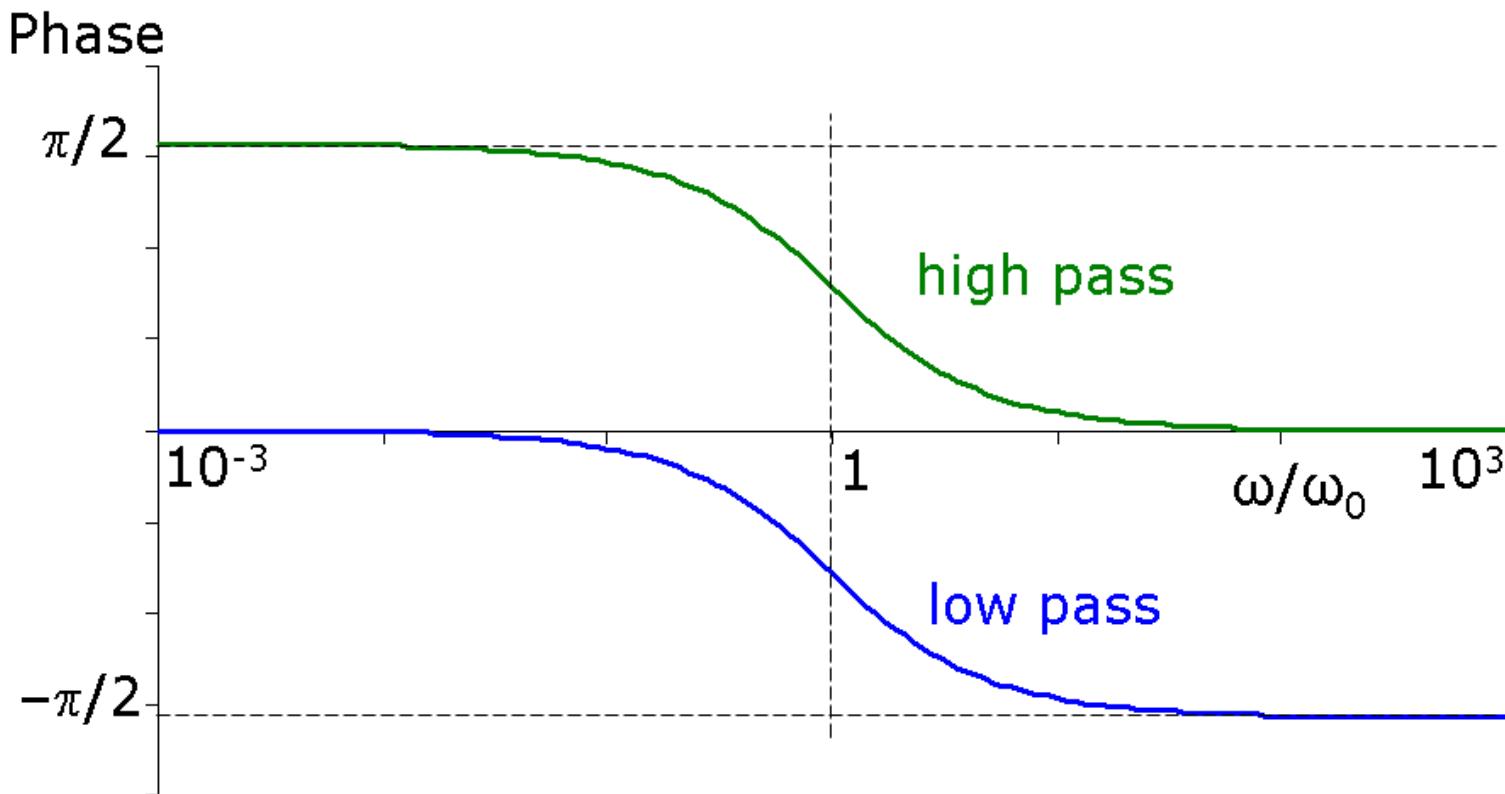

Something Interesting


- **Capacitor**
 - At low frequencies (like DC) → **Open circuit**
 - Not a surprise, it's got a gap!
 - At high frequencies (“fast”) → **Short circuit!**
- **Inductor**
 - At low frequencies → **Short circuit**
 - Not a surprise, it's just a wire really
 - At high frequencies → **Open circuit!**
- **Sometimes this can help you with your intuition on the circuit's behaviour.**



Go to black Board and

EXPLAIN PHASORS

LRC series circuit

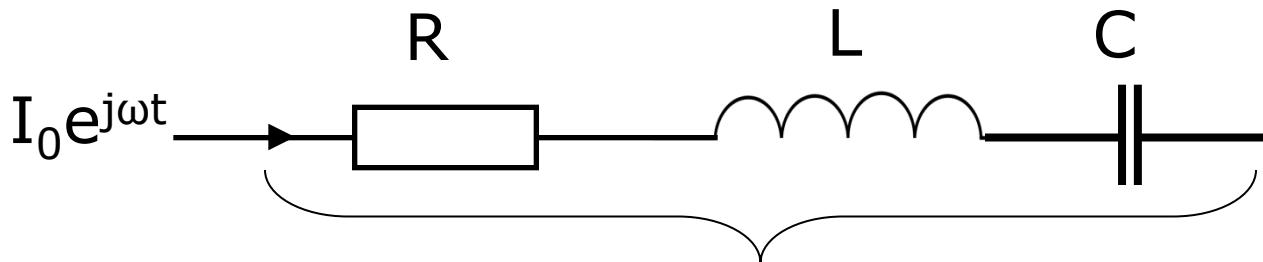

$$\begin{aligned}V &= V_R + V_L + V_C \\&= (Z_R + Z_L + Z_C)I \\&= \left(R + j\left(\omega L - \frac{1}{\omega C} \right) \right) I\end{aligned}$$


$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}$$

$$\varphi = \tan^{-1} \left(\frac{\omega L - \frac{1}{\omega C}}{R} \right)$$

Purely resistive at $\omega_R = \frac{1}{\sqrt{LC}}$ $\varphi=0$ $Z=R$

$$V = I_0 \cdot \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2} \cdot e^{j \left(\omega t + \tan^{-1} \left(\frac{\omega L - \frac{1}{\omega C}}{R} \right) \right)}$$

LRC parallel circuit

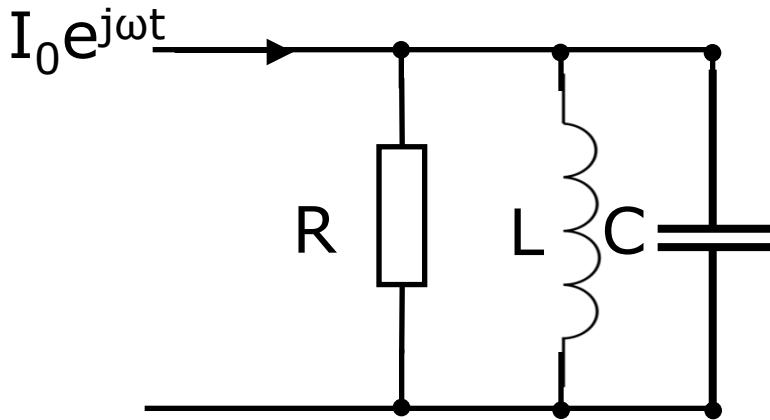

$$I = I_R + I_L + I_C = \frac{V}{Z}$$

$$\frac{1}{Z} = \frac{1}{R} + j \left(\omega C - \frac{1}{\omega L} \right)$$


$$Z = \frac{1}{\frac{1}{R} + j \left(\omega C - \frac{1}{\omega L} \right)} = \frac{\frac{1}{R} + j \left(\frac{1}{\omega L} - \omega C \right)}{\left(\frac{1}{R} \right)^2 + \left(\frac{1}{\omega L} - \omega C \right)^2}$$

Purely resistive at $\omega_R = \frac{1}{\sqrt{LC}}$ $\varphi=0$ $Z=R$

$$|Z| = \sqrt{\left(\frac{1}{R} \right)^2 + \left(\frac{1}{\omega L} - \omega C \right)^2}$$

$$\varphi = \tan^{-1} \left(R \left(\frac{1}{\omega L} - \omega C \right) \right)$$

Bandpass filter

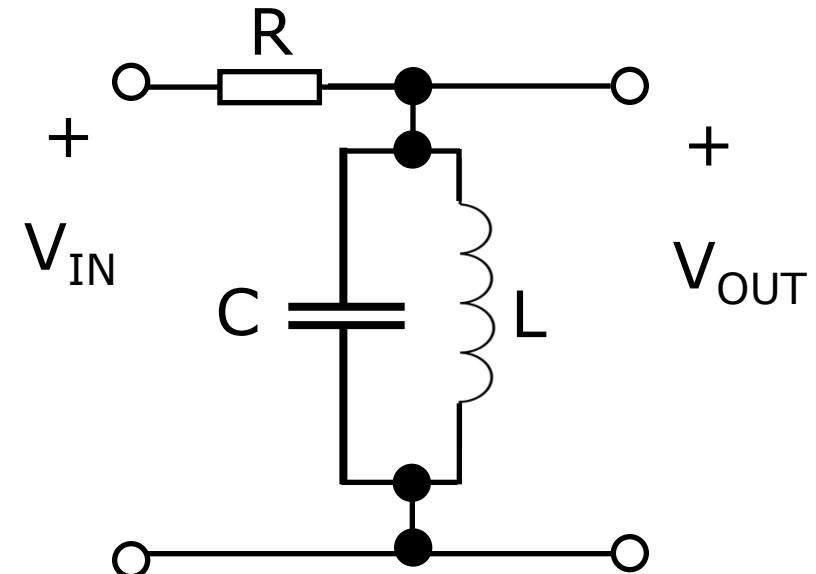

$$\left| \frac{V_{OUT}}{V_{IN}} \right| = \frac{1}{\sqrt{1 + R^2 \left(\frac{1}{\omega L} - \omega C \right)^2}}$$

ON BLACK BOARD TOO!

$$V_{OUT} = \frac{Z_{LC}}{R + Z_{LC}} V_{IN}$$

$$\frac{1}{Z_{LC}} = \frac{1}{j\omega L} + j\omega C$$

$$Z_{LC} = j \frac{1}{\left(\frac{1}{\omega L} - \omega C \right)}$$

$$V_{OUT} = \frac{j\omega L}{j\omega L + R(1 - \omega^2 LC)} V_{IN}$$

$$\omega \rightarrow \infty \quad \left| \frac{V_{OUT}}{V_{IN}} \right| \rightarrow 0 \quad \omega \rightarrow 0 \quad \left| \frac{V_{OUT}}{V_{IN}} \right| \rightarrow 0$$

$$\omega = \omega_0 = \frac{1}{\sqrt{LC}} \quad \left| \frac{V_{OUT}}{V_{IN}} \right| = 1$$

Bandpass filter

build a radio filter

$$\left| \frac{V_{\text{OUT}}}{V_{\text{IN}}} \right| = \frac{1}{\sqrt{1 + R^2 \left(\frac{1}{\omega L} - \omega C \right)^2}}$$

$$f_0 = 455 \text{ kHz}$$

$$\Delta f = 20 \text{ kHz}$$


$$\omega_0 = 2\pi f_0 = \frac{1}{\sqrt{LC}}$$

$$C = 10 \text{ nF}$$

$$L = 12.2 \mu\text{H}$$

$$\Delta\omega = 2\pi\Delta f$$

$$\omega = \omega_0 \pm \Delta\omega$$

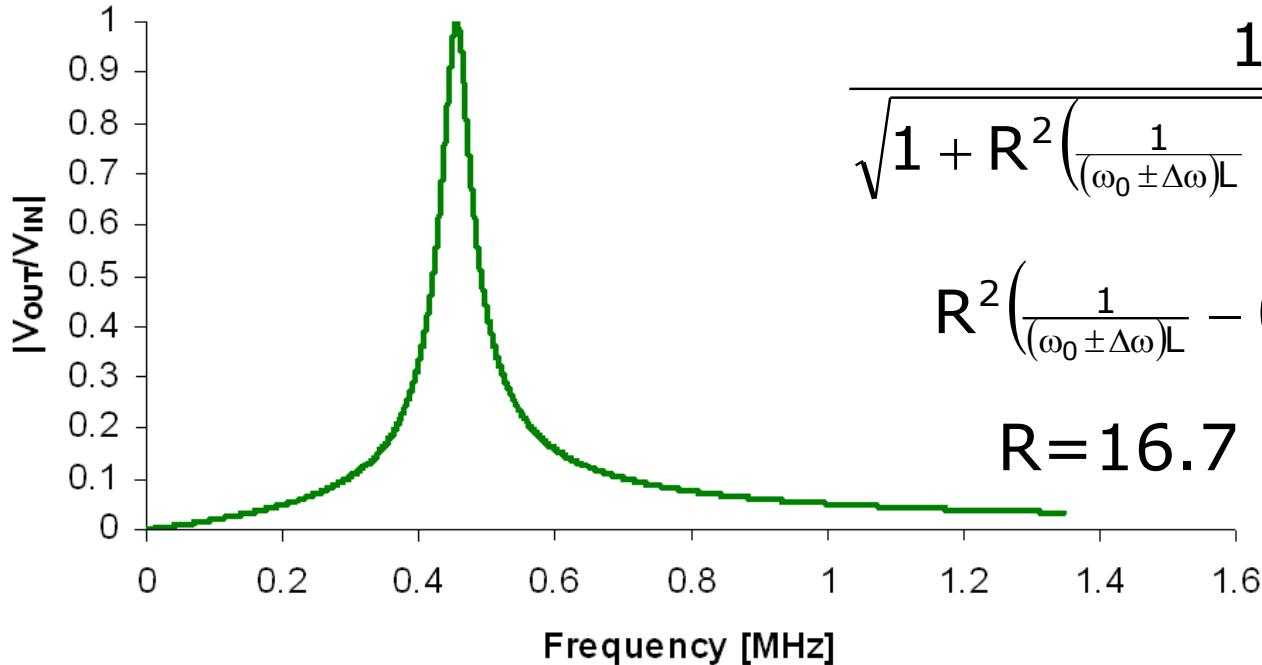


$$\frac{1}{\sqrt{1 + R^2 \left(\frac{1}{(\omega_0 \pm \Delta\omega)L} - (\omega_0 \pm \Delta\omega)C \right)^2}} = \frac{1}{\sqrt{2}}$$

$$R^2 \left(\frac{1}{(\omega_0 \pm \Delta\omega)L} - (\omega_0 \pm \Delta\omega)C \right)^2 = 1$$

$$R = 16.7 \text{ k}\Omega$$

LCR series circuit – current driven

$$I(t) = I_0 e^{j\omega t}$$

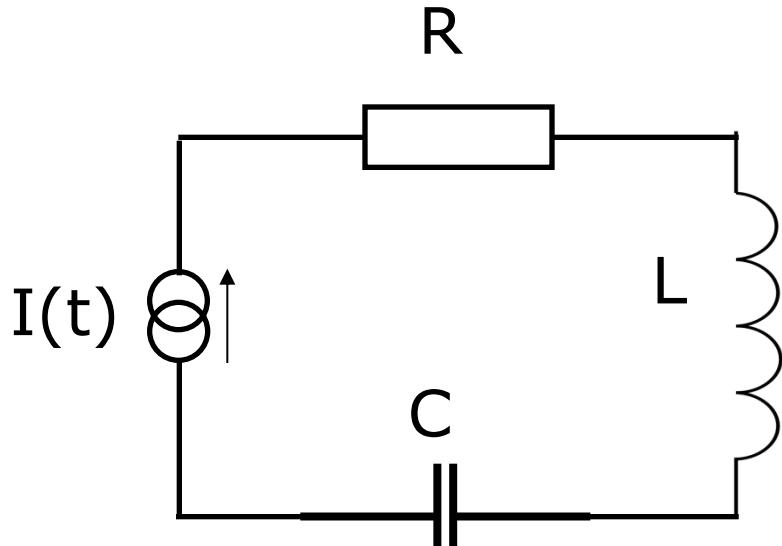

$$Z = R + j\omega L + \frac{1}{j\omega C}$$

$$Z = R + j \left[\omega L - \frac{1}{\omega C} \right]$$


$$V = IZ = I_0 \cdot |Z| \cdot e^{j\varphi} \cdot e^{j\omega t}$$

**Low Freq. → Wild Stuff!
NOT a Very Good Idea**

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}$$

$$\varphi = \tan^{-1} \left(\frac{\text{Im}}{\text{Re}} \right) = \tan^{-1} \left(\frac{\omega L - \frac{1}{\omega C}}{R} \right)$$

LCR series circuit – voltage driven

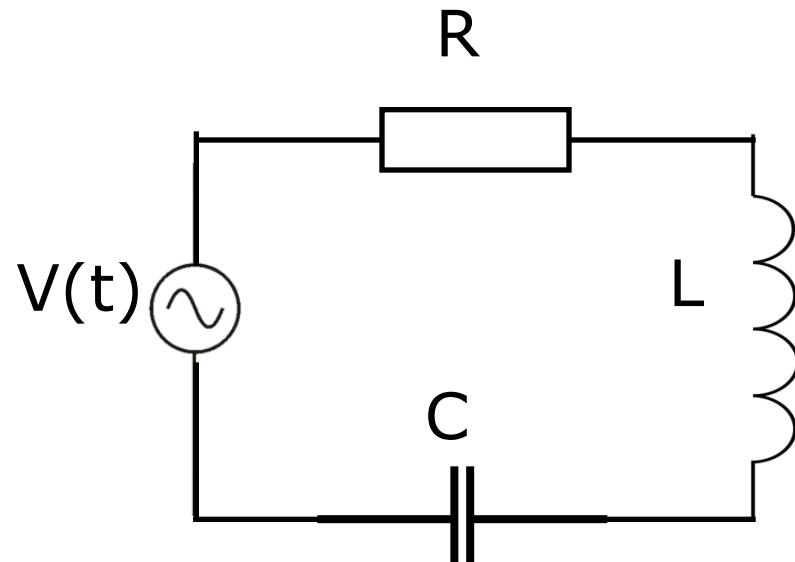

$$V(t) = V_0 e^{j\omega t}$$

$$I = \frac{V}{Z} = \frac{V_0}{|Z|} e^{-j\varphi}$$

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$


$$\varphi = \tan^{-1}\left(\frac{\omega L - \frac{1}{\omega C}}{R}\right)$$


$$|I| = \frac{V_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

$$\omega \rightarrow \infty \quad |I| \rightarrow 0$$

$$\omega \rightarrow 0 \quad |I| \rightarrow 0$$

$$\omega \rightarrow \omega_0 \quad |I| = \frac{V_0}{R} \quad \text{maximum}$$

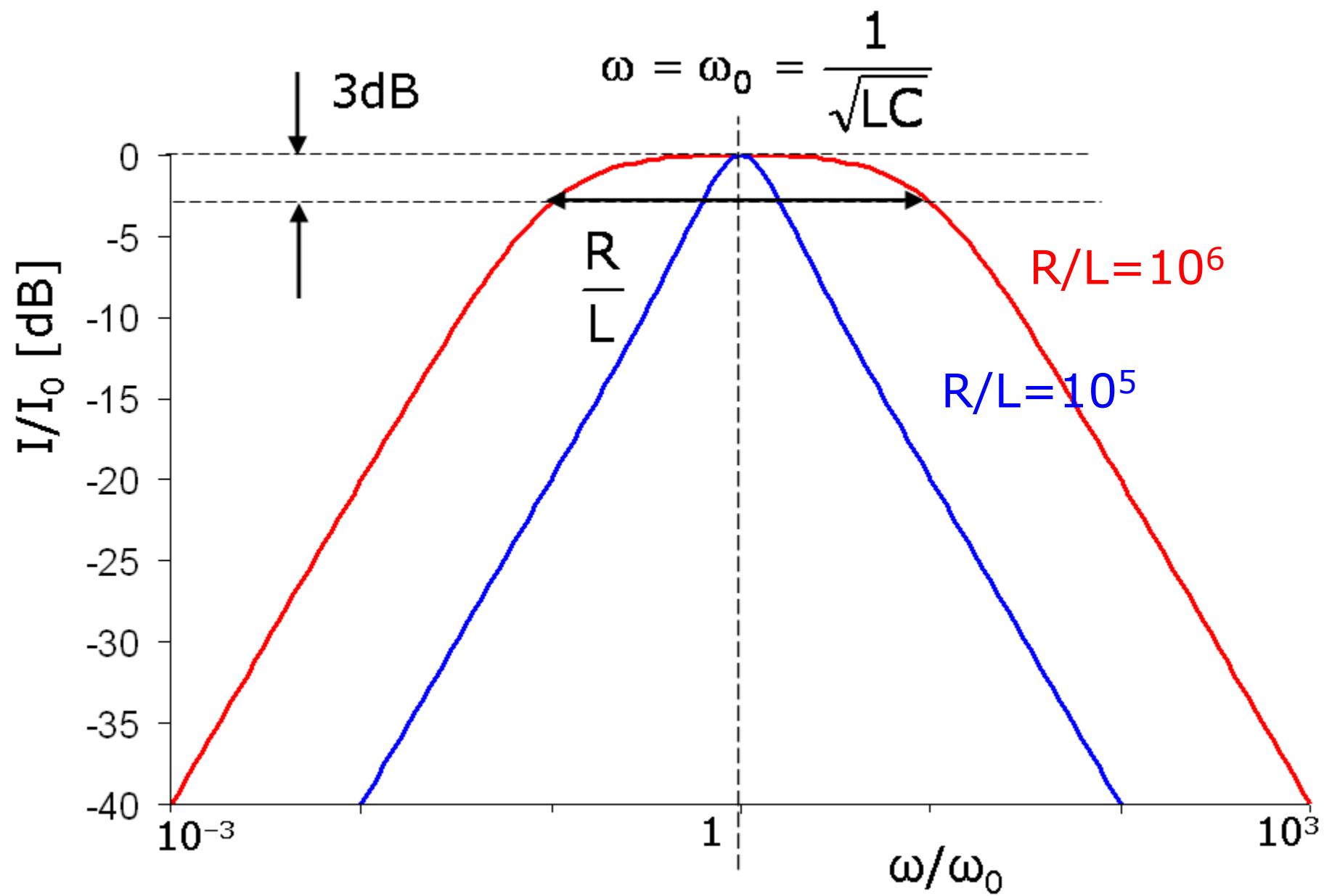

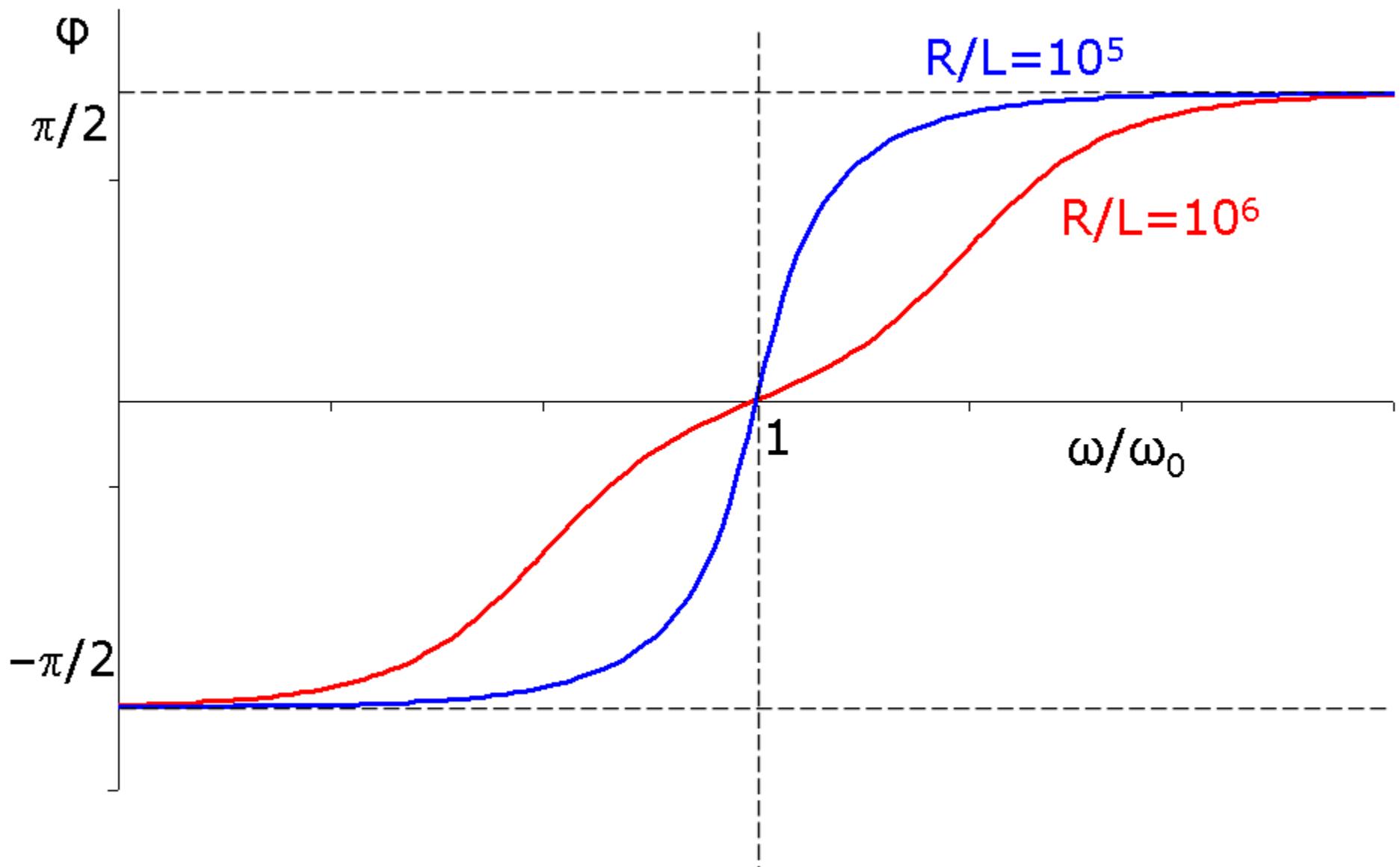

Q value

No longer on CP2 syllabus
(moved to CP3)

$$Q = 2\pi \frac{\text{peak energy stored}}{\text{energy dissipated per cycle}}$$

NOT ALWAYS HELPFUL


$$Q = \frac{\omega_0}{\Delta\omega_{FWHM}} = \frac{\text{Frequency at resonance}}{\text{Diff. in Freq. to FWHM}}$$

Power
not voltage

High Q value – narrow resonance

Q value


For what we did last time.

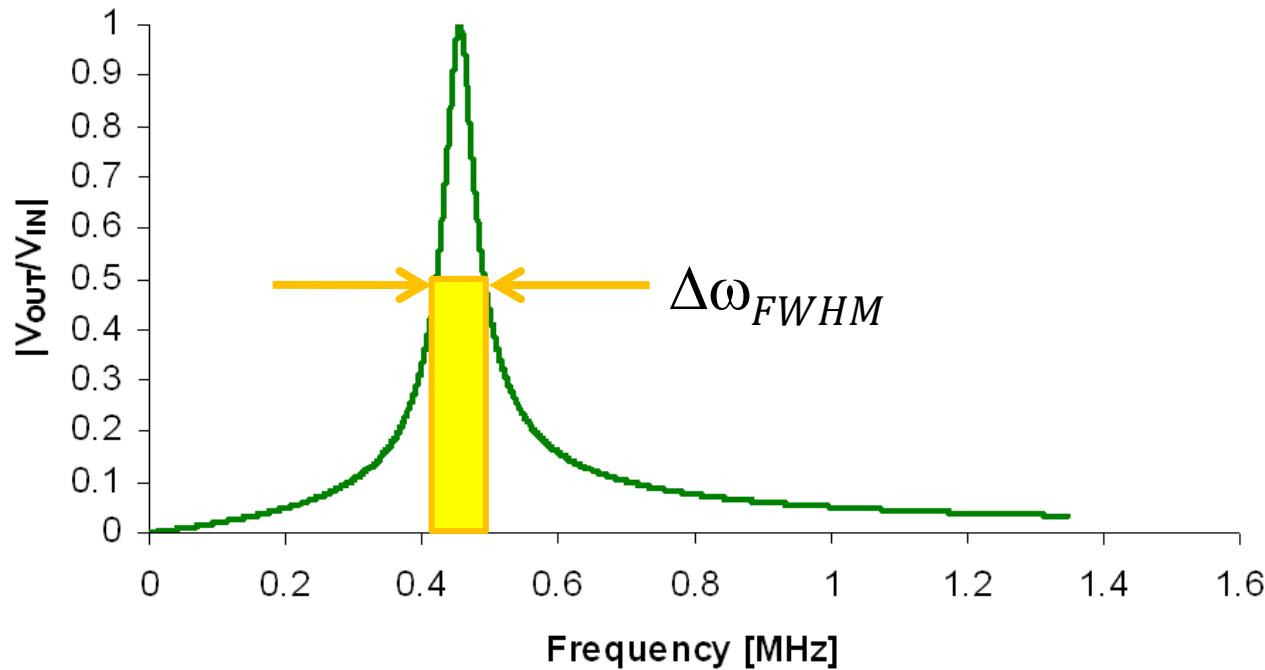

$$Q = \frac{\omega_0}{\Delta\omega_{FWHM}} = \frac{\omega_0}{2\Delta\omega} = \frac{1}{2} \cdot 2R \sqrt{\frac{C}{L}} = R \sqrt{\frac{C}{L}}$$

High Q value – narrow resonance

LC circuit – power dissipation

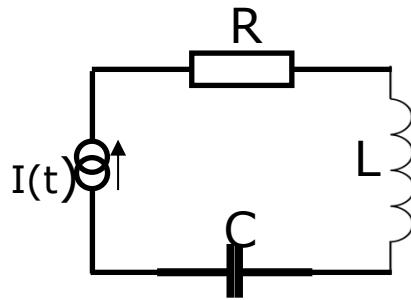

Power is only dissipated in the resistor

$$\langle P \rangle = \frac{1}{T} \int_0^T I(t)V(t)dt$$

$$T = \frac{2\pi}{\omega}$$

proof – power
dissipated
inductor and
capacitor –
none

$$I(t) = I_0 \sin(\omega t)$$

$$V_C = -\frac{1}{\omega C} I_0 \cos(\omega t)$$

$$V_L = \omega L I_0 \cos(\omega t)$$


$$V_X = X I_0 \cos(\omega t)$$

reactance

$$X = -\frac{1}{\omega C} \text{ or } \omega L$$

$$\langle P \rangle_{L,C} = \frac{1}{T} \int_0^T X I_0 \sin(\omega t) \cos(\omega t) dt = \left[\frac{1}{2\omega T} X I_0^2 \sin^2(\omega t) \right]_0^{T=2\pi/\omega} = 0$$

LRC Power dissipation
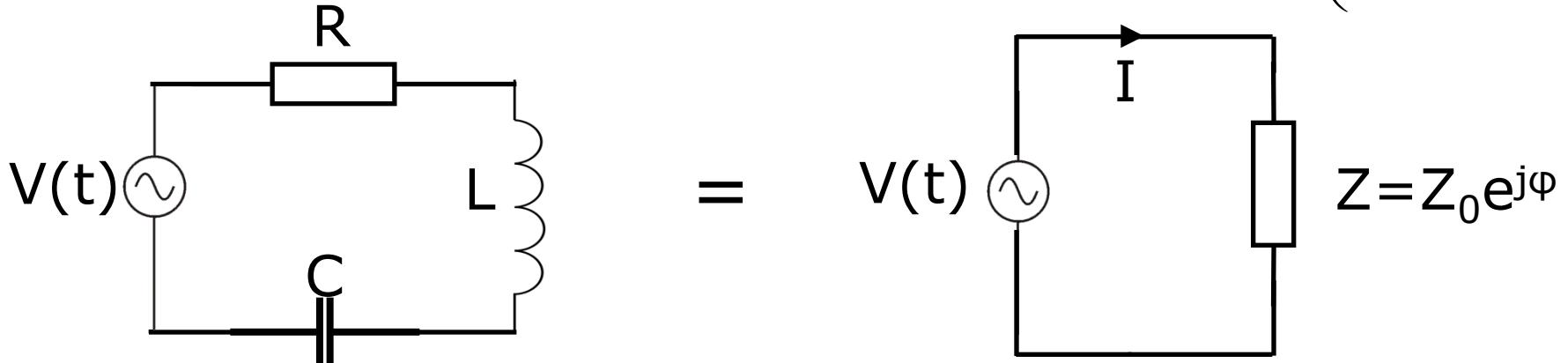
$$Z = R + j \left(\omega L - \frac{1}{\omega C} \right)$$


$$V(t) = V_0 \sin(\omega t)$$

$$I(t) = \frac{V_0}{Z_0} \sin(\omega t - \varphi)$$

$$P(t) = V(t)I(t) = \frac{V_0^2}{Z_0} \sin(\omega t) \sin(\omega t - \varphi)$$

$$Z_0 = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}$$

$$\tan \varphi = \frac{\left(\omega L - \frac{1}{\omega C} \right)}{R}$$

Instantaneous power

Power dissipation

$$P(t) = V(t)I(t) = \frac{V_0^2}{Z_0} \sin(\omega t) \sin(\omega t - \varphi)$$

$$= V_0 I_0 \sin(\omega t) [\sin(\omega t) \cos(\varphi) - \cos(\omega t) \sin(\varphi)]$$

$$\langle P \rangle = \frac{1}{T} \int_0^T V_0 I_0 [\sin^2(\omega t) \cos(\varphi) - \sin(\omega t) \cos(\omega t) \sin(\varphi)] dt$$

$$\langle P \rangle = \frac{V_0 I_0}{T} \int_0^T \frac{1}{2} (1 - \cos(2\omega t)) \cos(\varphi) dt = 0$$

$$= \frac{V_0 I_0}{T} \left[\frac{t}{2} \cos \varphi \right]_0^T$$

$$= \frac{V_0 I_0}{2} \cos \varphi = V_{\text{RMS}} I_{\text{RMS}} \cos \varphi$$

$\cos \varphi$ = power factor



On black board

But then go ahead and flip to next slide now anyway.

POWER IN COMPLEX CIRCUIT ANALYSIS

Power factor

$$\cos\varphi = \frac{\text{averagepower}}{\text{apparentpower}} = \frac{P}{V_{\text{RMS}} I_{\text{RMS}}}$$

Resistive load $Z=R$ $\cos\varphi=1$



Reactive load $Z=X$ $\cos\varphi=0$



**RECALL
THE PREVIOUS CIRCUIT:**


$R=1 \text{ k}\Omega$; $C=2.5 \mu\text{F}$; $L = 10 \text{ mH}$

Output Voltage Magnitude

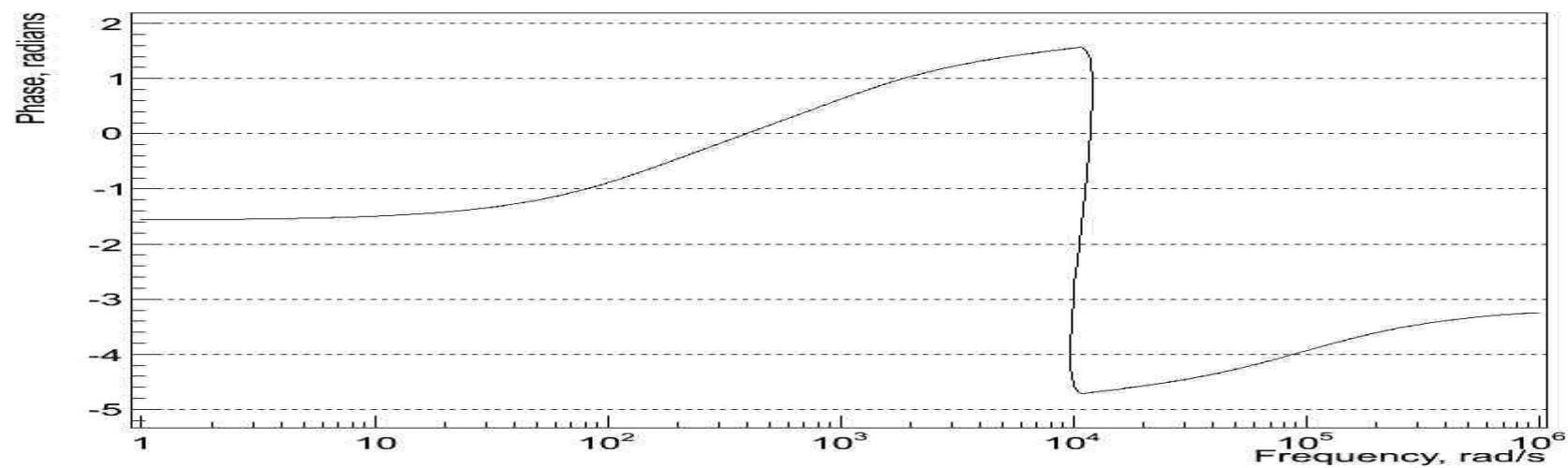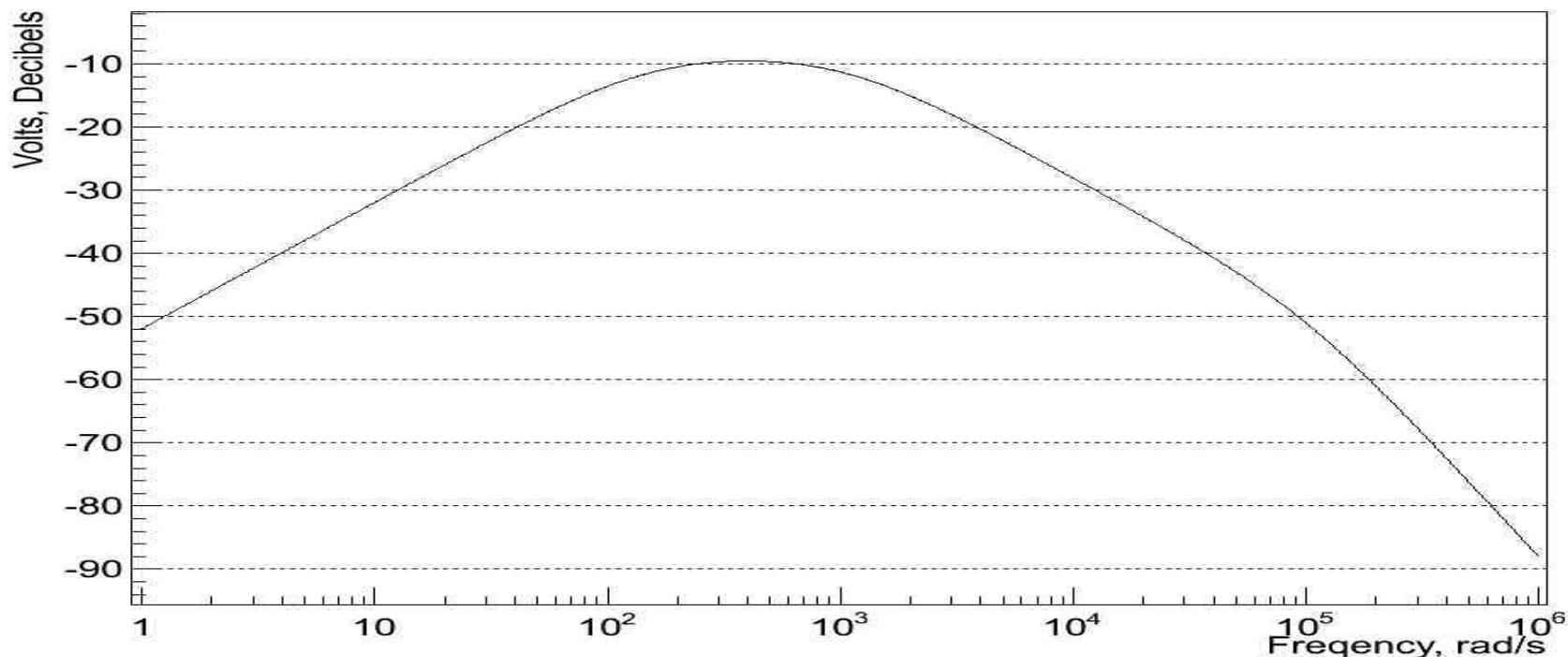

Bridge circuits

To determine an unknown impedance

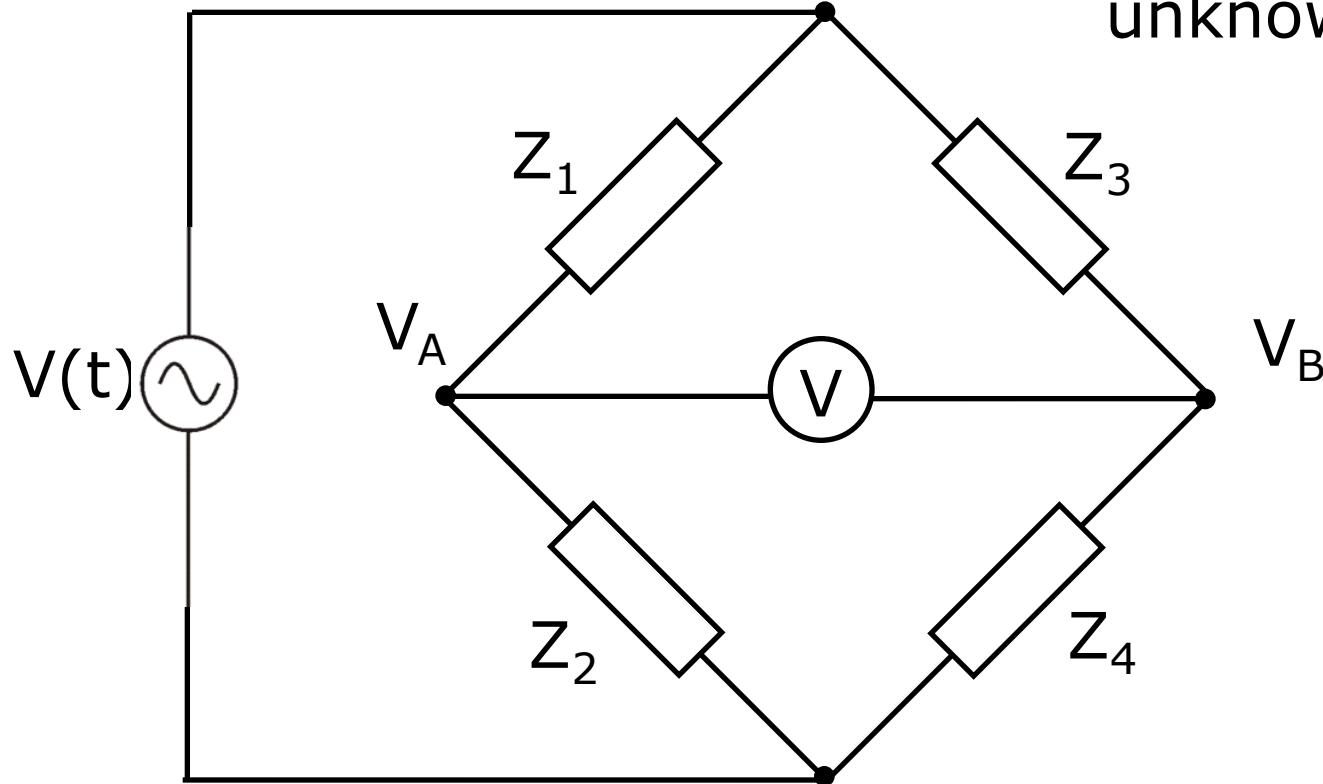

Bridge balanced when $V_A - V_B = 0$

$$\frac{Z_2}{Z_1 + Z_2} V(t) - \frac{Z_4}{Z_3 + Z_4} V(t) = 0$$

$$\frac{Z_2}{Z_1 + Z_2} = \frac{Z_4}{Z_3 + Z_4}$$

$$Z_2(Z_3 + Z_4) = Z_4(Z_1 + Z_2)$$


$$Z_2 Z_3 = Z_4 Z_1$$

Phasors and stuff

BACKUP SLIDES

CP2 September 2003

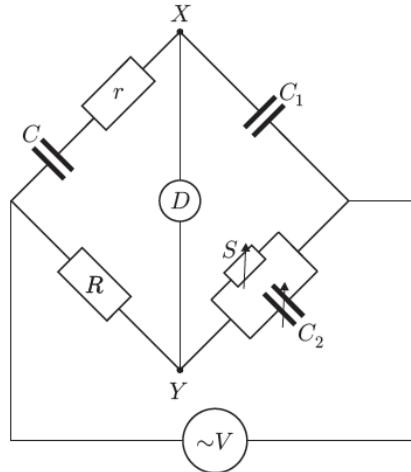9. (i) A Schering bridge is used to determine the capacitance C and resistance r of a lossy capacitor. In the diagram below the instrument D detects when X and Y are at the same potential, i.e. the bridge is balanced.



Show that the conditions for balancing the bridge are

$$C = C_1 S / R \quad \text{and} \quad r = C_2 R / C_1. \quad [10]$$

- (ii) A source of alternating voltage $V_0 \exp(j\omega t)$ with internal complex impedance $Z_1 = R_1 + jX_1$ is connected to a load of complex impedance $Z_2 = R_2 + jX_2$.

Show that the current through the load is given by

$$I = I_0 \exp[j(\omega t - \phi)],$$

where


$$I_0 = V_0 \left[(R_1 + R_2)^2 + (X_1 + X_2)^2 \right]^{-1/2},$$

and find an expression for ϕ . [4]

Hence show that the mean power $\langle P \rangle$ consumed by the load over one cycle is

$$\langle P \rangle = \frac{1}{2} I_0^2 R_2. \quad [6]$$

i) Bridge relations

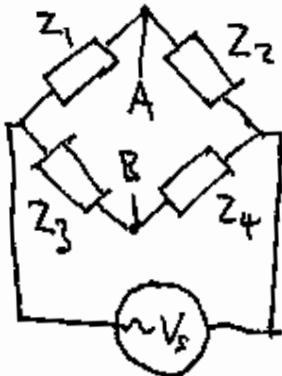

balanced when $V_A = V_B$


$$V_A = \frac{z_1}{z_1 + z_2} V_s$$

$$V_B = \frac{z_3}{z_3 + z_4} V_s$$

$$z_1(z_3 + z_4) = z_3(z_1 + z_2)$$

$$z_1 z_4 = z_3 z_2$$

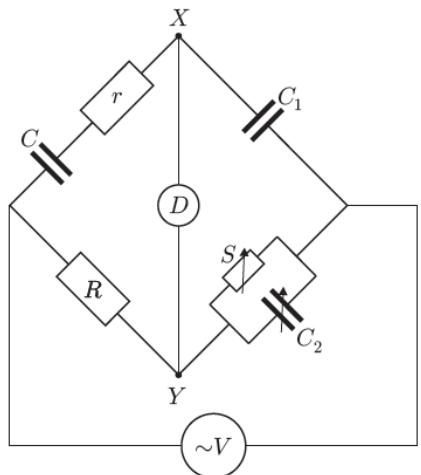Must be satisfied for both real and imaginary parts



$$Z_1 = Z_C + Z_r \\ = \frac{-j}{\omega C} + r$$

$$Z_3 = R$$

$$Z_2 = \frac{-j}{\omega C_1}$$

$$\begin{aligned} \frac{1}{Z_4} &= \frac{1}{Z_S} + \frac{1}{Z_{C_2}} \\ &= \frac{1}{S} + j\omega C_2 \\ &= \frac{1 + j\omega S C_2}{S} \end{aligned}$$

$$\frac{Z_1}{Z_2} = \frac{Z_3}{Z_4}$$


$$(r - \frac{j}{\omega C})j\omega C_1 = \frac{R}{S}(1 + j\omega S C_2)$$

$$j\omega C_1 r + \frac{C_1}{C} = \frac{R}{S} + j\omega R C_2$$

equate real and imaginary parts

$$C = \frac{C_1 S}{R} \quad r = \frac{C_2 R}{S}$$

ii)

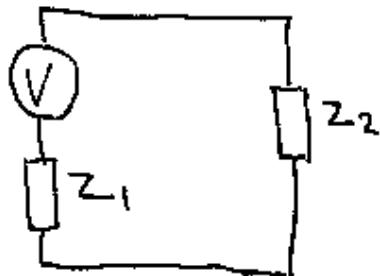

$$Z_1 = R_1 + jX_1$$

$$Z_2 = R_2 + jX_2$$

$$V = V_0 e^{j\omega t}$$

$$V = (Z_1 + Z_2) I$$

$$= [(R_1 + R_2) + j(X_1 + X_2)] I$$

$$I = V_0 \left[(R_1 + R_2)^2 + (X_1 + X_2)^2 \right]^{-\frac{1}{2}} e^{j(\omega t - \phi)}$$

$$\tan \phi = \frac{X_1 + X_2}{R_1 + R_2}$$

Power dissipated in load $P = I^2 R_2$


only resistive part of impedance contributes

$$P = I_0^2 R_2 \cos^2(\omega t - \phi)$$

\cos^2 or \sin^2 averaged over 1 cycle = $\frac{1}{2}$


$$\langle P \rangle = \frac{1}{2} I_0^2 R$$

Phasors

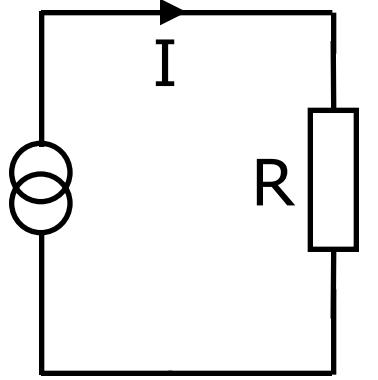

$$I = I_0 \sin(\omega t)$$


$$V_R = IR = I_0 R \sin(\omega t)$$

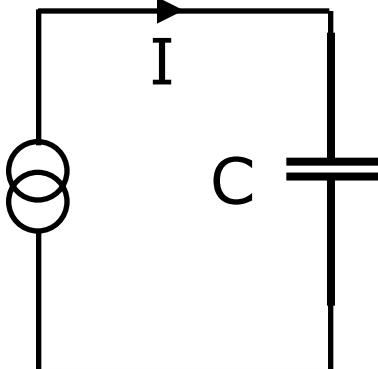

$$V_C = \frac{Q}{C} = \frac{1}{C} \int I_0 \sin(\omega t) dt$$



$$= -\frac{1}{\omega C} I_0 \cos(\omega t)$$
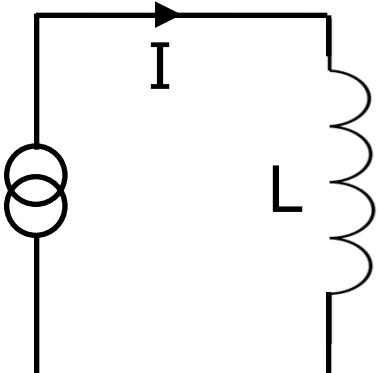
$$= \frac{1}{\omega C} I_0 \sin\left(\omega t - \frac{\pi}{2}\right)$$






$$V_L = L \frac{dI}{dt} = \omega L I_0 \cos(\omega t) = \omega L I_0 \sin\left(\omega t + \frac{\pi}{2}\right)$$

Phasors

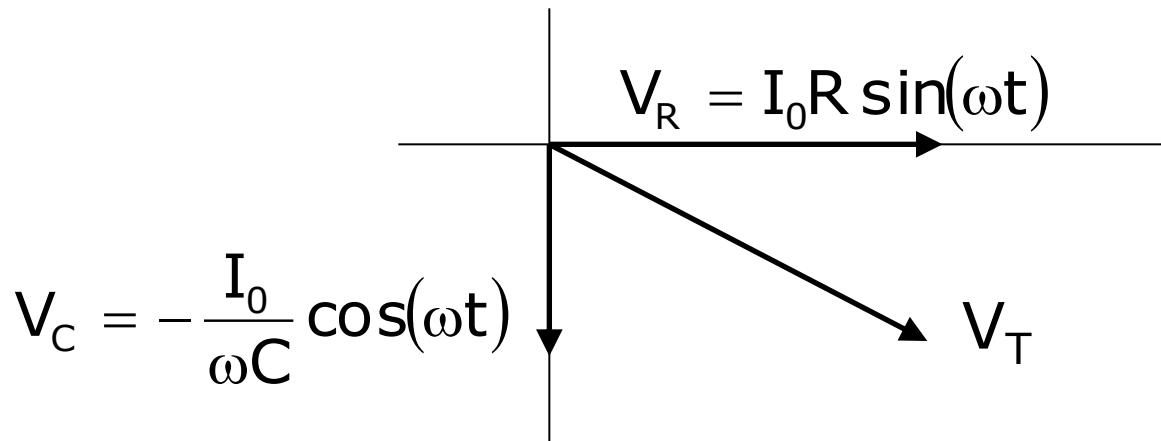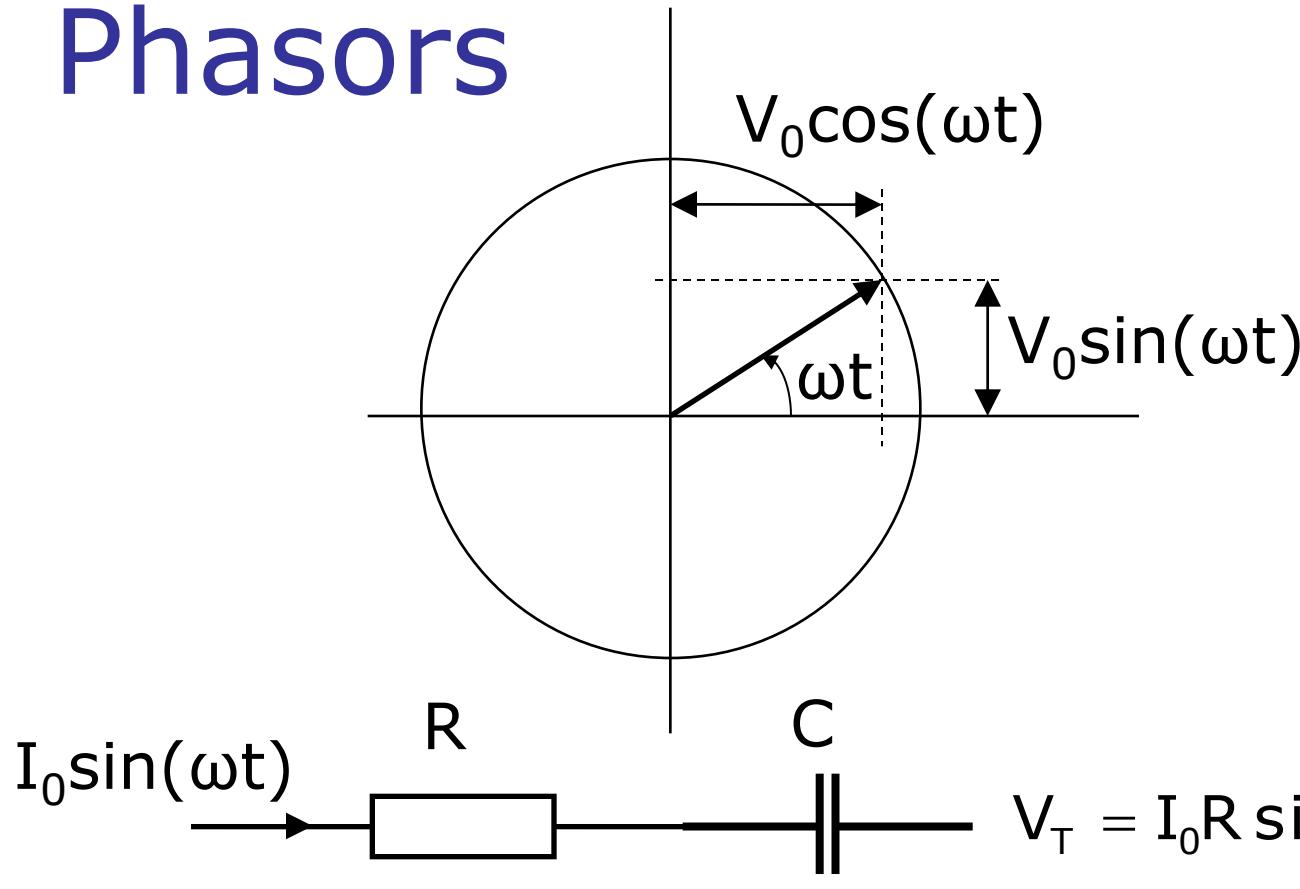

RC phasors

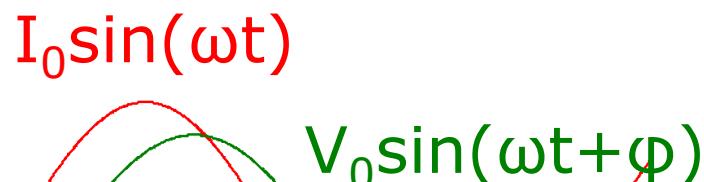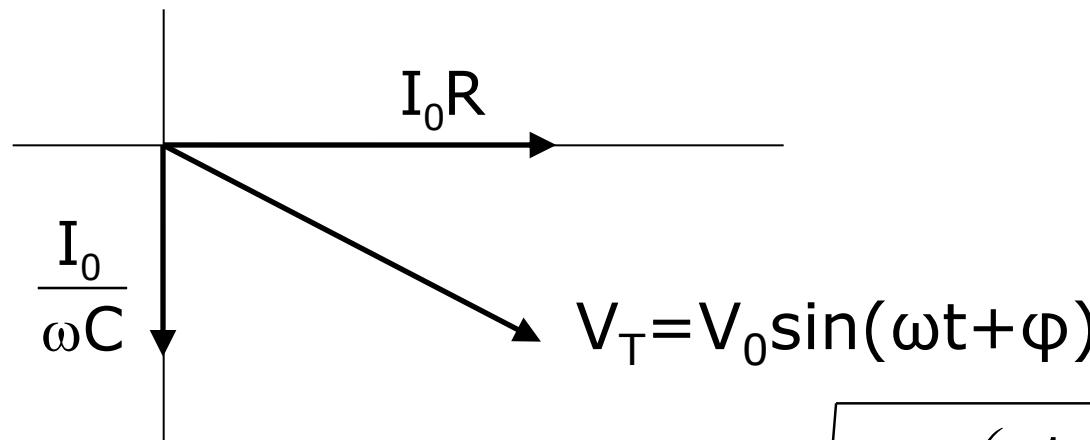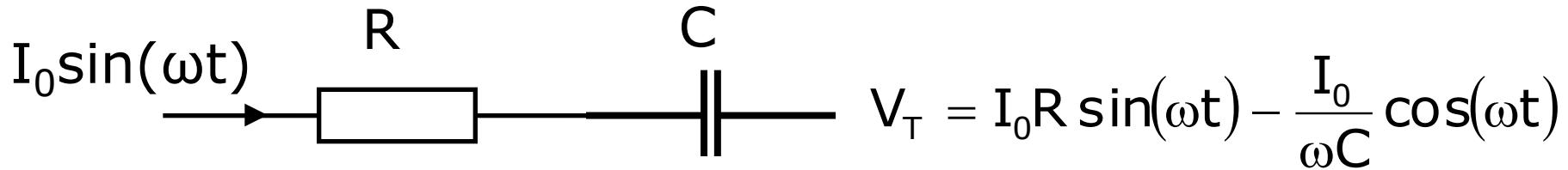

$$-\phi = \tan^{-1} \left(\frac{1}{\omega CR} \right)$$

$$V_0 = I_0 \sqrt{R^2 + \left(\frac{1}{\omega C} \right)^2}$$

$$\tan \phi = \frac{1}{\omega CR}$$

Phasors – mathematics

$$V_T = I_0 R \sin(\omega t) - \frac{I_0}{\omega C} \cos(\omega t)$$

$$V_T = V_0 \sin(\omega t + \phi)$$

$$V_0 = I_0 \sqrt{R^2 + \left(\frac{1}{\omega C} \right)^2}$$

$$\tan \phi = \frac{1}{-\omega CR}$$

$$A \sin(\omega t) + B \cos(\omega t) = R \sin(\omega t + \phi)$$

$$R \sin(\omega t + \phi) = R \sin(\omega t) \cos(\phi) + R \cos(\omega t) \sin(\phi)$$




$$A = R \cos(\phi) \quad B = R \sin(\phi)$$

$$A^2 + B^2 = R^2$$

$$B/A = \tan(\phi)$$

RL phasors

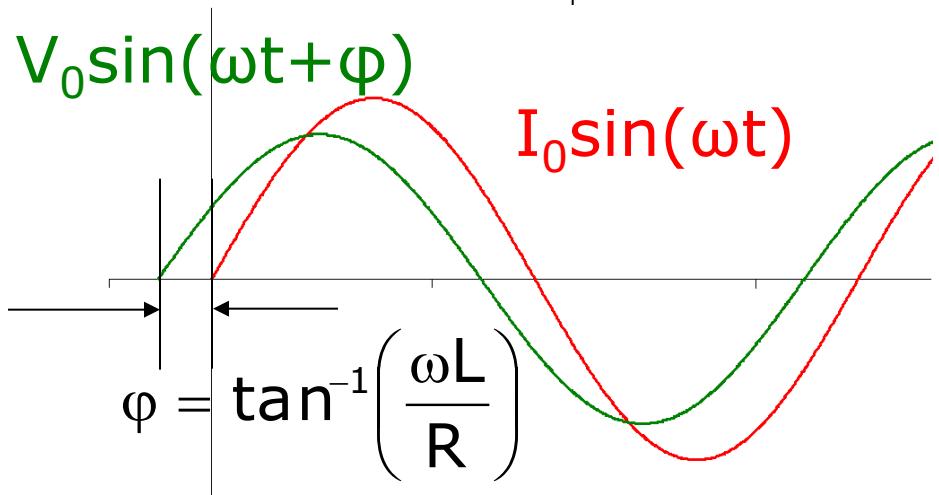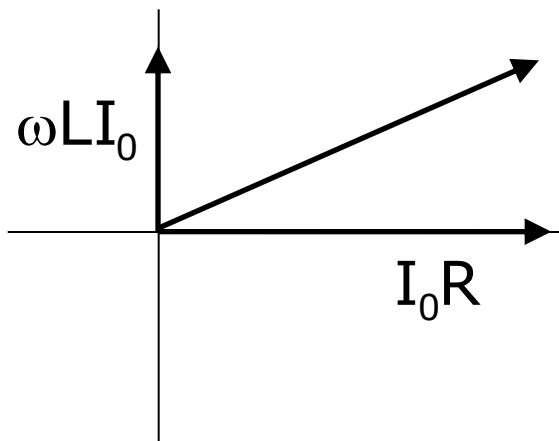
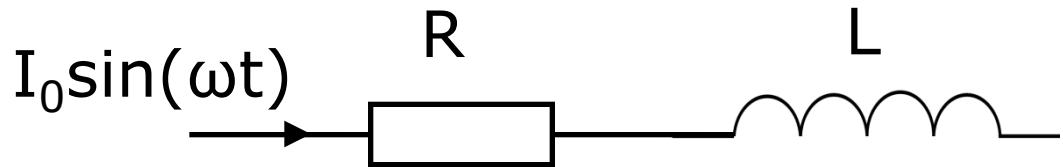
$$V_T = I_0 R \sin(\omega t) + \omega L I_0 \cos(\omega t)$$



$$V_0 = I_0 \sqrt{R^2 + (\omega L)^2}$$

$$\tan \varphi = \frac{\omega L}{R}$$

RL filter

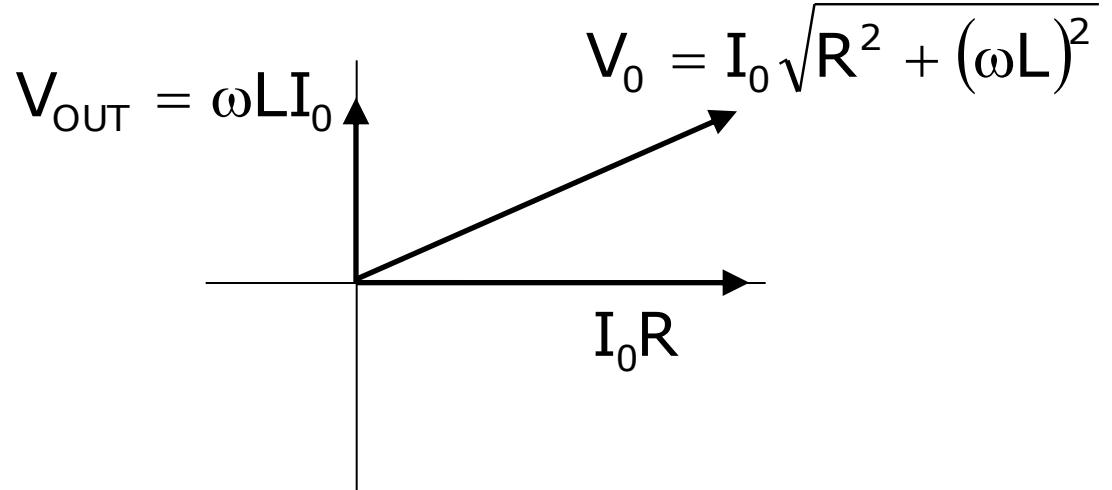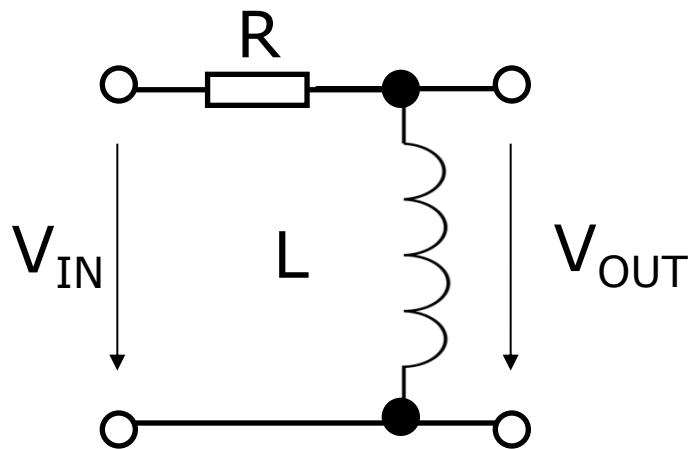


$$\left| \frac{V_{OUT}}{V_{IN}} \right| = \omega L \frac{1}{\sqrt{R^2 + (\omega L)^2}}$$

$$= \frac{\omega L / R}{\sqrt{1 + (\omega L / R)^2}}$$


$$\begin{aligned} \omega \rightarrow \infty & \quad \left| \frac{V_{OUT}}{V_{IN}} \right| \rightarrow 1 \\ \omega \rightarrow 0 & \quad \left| \frac{V_{OUT}}{V_{IN}} \right| \rightarrow 0 \end{aligned}$$

Phasors: RC filter

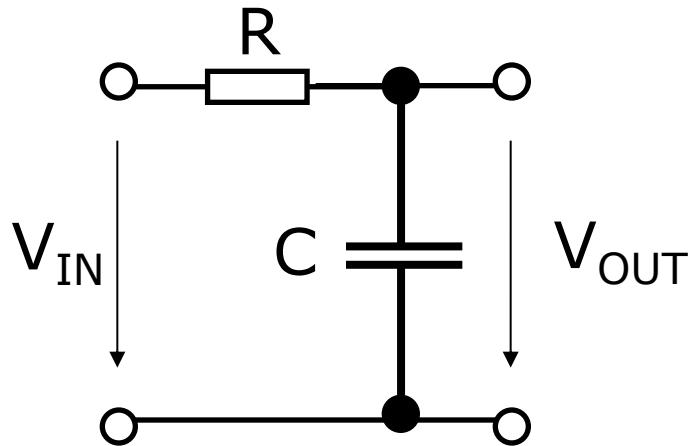

$$\left| \frac{V_{OUT}}{V_{IN}} \right| = \frac{1}{\omega C} \frac{1}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}}$$


$$= \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

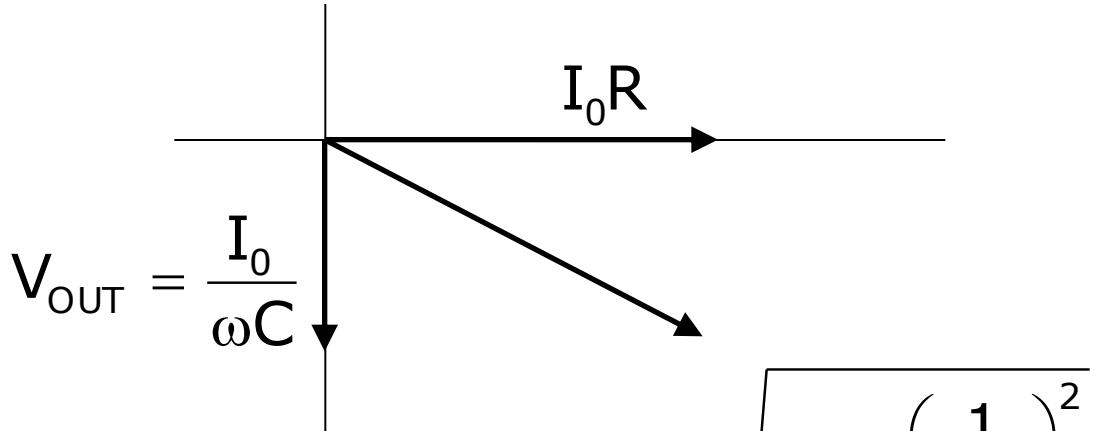

$$\omega \rightarrow \infty \quad \left| \frac{V_{OUT}}{V_{IN}} \right| \rightarrow 0$$


$$\omega \rightarrow 0 \quad \left| \frac{V_{OUT}}{V_{IN}} \right| \rightarrow 1$$

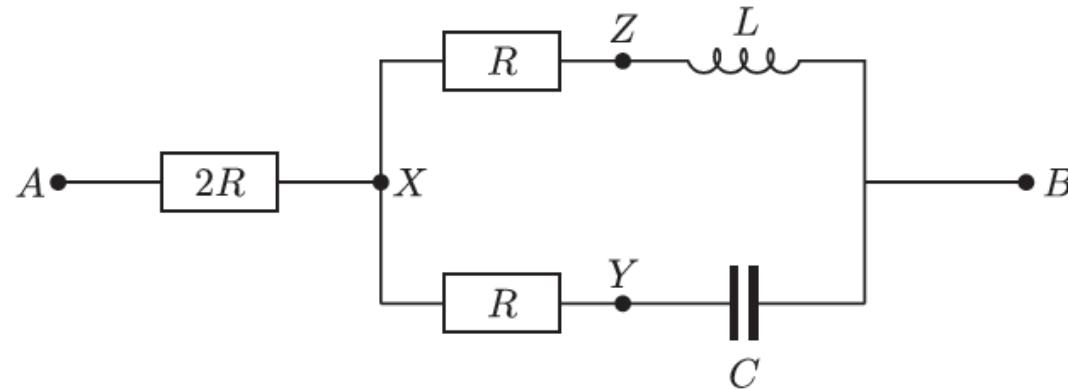7. Define what is meant by a complex impedance. What are the complex impedances of a resistor, a capacitor and an inductor? [6]



A voltage $V_{AB} = V_0 \cos \omega t$, where V_0 is a real amplitude, is applied between the points A and B in the network shown. Given that $\omega C = 1/(R\sqrt{15})$ and $\omega L = R\sqrt{15}$,

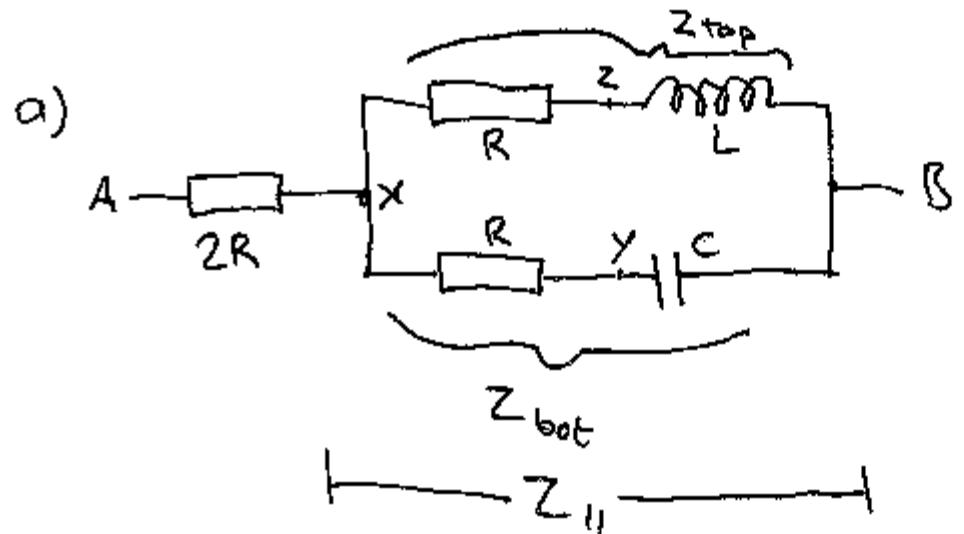- (a) calculate the total impedance between A and B, [4]
- (b) verify that voltages of equal amplitude are developed between the point X and the points A, Y and Z, and [6]
- (c) determine the phase of V_{XZ} relative to V_{AB} . [4]



$$\omega C = \frac{1}{R\sqrt{15}}$$

$$\omega L = R\sqrt{15}$$

$$Z_{AB} = 2R + Z_{II}$$

$$\frac{1}{Z_{II}} = \frac{1}{Z_{top}} + \frac{1}{Z_{bot}}$$

impedances in parallel

$$Z_{top} = R + j\omega L \quad \leftarrow$$

$$= R + jR\sqrt{15}$$

impedances in series

$$Z_{bot} = R + \frac{1}{j\omega C}$$

$$= R(1 - j\sqrt{15})$$



$$\frac{1}{Z_{II}} = \frac{1}{R(1+j\sqrt{15})} + \frac{1}{R(1-j\sqrt{15})}$$

$$Z_{II} = 8R$$

$$Z_{AB} = 10R$$

real
no net phase shift

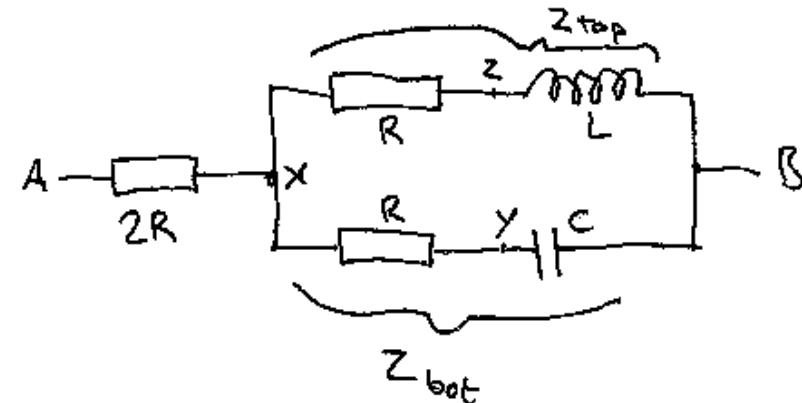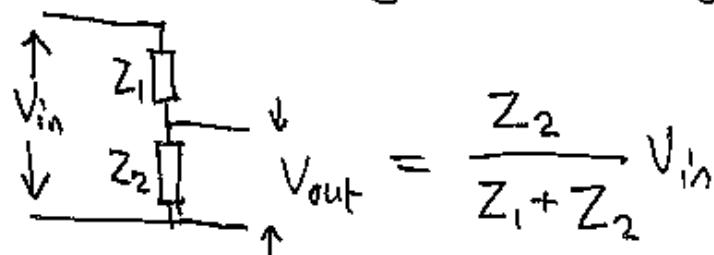b) To calculate voltage drops use general potential divider



$$V_{xA} = \frac{2R}{Z_{AB}} V_{AB} = \frac{1}{5} V_{AB}$$

$$V_{xx} = \frac{R}{Z_{bot}} V_{x_B}$$

$$V_{xz} = \frac{R}{Z_{top}} V_{x_B}$$

$$V_{xB} = \frac{4}{5} V_{AB}$$

$$= \frac{R}{R(1-j\sqrt{5})} \frac{4}{5} V_{AB}$$

$$= \frac{R}{R(1+j\sqrt{5})} \frac{4}{5} V_{AB}$$

$$= \frac{1}{4} e^{j\phi_{xy}} \frac{4}{5} V_{AB}$$

$$= \frac{1}{5} V_{AB} e^{j\phi_{xz}}$$

$$= \frac{1}{5} V_{AB} e^{j\phi_{xy}}$$

$$\text{so } |V_{xA}| = |V_{xx}| = |V_{xz}| = \frac{1}{5} V_0$$

c) V_{xz} lags behind V_{AB} by $\phi_{xy} = \tan^{-1} \sqrt{5}$