
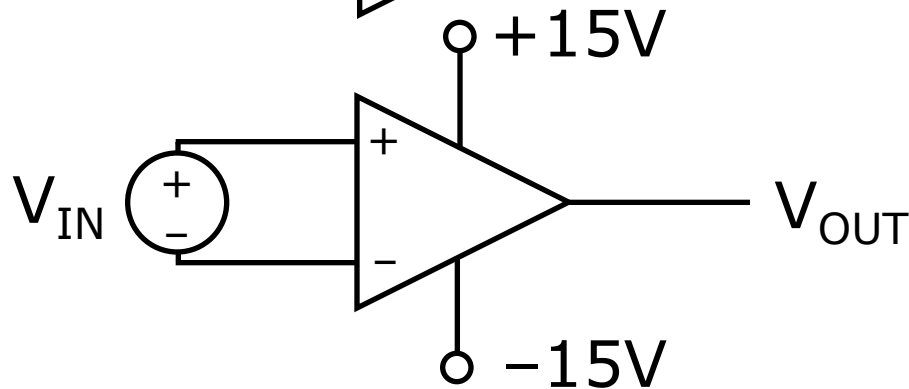




The Ideal Op-amp

(Operational amplifier)


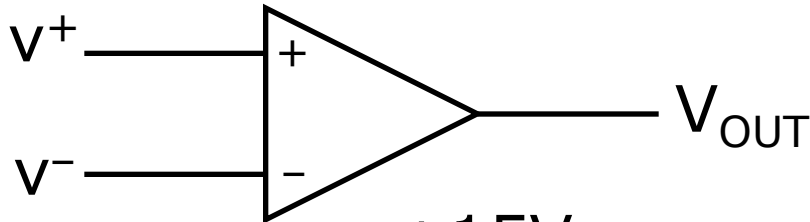


$$V_{OUT} = A(v^+ - v^-)$$

$$A \sim 10^5$$

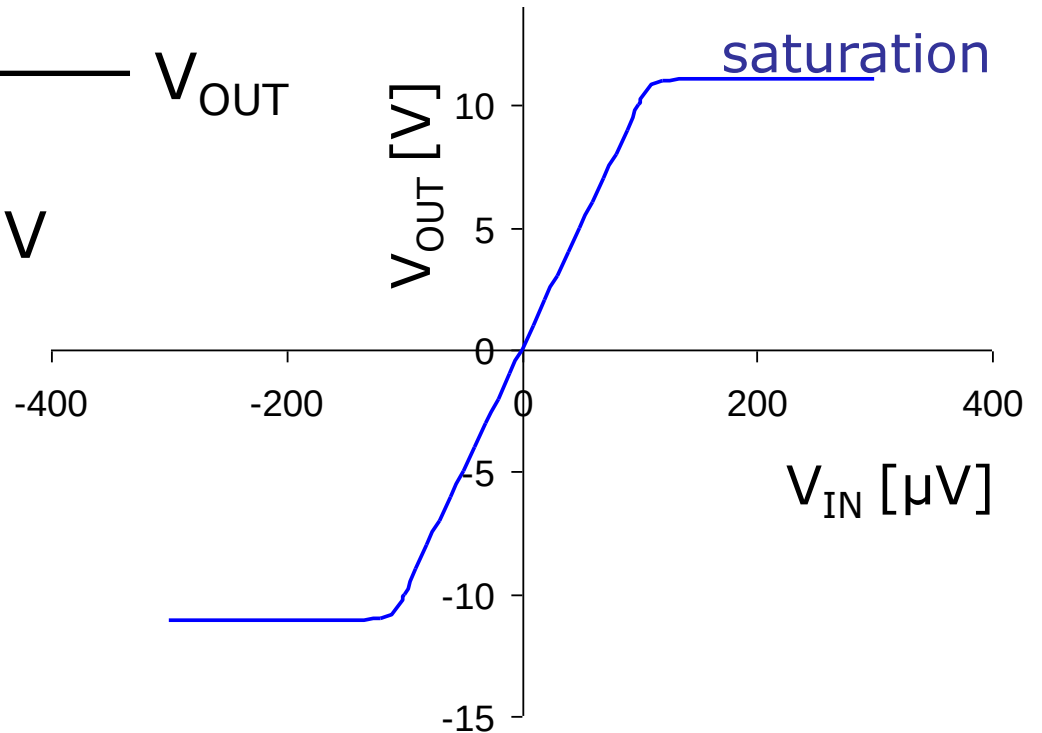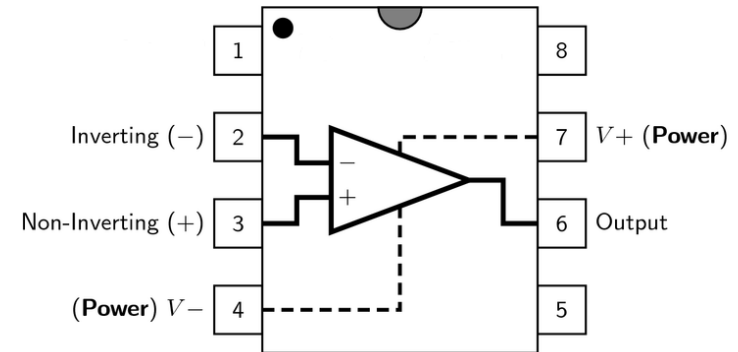

Op-amp Feedback

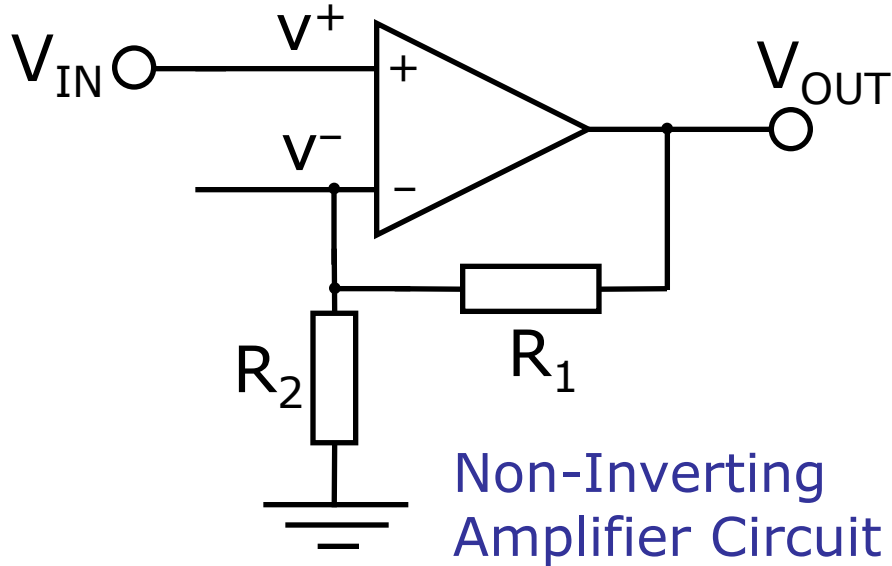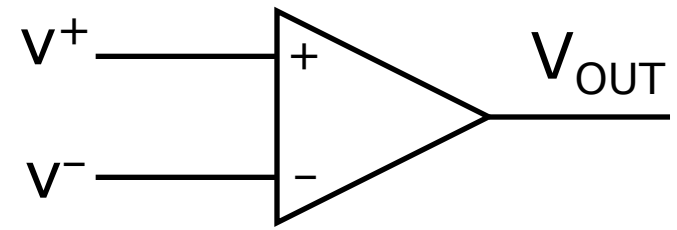

$$V_{OUT} = A(v^+ - v^-)$$

$$V_{OUT} = A \left(V_{IN} - V_{OUT} \frac{R_2}{R_1 + R_2} \right)$$

$$V_{OUT} \left(1 + A \frac{R_2}{R_1 + R_2} \right) = AV_{IN}$$

$$\frac{V_{OUT}}{V_{IN}} = \frac{A}{1 + \frac{AR_2}{R_1 + R_2}} \approx \frac{R_1 + R_2}{R_2}$$



Op-amp Feedback

Assumptions:


Gain is very large ($A \rightarrow \infty$)

Inputs draw no current ($Z_{IN} = \infty$)

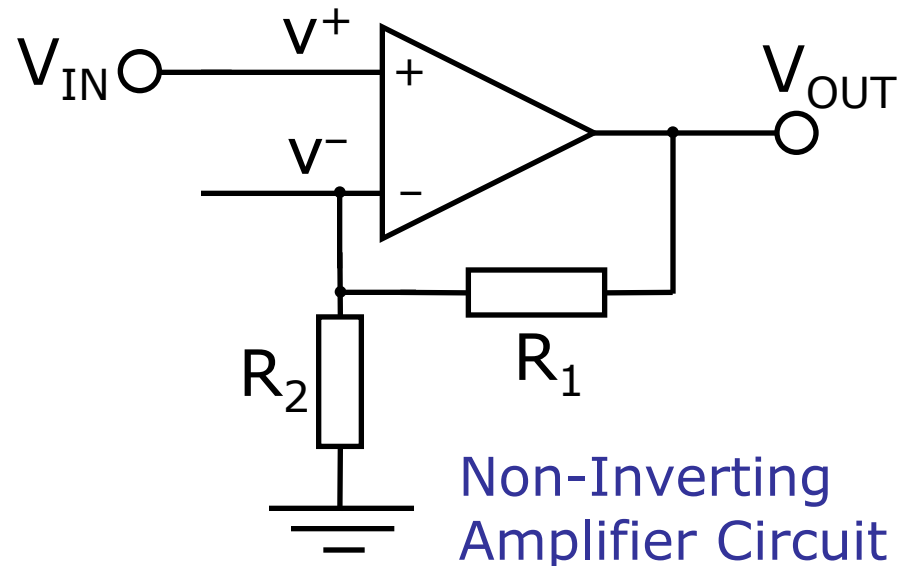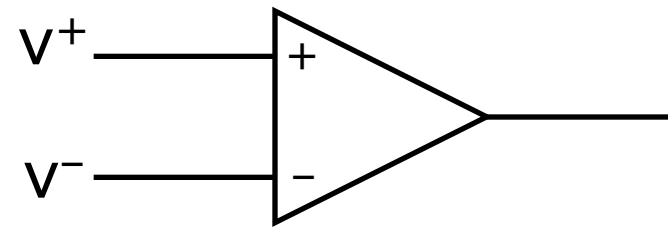Output attempts to make input voltage difference zero ($v^+ = v^-$)



Inverting Amplifier Circuit

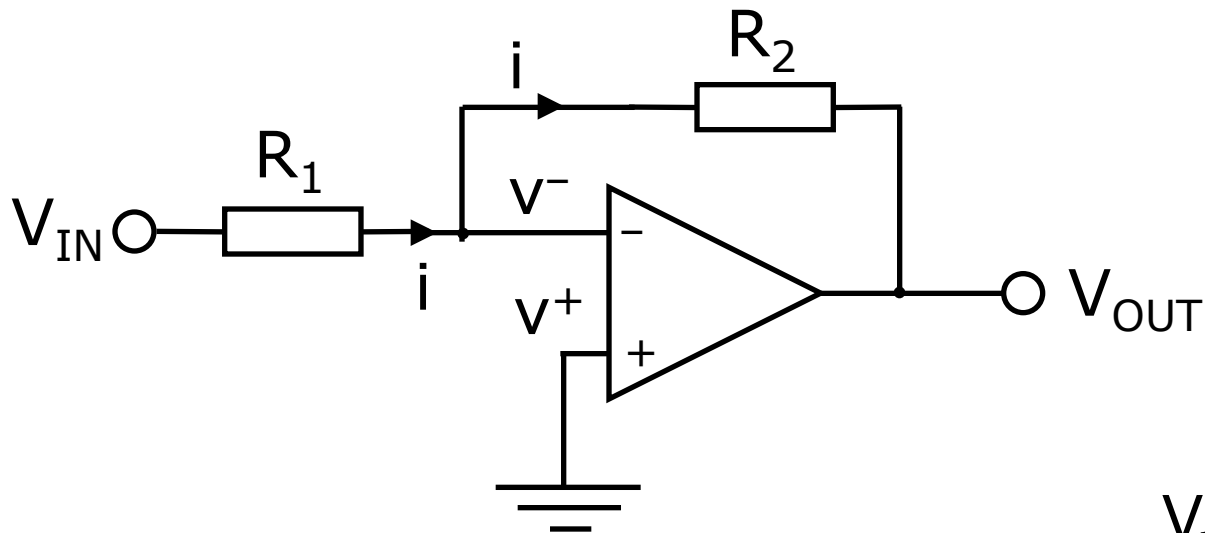


$$v^- \approx v^+ = 0$$

$$i = \frac{V_{IN}}{R_1} = -\frac{V_{OUT}}{R_2}$$


$$\frac{V_{OUT}}{V_{IN}} = -\frac{R_2}{R_1}$$

$$i = \frac{V_1}{R_1} + \frac{V_2}{R_1} + \frac{V_3}{R_1} = -\frac{V_{OUT}}{R_2}$$
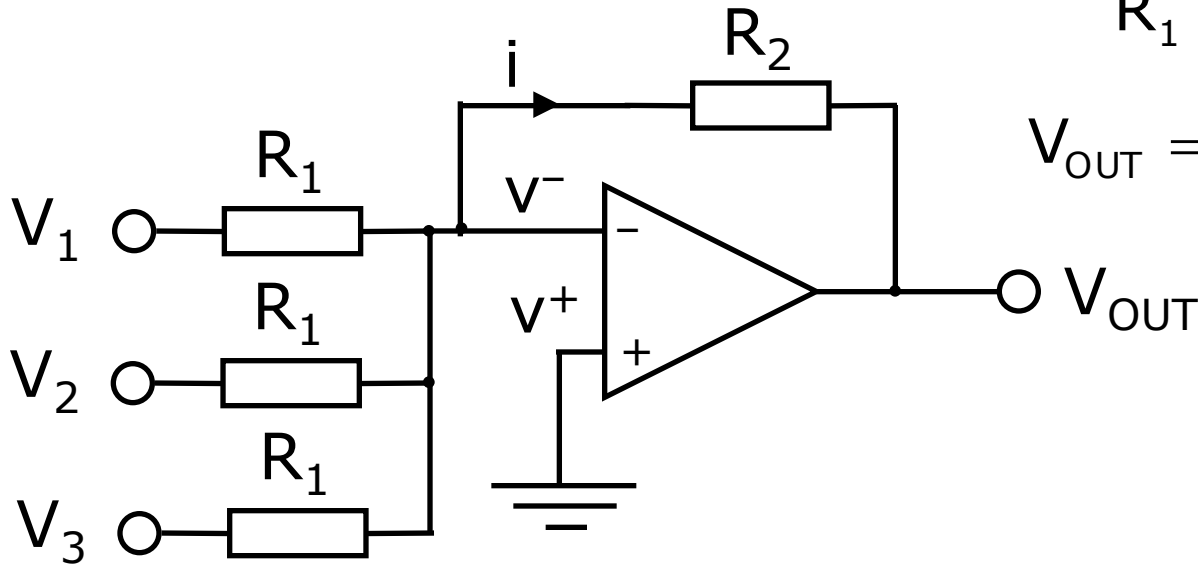
$$V_{OUT} = -\frac{R_2}{R_1} (V_1 + V_2 + V_3)$$




Summing amplifier

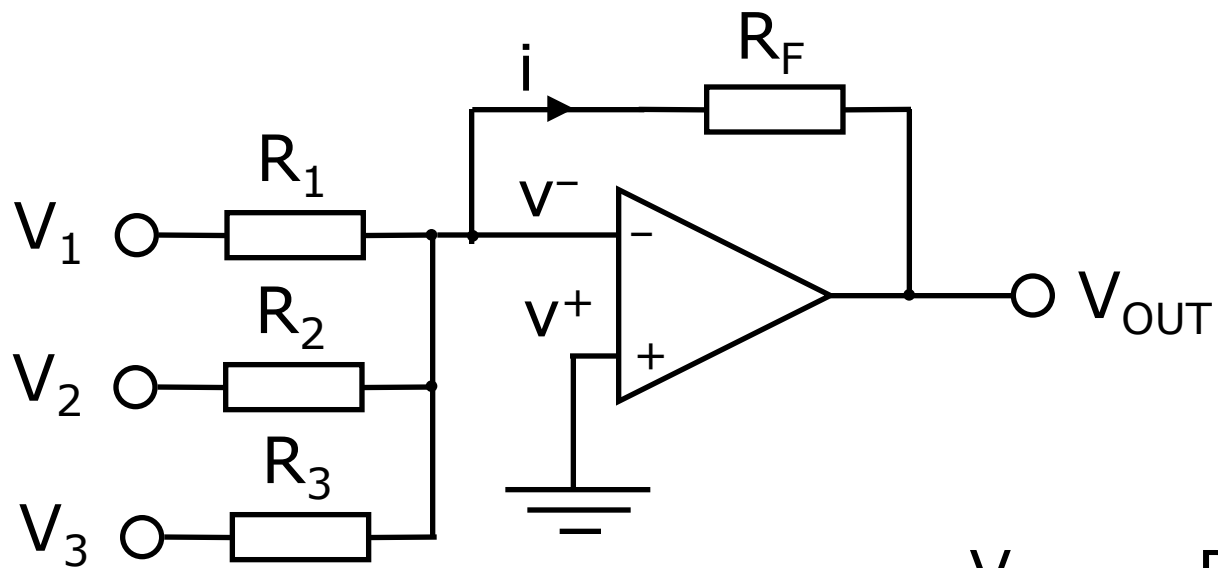

$$V_{OUT} = -R_F \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

Difference amplifier

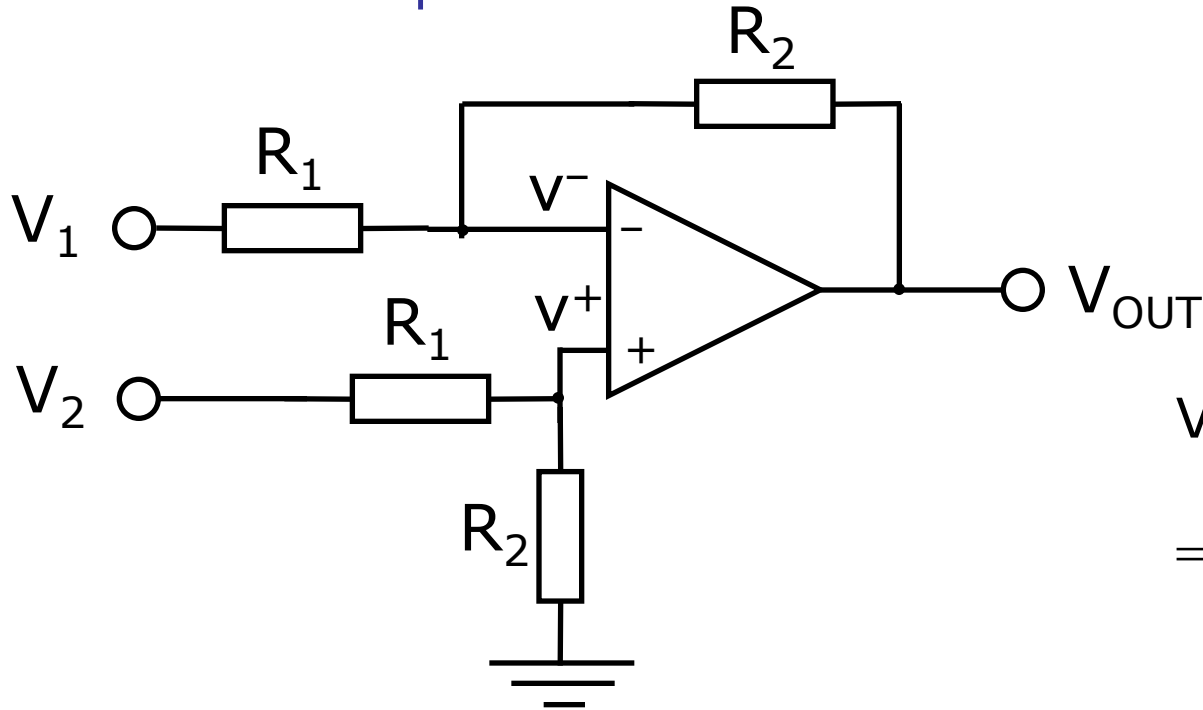


$$\begin{aligned}
 V_{OUT} &= v^- - iR_2 \\
 &= v^- - \left(\frac{V_1 - v^-}{R_1} \right) R_2 \\
 &= v^- \left(1 + \frac{R_2}{R_1} \right) - V_1 \frac{R_2}{R_1}
 \end{aligned}$$

$$v^+ = V_2 \frac{R_2}{R_1 + R_2}$$


$$v^+ \approx v^-$$

$$\begin{aligned}
 V_{OUT} &= V_2 \frac{R_2}{R_1 + R_2} \left(\frac{R_1 + R_2}{R_1} \right) - V_1 \frac{R_2}{R_1} \\
 &= (V_2 - V_1) \frac{R_2}{R_1}
 \end{aligned}$$

Integrator

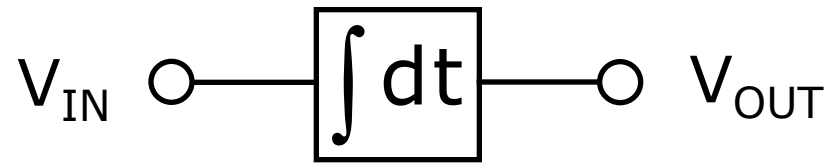


Capacitor as integrator

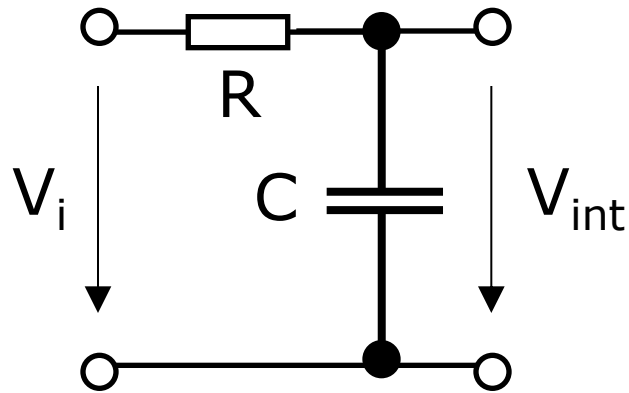


$$V_{int} = V_C = \frac{1}{C} \int_0^t I dt'$$
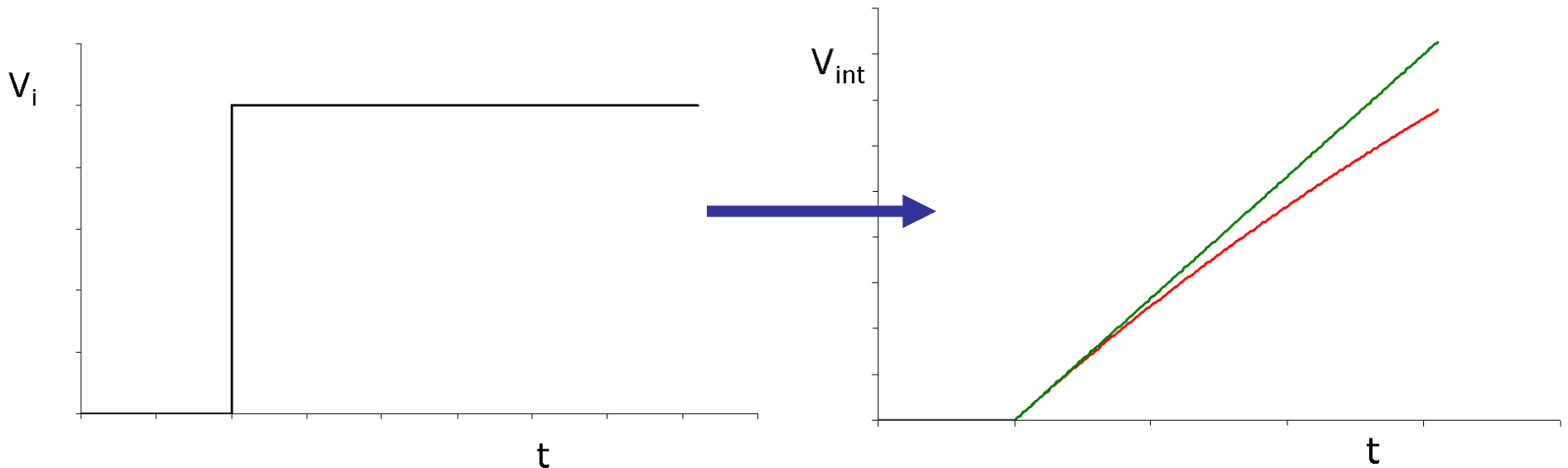
$$V_C = \frac{1}{C} \int_0^t \frac{V_i - V_C}{R} dt' \quad \text{If } RC \gg t$$
$$\approx \frac{1}{RC} \int_0^t V_i dt' \quad V_C \ll V_i$$



Op-amp Integrator

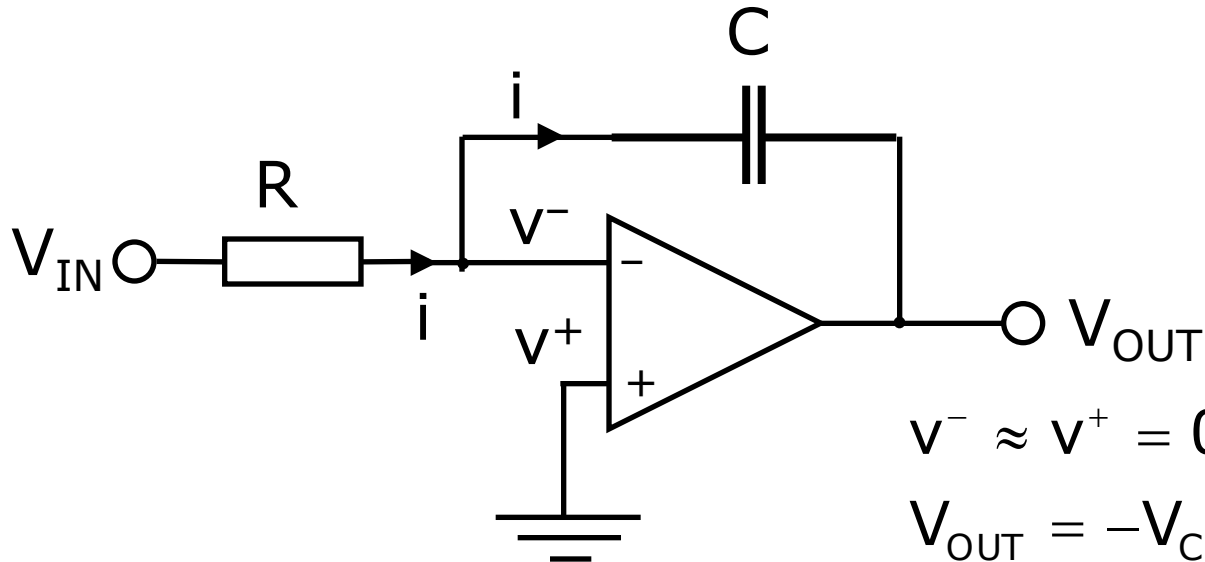


$$v^- \approx v^+ = 0$$

$$V_{OUT} = -V_C$$

$$V_{OUT} = -\frac{1}{C} \int_0^t i dt$$

$$V_{OUT} = -\frac{1}{C} \int_0^t \frac{V_{IN}}{R} dt$$


Differentiation

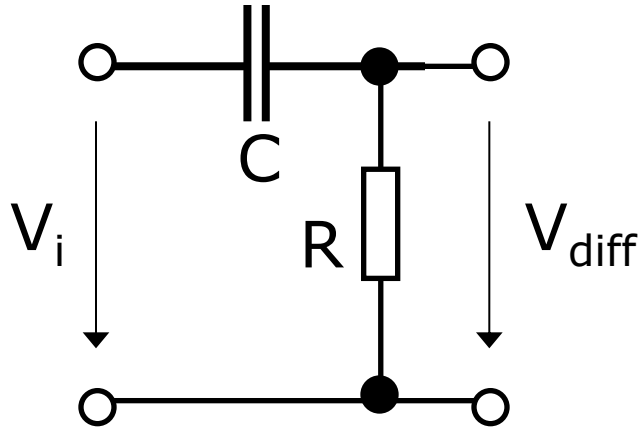



$$V_{diff} = V_R = RI = RC \left(\frac{dV_i}{dt} - \frac{dV_R}{dt} \right)$$

$$\text{Small } RC \rightarrow \frac{dV_i}{dt} \gg \frac{dV_R}{dt}$$

$$V_{diff} \approx RC \frac{dV_i}{dt}$$

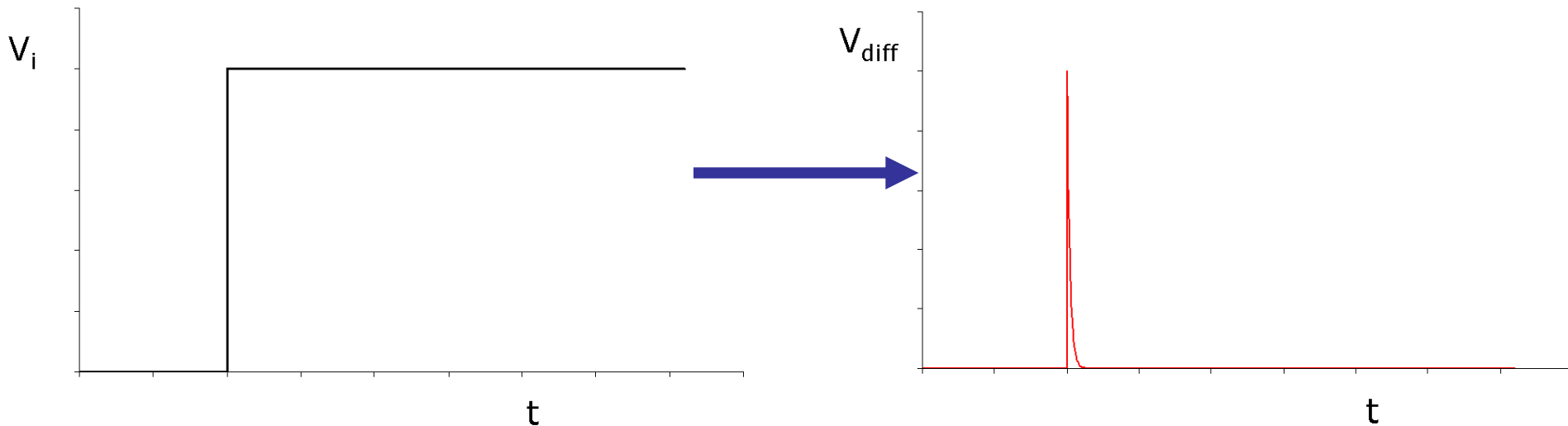

Op-amp Differentiator

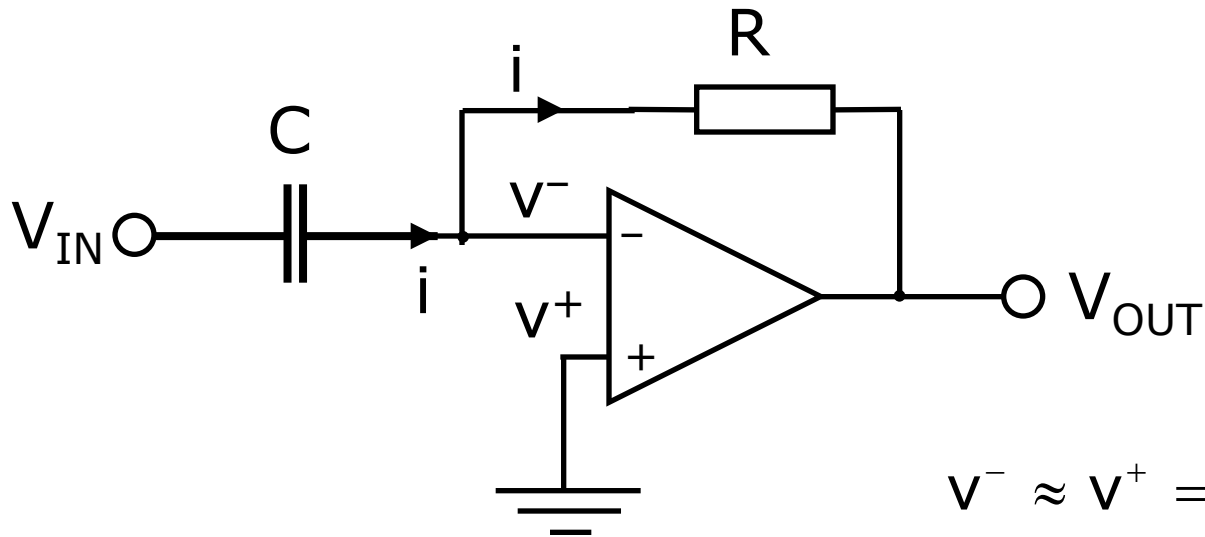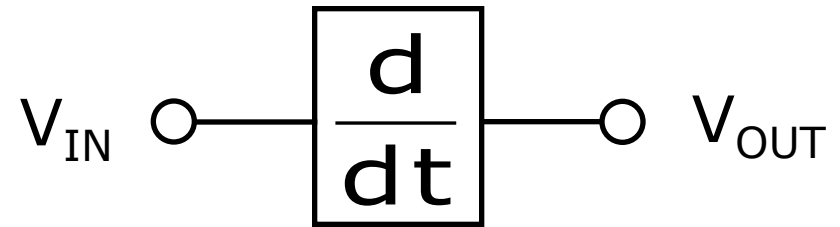


$$v^- \approx v^+ = 0$$

$$V_{OUT} = -iR$$

$$V_{OUT} = -RC \frac{dV_{IN}}{dt}$$

Complex analysis

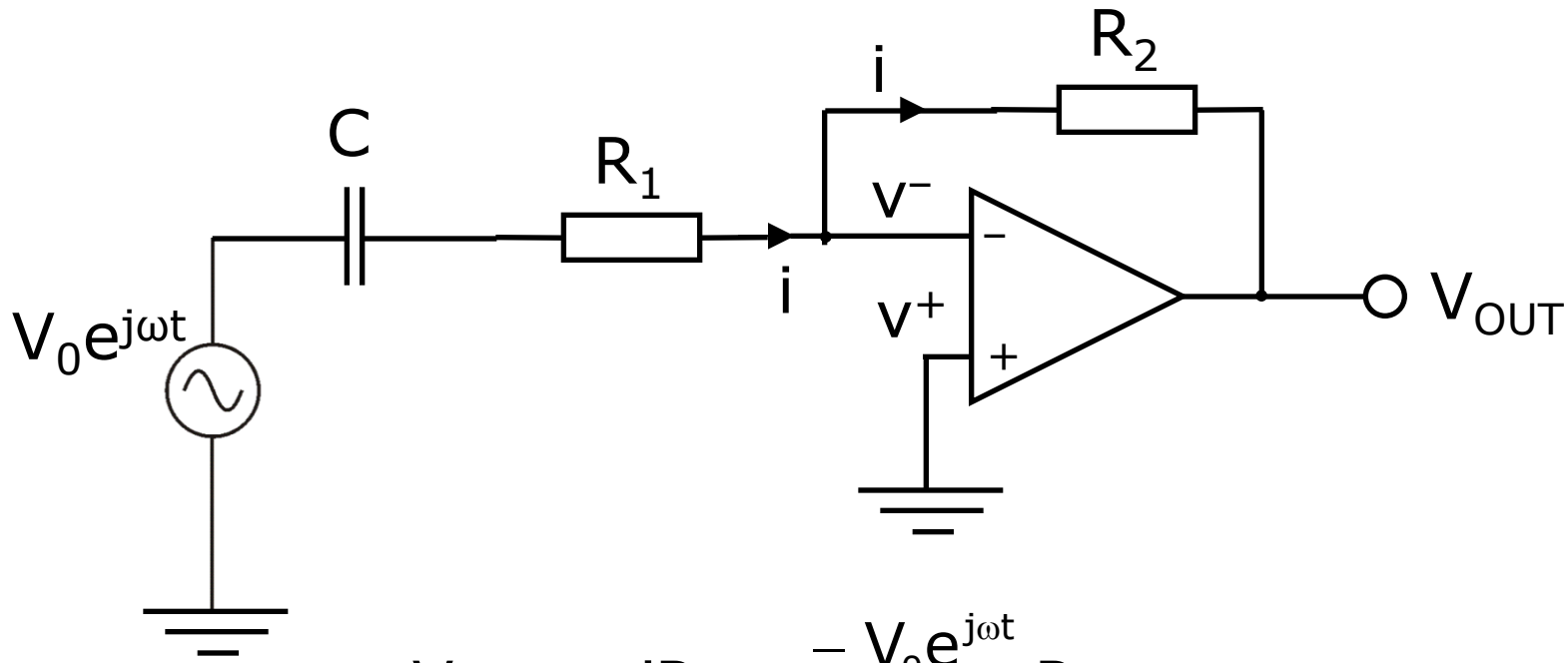

$$V_{OUT} = -iR_2 = \frac{-V_0 e^{j\omega t}}{R_1 - \frac{j}{\omega C}} R_2$$


$$= \frac{-j\omega CR_2 e^{j\omega t}}{1 + j\omega CR_1} V_0$$

High pass filter

$$\omega \rightarrow 0 \quad V_{OUT} = 0$$

$$\omega \rightarrow \infty \quad V_{OUT} = -\frac{R_2}{R_1} V_0 e^{j\omega t}$$

Exploiting op-amp saturation

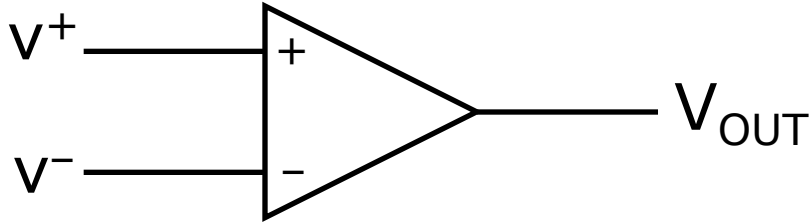


$$V_{OUT} = A(v^+ - v^-)$$

$A \rightarrow \infty$


Saturation voltage

$V_{OUT} = +V_{Sat} \quad v^+ > v^-$


$V_{OUT} = -V_{Sat} \quad v^+ < v^-$

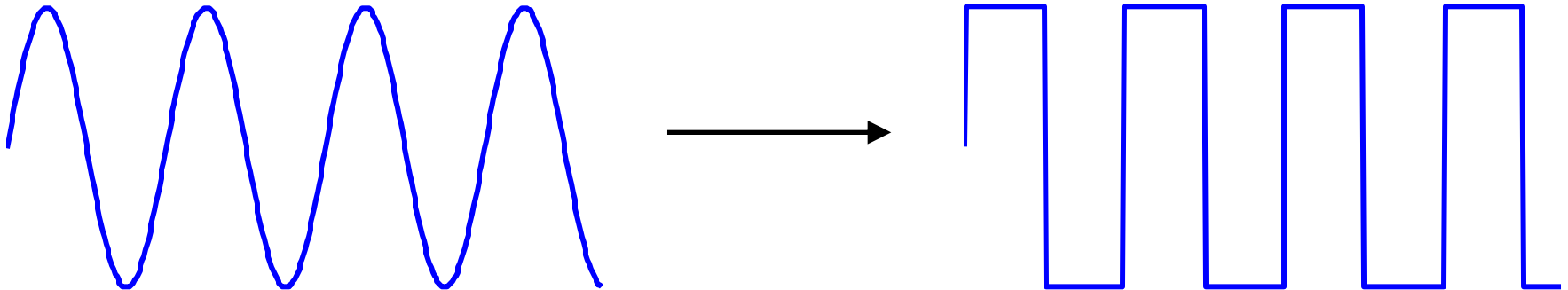

Analogue – digital conversion (ADC)

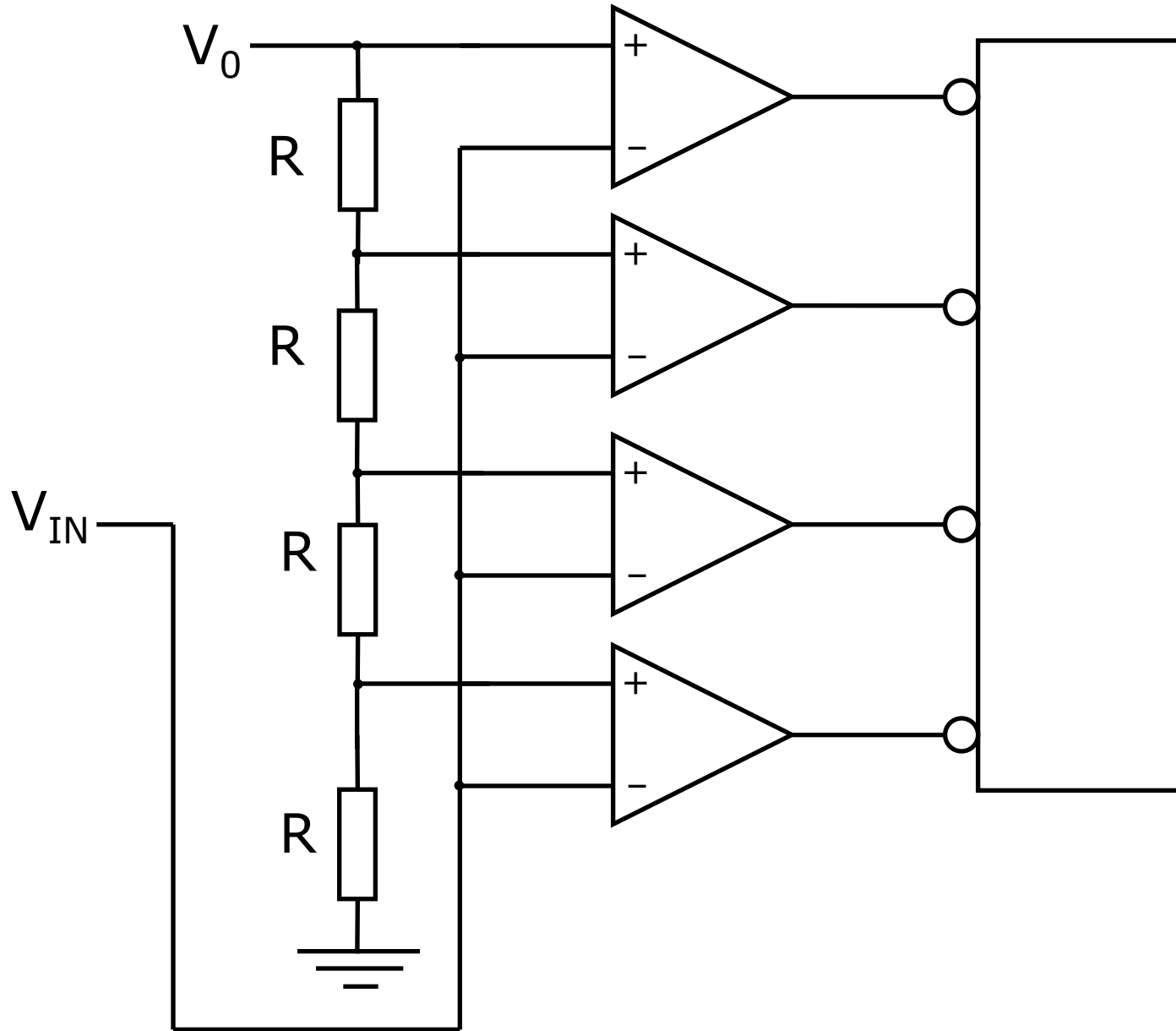

Oscillator

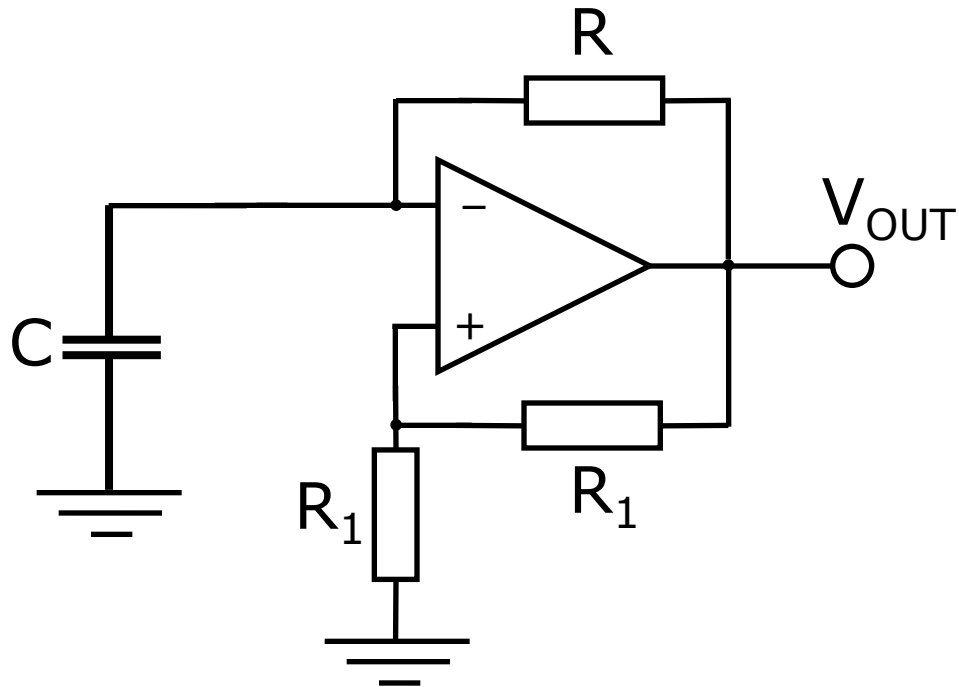

Op-amp applications

Building block of analogue electronics

Signal amplifiers

Audio amplifiers

Integrators / differentiators


Voltage / current sources

Active filters

Oscillators

Digital-analogue and analogue-digital convertors

Bridge circuits

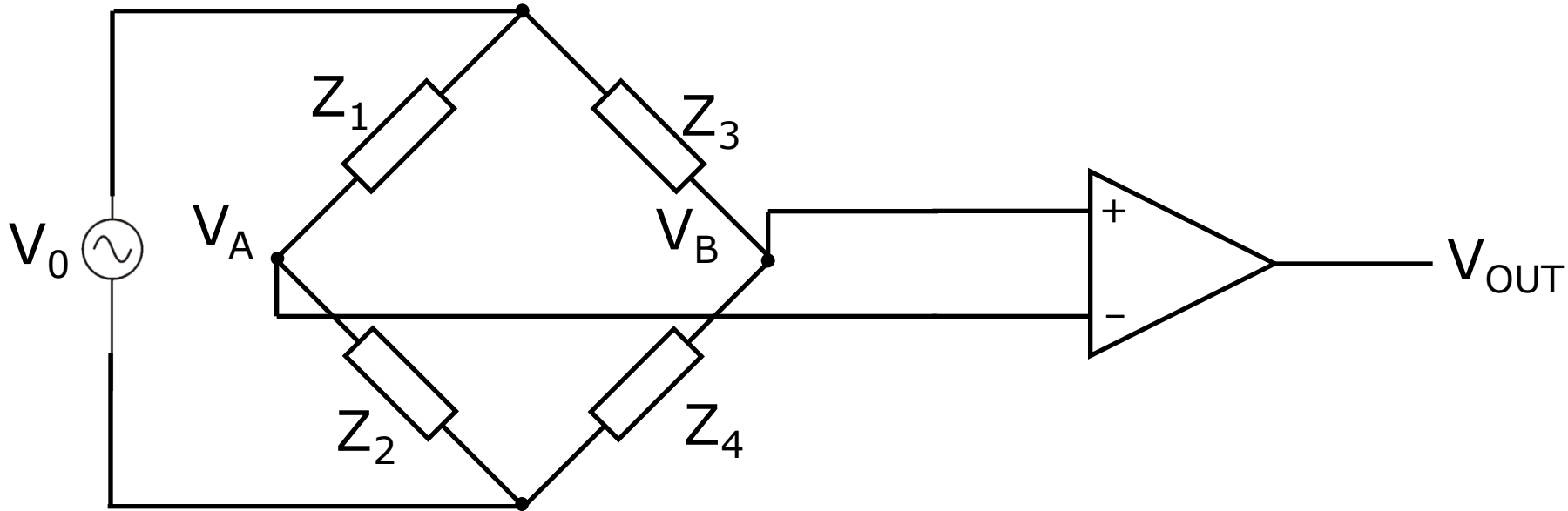

Bridge balanced when $V_A - V_B = 0$

$$Z_2 Z_3 = Z_4 Z_1$$



END OF OP-AMPS!