

¹ *Todd Huffman*

² **2nd year electronics**

³ Lecture notes

Contents

7	Reminder of 1st year material	1
8	Passive sign convention	1
9	Kirchhoff's laws	1
10	Network replacement theorems	2
11	AC circuit theory	2
12	Ideal op-amps	3
13	More realistic op-amps	4
14	Semiconductors	7
15	Diodes	7
16	Transistors	10
17	A first transistor amplifier circuit	12
18	The common-emitter amplifier	14
19	The common-collector amplifier or emitter follower	17
20	The long-tailed pair	18
21	The current mirror	19
22	Appendices	21
23	A Semiconductor principles	21
24	B Summary of approximate transistor circuit properties	23
25	C Circuit diagram symbols	24
26	D Open issues	25
27	Todd:	25
28	Tony	25
29	Index	27

Reminder of 1st year material

Passive sign convention

The passive sign convention is the standard definition of power in electric circuits. It defines electric power flowing from the circuit into an electrical component as positive, and power flowing into the circuit out of a component as negative. A passive component which consumes power, such as a resistor, will have positive power dissipation. Active components, sources of power such as electric generators or batteries, can have positive or negative power dissipation if there are more than one of them in a circuit, but if there is only one, it will have negative power dissipation.

The practical application of this principle of power for passive circuit elements is that one must label the positive terminal of the passive element as the one in which current flows. One can choose whether to first label the positive voltage terminal or to choose the direction of current flow, but once one of these two options is chosen, the other must be set accordingly so that the current flows into the positive terminal.

Kirchhoff's laws

There are two circuit laws first described by the German physicist Gustav Kirchhoff in 1845, which are extremely useful to understand any electrical circuit. The first one deals with the currents in the circuit:

At any point in the circuit the sum of currents flowing in is equal to the sum of currents flowing out.

This is also called 'Kirchhoff's current law' or KCL. For example see figure 1. Here the KCL at the node gives

$$\sum_n I_n = I_1 + I_2 - I_3 - I_4 = 0.$$

For physicists this is an obvious consequence of the charge carrier densities following a continuity equation, and ultimately local conservation of charge.

The second of Kirchhoff's laws is Kirchhoff's voltage law (KVL):

The directed sum of the electrical potential differences (voltage) around any closed network is zero.

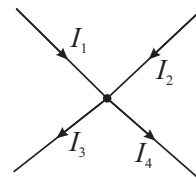


Figure 1: Example for Kirchhoff's current law.

61 The direction of the potential drops across resistances is given by the
 62 direction of the currents flowing through the resistor. For an example see
 63 figure 2. For this circuit

$$\sum_n V_n = -V_0 + IR_1 + IR_2 + IR_3 = 0.$$

64 The KVL is a consequence of the conservative character of the electro-
 65 magnetic force.

66 *Network replacement theorems*

67 Any linear electrical network with voltage and current sources and re-
 68 sistances can be replaced by an equivalent source and an equivalent
 69 resistor. Two types of equivalences are possible:

- 70 • Thevenin equivalent: The circuit can be replaced by an equivalent
 71 voltage source in series with an equivalent resistance. The equivalent
 72 voltage is the voltage obtained at the terminals of the network when
 73 they are not connected. The equivalent resistance is the resistance
 74 between the terminals if all voltage sources in the circuit are replaced
 75 by a short circuit and all current sources are replaced by an open
 76 circuit.
- 77 • Norton equivalent: The circuit can also be replaced by an equivalent
 78 current source in parallel with an equivalent resistance. The equiv-
 79 alent current is the current obtained if the terminals of the network
 80 are short-circuited. The equivalent resistance is again the resistance
 81 obtained between the terminals of the network when all its voltage
 82 sources are shorted and all its current sources open circuit.

83 The equivalent resistances for the two cases are the same, and the equiv-
 84 alent voltage and current sources are related as $V_{\text{Thevenin}} = R_{\text{eq}} I_{\text{Norton}}$
 85 with the equivalent resistance R_{eq} . The equivalent resistance can there-
 86 fore be found from the ratio of the voltage between the terminals with
 87 no load connected (V_{Thevenin}) divided by the current flowing when the
 88 terminals are shorted (I_{Norton}).

89 *AC circuit theory*

90 Alternating currents (AC) can be described by a harmonic time depen-
 91 dence $V(t) = V_0 \cos(\omega t)$. More complicated time dependencies can be
 92 expressed by the superposition of harmonic components with different
 93 frequencies using a Fourier series. In general the Fourier series is com-
 94 plex and we therefore describe the voltage by $V = V_0 e^{j\omega t}$. The complex
 95 phase introduced by this generalization is relevant as different param-
 96 eters in a circuit can have a different complex phase, equivalent to a phase
 97 shift of their harmonic development.

98 In passive circuits we can use a generalized form of Ohm's law

$$V = ZI, \quad (1)$$

99 where the impedance of a pure resistor is $Z = R$. For a pure inductor
 100 $Z = j\omega L$ (can be easily seen from the definition of the self-inductance

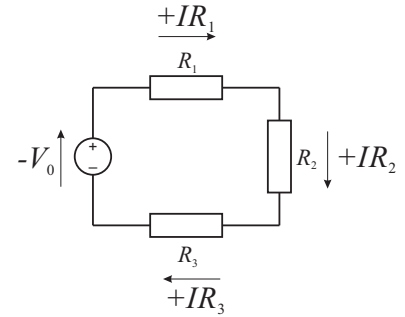


Figure 2: Example for Kirchhoff's voltage law.

These theorems can be extended to capacitances and inductances when they are expressed by their complex impedances (see next section below).

A voltage source is an electrical component which generates and maintains a difference in the electrical potential between its terminals, independent of the load (current).

A current source is a component which provides a defined current, independent of the voltage between its terminals.

Electronics engineers prefer the use of the letter 'j' for the imaginary unit, to distinguish it from 'i', which is often used to denote a current. We will follow this convention.

101 $V = L \frac{dI}{dt}$, and for a pure capacitance $Z = (j\omega C)^{-1}$ (from $Q = VC$ and
 102 $I = \frac{dQ}{dt}$). These can be combined, and the overall impedance of a passive
 103 network can be written as

$$Z = |Z|e^{j\phi}. \quad (2)$$

104 The current is then given by

$$I = \frac{V}{Z} = \frac{V_0 e^{j\omega t}}{|Z|e^{j\phi}} = \frac{V_0}{|Z|} e^{j(\omega t - \phi)}.$$

105 $|Z|$ gives the ratio of magnitudes of V and I , and ϕ gives the phase differ-
 106 ence by which the current lags the voltage.

107 Notice that the time-dependent part is a common factor for voltage
 108 and current, so $e^{j\omega t}$ can be omitted, but it is understood to be present
 109 when returning to the time domain.

Warning: this is only true for circuits with linear behaviour.

110 Ideal op-amps

111 An ideal op-amp is a differential amplifier: its output is $V_{\text{out}} = A(V_+ - V_-)$,
 112 with A the open-loop gain. Ideally, the open-loop gain is very large
 113 ($A \rightarrow \infty$), and the inputs have infinite input impedance (no current is
 114 flowing into the '+' and '-' inputs). The output impedance of the ideal
 115 op-amp is 0. Often op-amps are used in circuits with negative feedback
 116 (for examples see figures 3 and 4). In circuits with negative feedback the
 117 voltages at the two inputs adjust until they are equal, so that $V_+ = V_-$.
 118 This equality is sometimes referred to as a 'virtual' short.

Negative feedback circuits are circuits where the output is connected (through a resistor) back to the input, reducing the input (here connecting back to the '-' input).

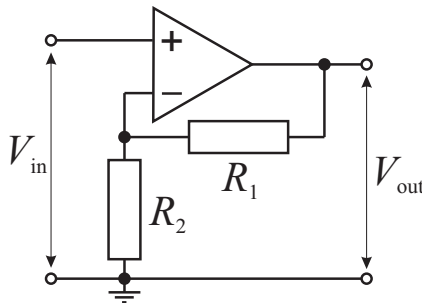


Figure 3: Non-inverting amplifier. The ideal gain of this circuit is $V_{\text{out}}/V_{\text{in}} = (R_1 + R_2)/R_2$ (You can see that from $V_+ = V_-$ and the voltage divider R_1 and R_2).

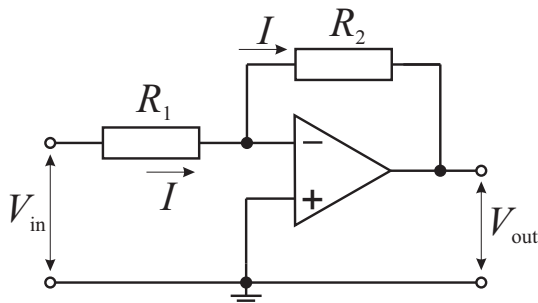


Figure 4: Inverting amplifier. The ideal gain of this circuit is $V_{\text{out}}/V_{\text{in}} = -R_2/R_1$ (You can see that from $V_- = 0$ and the currents through the resistors must be equal as there is no current flowing into the op-amp).

119 *More realistic op-amps*

120 A more realistic model of the op-amp will encompass a finite and
 121 frequency-dependent open-loop gain. Commonly the frequency re-
 122 sponse will be similar to a simple low-pass RC filter. Stray capacitances
 123 within the circuit would cause such a behaviour, but often it is achieved
 124 by design and the deliberate use of capacitances in the circuit, to pre-
 125 vent instabilities at high frequencies. Typical DC gains for real op-amps
 126 are about 10^6 , and the gain starts to decrease above a frequency around
 127 $\omega = 1 \text{ rad/s}$ (see figure 6 for an example).

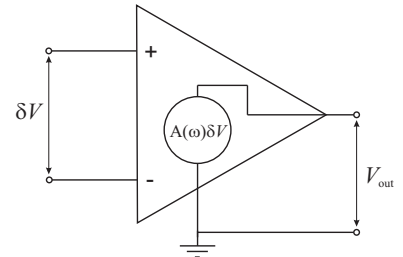


Figure 5: More realistic op-amp replacement diagram.

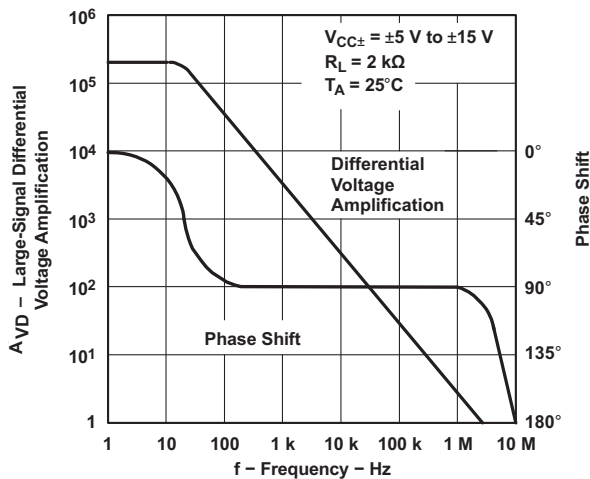


Figure 6: Frequency response of the TL081, a widely used operational amplifier from Texas Instruments (datasheet from <http://www.ti.com/lit/ds/symlink/tl081.pdf>).

This specific op-amp has a slightly lower gain ($\sim 2 \times 10^5$) and cuts-off at a slightly higher frequency ($f_{\text{cut-off}} \approx 20 \text{ Hz}$) than described in the text.

128 A simple replacement circuit reproducing the behaviour around the
 129 roll-off and up to reasonably high frequencies ($\sim 1 \text{ MHz}$) is shown in
 130 fig. 7.

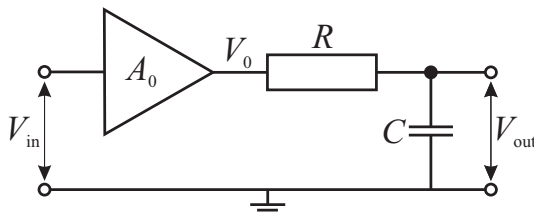


Figure 7: Simple replacement circuit to model a real op-amp.

131 The amplifier in this circuit is again an ideal op-amp with frequency-
 132 independent open-loop gain A_0 , so that $V_0 = A_0 V_{\text{in}}$. Here we assume
 133 that the load which we will connect to this circuit has infinite input
 134 impedance, so that due to the KCL the current the resistor equals the

135 current through the capacitor

$$\frac{V_{\text{out}} - V_0}{R} + j\omega C V_{\text{out}} = 0.$$

136 Substituting V_0 yields

$$A(\omega) = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{A_0}{1 + j\omega CR} = \frac{A_0}{1 + j\frac{\omega}{\omega_0}}, \quad (3)$$

137 with the cut-off frequency ω_0 .

138 What effect does this frequency characteristics have on the gain in a
139 negative feedback circuit? We will study this here for the example of an
140 inverting amplifier (figure 4). We start with the KVL for the input and the
141 feedback legs:

$$V_{R_1} - \delta V - V_{\text{in}} = 0$$

$$V_{R_2} + \delta V + V_{\text{out}} = 0.$$

Note that we do not assume $\delta V = 0$ anymore.

142 We still assume that no current is flowing into the op-amp and therefore,
143 using the KCL,

$$\frac{V_{R_1}}{R_1} = \frac{V_{R_2}}{R_2}.$$

144 Combining these equations yields

$$\frac{V_{\text{in}} + \delta V}{R_1} = -\frac{V_{\text{out}} + \delta V}{R_2},$$

145 OR

$$\frac{V_{\text{in}}}{R_1} = -\frac{V_{\text{out}}}{R_2} - \delta V \left(\frac{1}{R_2} + \frac{1}{R_1} \right).$$

146 We can now use the gain characteristics described before

$$V_{\text{out}} = A(\omega)\delta V,$$

147 and we get

$$V_{\text{in}} = -\frac{R_1}{R_2} V_{\text{out}} - \frac{V_{\text{out}}}{A(\omega)} R_1 \left(\frac{1}{R_2} + \frac{1}{R_1} \right),$$

148 and

$$\frac{V_{\text{out}}}{V_{\text{in}}} = -\frac{R_2}{R_1 + \frac{R_1 + R_2}{A(\omega)}}.$$

149 With the parametrization in eq. (3) $A(\omega) = A_0(1 + j\omega RC)^{-1}$ this yields

$$\frac{V_{\text{out}}}{V_{\text{in}}} = -\frac{R_2}{R_1 + \frac{(R_1 + R_2)(1 + j\omega/\omega_0)}{A_0}}.$$

150 A further approximation is that to achieve some gain $R_2 \gg R_1$ and
151 therefore

$$\frac{V_{\text{out}}}{V_{\text{in}}} \simeq -\frac{R_2}{R_1 + \frac{R_2(1 + j\omega/\omega_0)}{A_0}}.$$

152 This equation is demonstrated in figure 8. Note that despite the strong
153 frequency dependency of the open loop gain the gain of the feedback
154 circuit is constant up to much higher frequencies (10^4 rad/s compared to
155 $\omega_0 = 1$ rad/s in this example). This is because the amplifier only needs to
156 provide the gain to uphold the feedback, which is much lower than the
157 open loop gain it can provide at low frequency.

158 The frequency response for the non-inverting amplifier has a similar
159 behaviour.

You will see this in the EL16 practical.

160 The next level of op-amp imperfection which could be considered
161 for an even more realistic op-amp model would be the finite input and
162 output impedances.

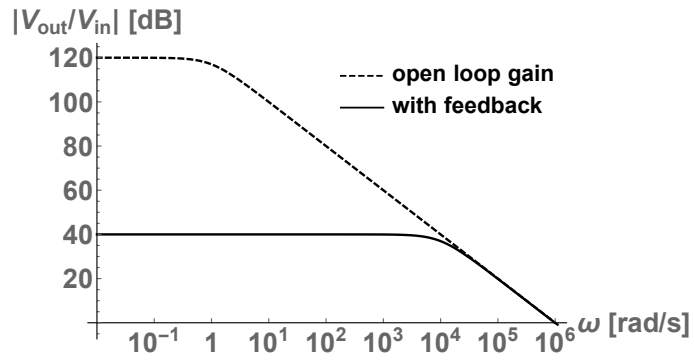


Figure 8: Frequency response of inverting amplifier ($A_0 = 10^6$, $\omega_0 = 1$ rad/s, $R_2 = 10$ k Ω and $R_1 = 100$ Ω).

dB is a unit often used in electronics. It is defined as $20 \log_{10}(V_{out}/V_{in})$.


Semiconductors

Let's now investigate the components which allow us to build active circuits like operational amplifiers. Today almost all these components are made from semiconductors, typically silicon or germanium.

In this course we will use very simple models for the behaviour of semiconductor devices like the diode or the transistor in electrical circuits which do not require a detailed understanding of the quantum mechanics and the solid state physics in the semiconductor. If you are interested in these topics there is a slightly more detailed discussion in the appendix of this document and further material can be found in the Practical Course Electronics Manual.

Diodes

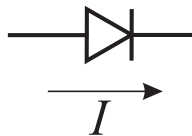A circuit diagram representation of a diode is shown in figure 9.



In a diode there is one direction in which a current will easily flow (indicated by the arrow in figure 9). A current in the opposite direction will be blocked.

The number of charge carriers which are capable of entering the valence band at a temperature T is given by the Boltzmann distribution and therefore the current-voltage relation for a diode is given by

$$I = I_0 \left(e^{\frac{eV_D}{k_B T}} - 1 \right), \quad (4)$$

where I is the current through the diode and V_D the voltage across the diode. At room temperature $k_B T/e \approx 25$ mV. I_0 is the reverse bias saturation current. Its exact value depends on the doping concentrations and the temperature, but is typically of the order $I_0 \approx 10^{-10}$ mA for silicon diodes. The resulting characteristics is shown in figure 10. Note that the second term in the bracket quickly becomes negligible against the exponential for positive bias voltages, and can be omitted in that case.

It should be obvious that a diode is a highly non-linear device. Ohm's law does not apply. Other tricks that don't work are

1. the Norton equivalent,
2. the Thevenin equivalent, and

Due to the limited time available we will not discuss diodes in the lectures, but this section is part of the notes to give useful background material.

Figure 9: Circuit diagram representation of a diode.

This equation is also known as the Shockley diode equation.

A more general version of this equation includes an ideality factor n (typically varies from 1 to 2) in the denominator of the exponential, to account for imperfections of junctions in real devices.

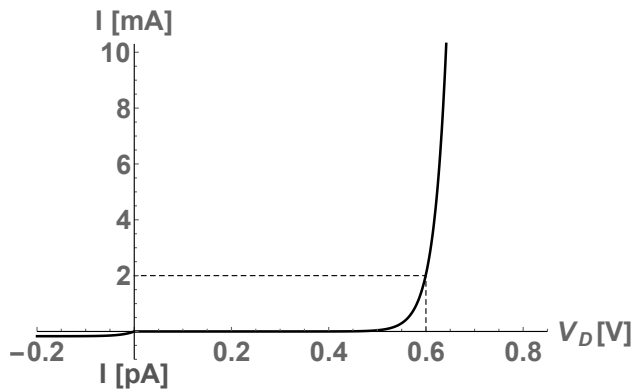


Figure 10: Diode current-voltage relation. The scale on the positive and negative y-axis differs by a factor 10^9 .

For a real diode there is a breakdown voltage at which the diode becomes conductive in reverse bias (not shown in this figure). Usually this breakdown is avoided in circuit design, because its properties are badly defined, but there is a special class of diodes, so called Zener diodes, which exploit this breakdown.

193 3. superposition.

194 Still valid are KCL and KVL and the relation for power ($P = VI$, but not
195 the $P = I^2R$ or $P = V^2/R$ variants).

196 A simple circuit with a diode is shown in figure 11. How can we find
197 the operating point of this circuit?

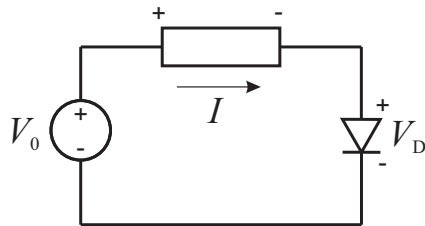


Figure 11: A simple circuit with a diode.

Note that the diode is not an active component and therefore not a power source, which justifies the signs in the figure.

198 We have

$$V_0 = V_R + V_D$$

199 and

$$I = I_0 \left(e^{\frac{eV_D}{k_B T}} - 1 \right), \text{ and} \quad (5)$$

$$I = \frac{V_R}{R} = \frac{V_0 - V_D}{R}.$$

200 The easiest way to solve these two equations for I and V_D is by graph-
201 ical or numerical means. Each of these equations can be plotted in a
202 current-voltage diagram for the diode and where the two intersect is the
203 operating point of the diode (figure 12).

204 This is very nice, and also correct, but difficult to do for more compli-
205 cated circuits. Let's try a different approach.

206 We start with noting that

$$\frac{dI}{dV_D} = \frac{I_0 e^{\frac{eV_D}{k_B T}}}{k_B T} \equiv \frac{1}{r_D},$$

207 where r_D is the small signal equivalent resistance of the diode. We have
208 seen that at room temperature the forward bias is approximately 0.6 V.

209 We can use $I \approx I_0 e^{\frac{eV_D}{k_B T}}$ for forward bias to get

$$\frac{dV_D}{dI_D} = r_D \approx \frac{25 \text{ mV}}{I_D} = \frac{25 \Omega}{I_D [\text{mA}]} \quad (6)$$

We will use the following notation convention: DC currents and voltages defining the working point are capitalized (e.g. V_0 , I_D etc.). Small signals around that working point (and corresponding resistances) are written in small cursive script (e.g. v_{in} , i_D , r_D , etc.). These are often, but not necessarily, AC.

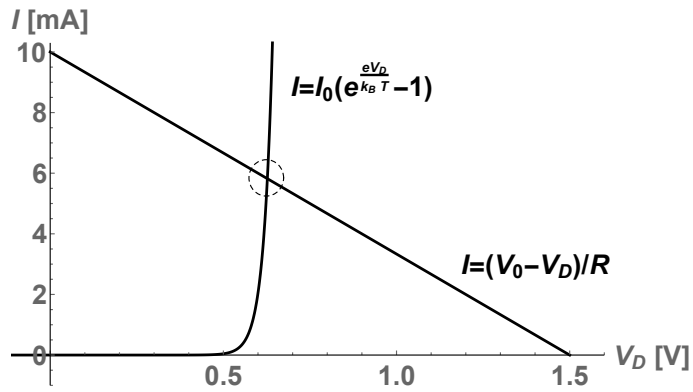


Figure 12: Finding the operating point for the diode ($V_0 = 1.5 \text{ V}$, $R = 150 \Omega$). Note that the voltage across the diode is always close to 0.6 V as long as the current is reasonably large. This voltage is sometimes referred to as the 'knee' voltage of the diode.

210 For small deviations from the operating point this gives a linear be-
 211 haviour and we can use an equivalent linear circuit, which will work as
 212 long as we have "small signals" (figure 13). However, we should be aware
 213 that this equivalent resistance is not a constant, but depends on the
 214 operating point (current).

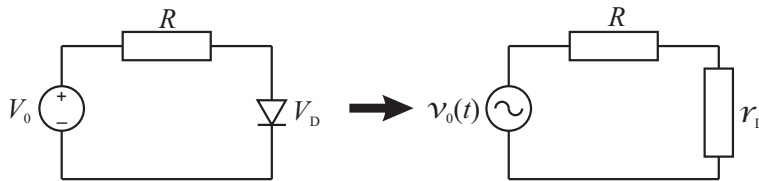



Figure 13: Equivalent small signal replacement for the diode.

215 For example, if $R = 1 \text{ k}\Omega$ and $V_0 = 1.6 \text{ V}$, then $V_R = V_0 - 0.6 \text{ V} = 1 \text{ V}$ and
 216 $I = 1 \text{ mA}$, implying that $r_D = 25 \Omega$.

217 We can use the same approach also for more complex circuits. This
 218 allows us to use all the tricks for linear circuits, but for small signals only.

Transistors

220 A bipolar junction transistor (BJT) consists of three regions with different
 221 doping (*pn*p or *np*n). The central doping region is called the base and
 222 the outer two regions are emitter and the collector. The two junctions form
 223 two back-to-back diodes, but with two important geometrical details
 224 (You cannot build a transistor from two discrete diodes). First, the central
 225 region (the base) is very thin so that minority charge carriers in this re-
 226 gion (electrons in an *npn* transistor) can diffuse through to the collector.
 227 The second feature of a standard BJT is that its geometry is asymmetric,
 228 so that the collector completely surrounds the base to efficiently collect
 229 all charge carriers. In normal operation (active region) the emitter-base
 230 diode is forward biased (all discussions from the previous section apply),
 231 and the base-collector diode is reverse biased.

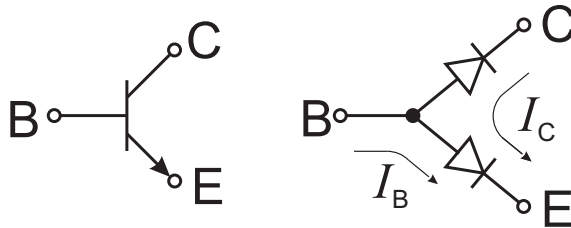

In this course we will focus on the BJT as one of the two most widely used types of transistors. The other important family of transistors are field effect transistors (FETs).

Here and in the following we will discuss the *npn* transistor. For *pn*p reverse all arrows (currents or diodes).

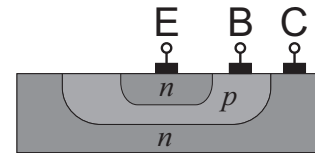


Figure 14: Cross-section of an *npn* BJT.

Figure 15: BJT circuit diagram symbol (left) and junction diodes (right). Note that as described in the text the actual junction geometry is different than the right schematics suggests.

232 In a very simple picture the transistor can be seen as a valve. You
 233 can use the valve as a switch (flow is on or off), and in between you can
 234 regulate the flow by the amount you open the valve. What makes the
 235 transistor work like a valve is the fact that the base current I_b flowing
 236 through the forward-biased base-emitter junction controls the current I_c
 237 from the collector to the emitter.

238 This can be seen in the characteristic curves for the collector current
 239 of a BJT (figure 16). When the valve is closed $I_c = 0$, and when it's open a
 240 large current can flow. If we take the analogy with a valve to the extreme
 241 then there is no pressure drop over a fully open valve, which is equivalent
 242 to $V_{ce} \approx 0$. In this case both junctions become forward biased and the
 243 transistor behaves almost ohmic (I_c increases with V_{ce}). This is referred
 244 to as “saturated region” (close to the y -axis in the left plot of fig. 16).

245 For us the most interesting region in figure 16 is the region with
 246 $V_{ce} > 0.6V$, which is also referred to as “active region”. There the collector
 247 current is (to good approximation) proportional to the base current

$$I_c = \beta I_b,$$

248 with β typically a very few 100. This proportionality is what makes the

We will modify this argument slightly when we will discuss a slightly more quantitative model of the BJT.

Depending on the model used to describe the transistor behaviour you will sometimes see the proportionality factor written as h_{FE} . For our purposes these two parameters are identical.

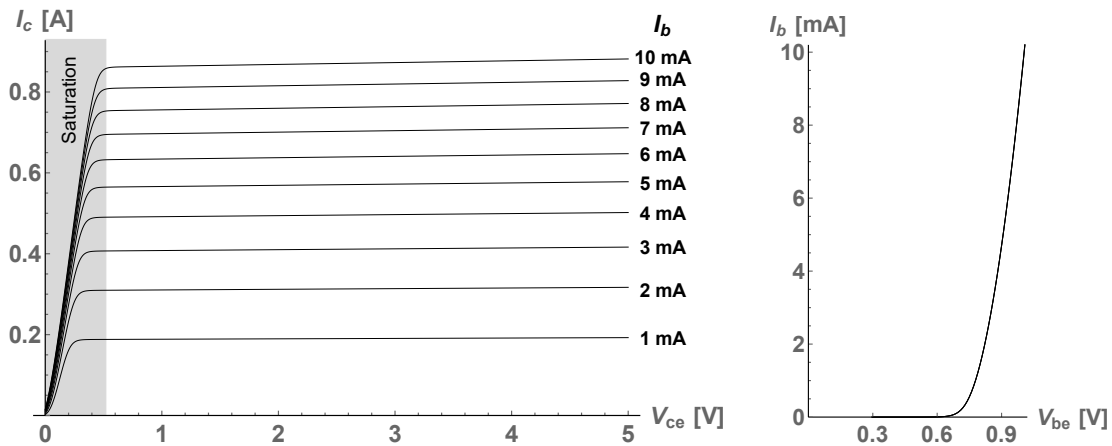


Figure 16: Characteristics of a BC337 BJT. Collector current versus V_{ce} (left) and base current versus V_{be} (right). The data has been obtained using MULTISIM, which uses the SPICE electronics simulation software.

249 transistor such a useful device. It is important, though, to appreciate that
 250 the exact value for β in real devices varies strongly (by several 100%) and
 251 the art of using transistors in electronics is to use them in circuits where
 252 the transistor provides amplification, but the exact gain is defined by
 253 other, more reproducible components (typically resistors). This typically
 254 entails a trade-off between gain and other desirable properties (linearity,
 255 stability, etc.).

256 One should be cautious about the analogy to the mechanical valve,
 257 though. Figure 16 also works the other way round. In a circuit where the
 258 collector current is set by external means the base current will adjust
 259 accordingly. Adjustment of the valve position in response to the flow is
 260 usually not a feature of mechanical flow valves.

261 To allow us to study transistor circuits in some more detail we will
 262 rely on a commonly used model of transistor behaviour, the Ebers-Moll
 263 model. In this model it is actually the base-emitter voltage V_{be} which
 264 controls the collector current,

$$I_c = I_0 \left(e^{\frac{eV_{be}}{k_B T}} - 1 \right). \quad (7)$$

265 This equation is rather similar to the Shockley equation for the diode
 266 characteristics discussed before (eq. (4)). Again, the behaviour is highly
 267 non-linear. Significant currents will flow at $V_{be} \approx 0.6$ V, and significant
 268 changes of I_c will correlate with tiny changes of V_{be} .

269 So, to effectively control the collector current, the base will have to be
 270 DC biased to 0.6 V. Small variations around that bias level will then result
 271 in sizable changes in the collector current. Again, we can focus on the
 272 analysis of these small fluctuations using a small signal analysis. For this
 273 we

- 274 1. assume $V_{be} = 0.6$ V,
- 275 2. assume $V_{ce} > 1$ V (transistor in active region),
- 276 3. assume $\beta \approx 100$ (although, as discussed above, the circuit should not
 277 rely on a specific value for β),

The actual Ebers-Moll model is more detailed but we are using a simplified version, which is sufficient in the active region and at low frequencies.

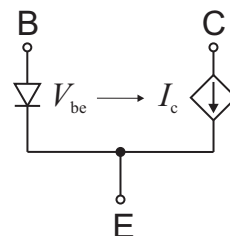


Figure 17: Simplified Ebers-Moll transistor model.

- 278 4. solve the circuit for a linear version for small signals using KVL, KCL
279 and Ohm's law, and re-think if an inconsistency is found.


280 Note that the Ebers-Moll equation describes a transconductance
281 amplifier: a small change in input voltage results in a large change of
282 current through the collector. Or, if we look again at small signals,

$$i_c = g_m v_{be}$$

283 with the transconductance g_m in units of Ω^{-1} or S (Siemens). In the
284 Ebers-Moll model the transconductance is

$$g_m = \frac{dI_c}{dV_{be}} = \frac{e}{k_B T} I_c, \quad (8)$$

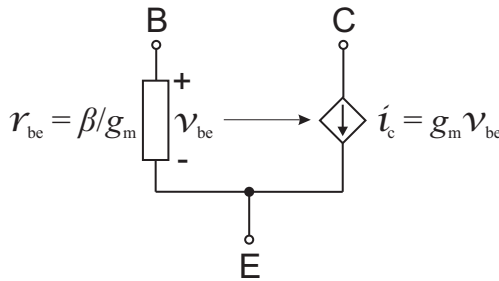285 where the derivative and I_c are evaluated at the working point. At room
286 temperature again a good approximation is $g_m \approx I_c / (25 \text{ mV})$. The small
287 signal equivalent circuit diagram for the transistor is shown in figure 18.



In the past also the Mho was used as a unit, which is Ohm spelled backwards.

The working point is sometimes called the quiescent point, and the current I_c the quiescent current.

Figure 18: Equivalent small signal circuit diagram for a transistor.

288 The small signal resistance r_{be} can be found from

$$r_{be} = \frac{dv_{be}}{di_b} \approx \frac{dv_{be}}{\frac{1}{\beta} di_c} = \frac{\beta}{g_m}. \quad (9)$$

289 A final addition to our phenomenological description of a transistor
290 in the active region stems from the observation that I_c is not entirely
291 independent of V_{ce} for a given base voltage (you can see this also in
292 fig. 16). This is called the Early effect. It can be parametrized as

$$\frac{dV_{be}}{dV_{ce}} = -\alpha$$

293 for a fixed collector current, with $\alpha \approx 10^{-4}$.

As this coefficient is small we will ignore this for most applications.

294 *A first transistor amplifier circuit*

295 A first transistor amplifier circuit is shown in figure 19.

296 As we will discuss later this circuit has some serious shortcomings and
297 it should never be implemented like this, but it is instructive to look at
298 how the assumptions above can be achieved, and the small signal gain
299 found.

300 For simplicity we assume $V_{CC} = 10.6 \text{ V}$ and we will aim for a quiescent
301 collector current of 2 mA. The first thing we need to do is to bias the cir-
302 cuit correctly. For this we assume $\beta = 100$, so that $I_b = I_c / 100 = 20 \mu\text{A}$.

It is a widely used practice to identify the power supply line which is close to the collector with V_{CC} . (Similarly a supply close to the emitter, but different than ground, is labeled as V_{EE} .)

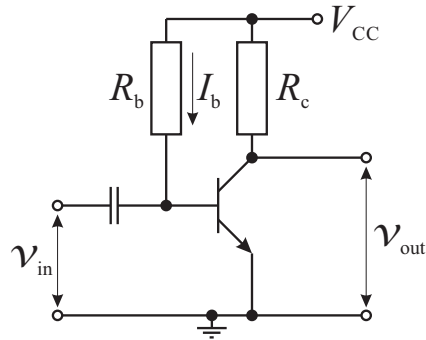


Figure 19: A first transistor amplifier circuit.

303 The DC current going into the base is the same current as is going
304 through R_b , so that we need

$$R_b = \frac{V_{CC} - 0.6 \text{ V}}{20 \mu\text{A}} = 500 \text{ k}\Omega.$$

305 To maximize the possible output swing we choose a quiescent collec-
307 tor voltage in the middle of the available range, for example $V_c = 5 \text{ V}$. This
308 also puts us well into the active region of the transistor ($V_{ce} > 1 \text{ V}$). This is
309 achieved for

$$R_c = \frac{5 \text{ V}}{2 \text{ mA}} = 2.5 \text{ k}\Omega.$$

310

311 To obtain the small signal gain of the circuit we can assume that the
312 input is AC. All bias is DC and is therefore like ground for the small signal
313 analysis. The equivalent small signal circuit is therefore

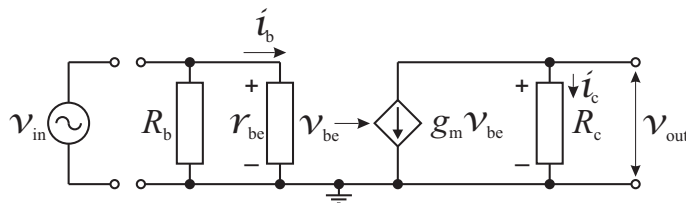


Figure 20: Small signal equivalent of the circuit in fig. 19.

314 From the left side of the equivalent circuit we can see that $v_{be} = v_{in}$.
315 On the output side $v_{out} = i_c R_c$ (for now we will assume that any load
316 connected to the output of this circuit has infinite impedance) and there-
317 fore

$$i_c = -g_m v_{be} = -g_m v_{in}$$

318 and

$$v_{out} = -R_c g_m v_{in}.$$

319 For our example we chose a working point which has $R_c = 2.5 \text{ k}\Omega$ and
320 $g_m = 2 \text{ mA}/25 \text{ mV} = 0.08 \Omega^{-1}$, and therefore the small signal gain for this
321 circuit is

$$G = \frac{v_{out}}{v_{in}} = -R_c \frac{e}{k_B T} I_c = -200.$$

The gain is negative, it is an inverting amplifier.

However, this circuit has some serious short-comings:

1. For the biasing we have relied on $\beta = 100$. We have already said that this factor is highly device-dependent (even for different transistors of the same type). It is quite common for a different transistor of the same type to have $\beta = 400$, or $\beta = 50$. As we have programmed the base current by R_b , this would mean that the quiescent parameters (collector current and voltage) are all over the place.
2. This circuit is highly non-linear. If we have a signal with $\Delta v_{in} = 5 \text{ mV}$, then $\Delta v_{out} = 200 \times 5 \text{ mV} = 1 \text{ V}$, so $\Delta I_c = 0.5 \text{ mA}$ and the transconductance and with it the gain of the circuit will change by 50% over a cycle.
3. The gain will depend on the impedance of the load. If a load with a resistance R_l is connected (this is just a resistance connecting the output to ground) the current through R_c is now shared between the transistor and the load and

$$g_m v_{in} = -i_c - i_l = -\frac{v_{out}}{R_c} - \frac{v_{out}}{R_l},$$


and therefore

$$G = \frac{v_{out}}{v_{in}} = g_m \frac{R_c R_l}{R_c + R_l}.$$

If R_l is large the gain will be reasonable, but if it is small the gain will suffer.

The common-emitter amplifier

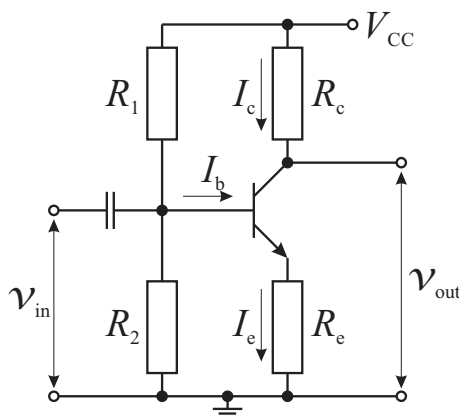The amplifier circuit in figure 21 overcomes most of the issues observed in the previous section. It has its name because the input connects to the base and the output to the collector, and the emitter is shared between the two.



We start again with our assumptions that $I_c \approx \beta I_b$ and $V_{be} \approx 0.6 \text{ V}$. From the first of these we can see that for a collector current around 2 mA the base current is about $20 \mu\text{A}$. Therefore, as long as the resistors in the voltage divider R_1 and R_2 are in the range of $50 \text{ k}\Omega$ or lower, the base current will be an insignificant current leak from the voltage divider. The

In practice this can be tolerated if the amplifier is used in a larger circuit with negative feedback.


Technically the amplifier in the previous section is already a (grounded) common-emitter amplifier but we will use this name here for the more general and also capable circuit.

Figure 21: The common-emitter amplifier circuit.

350 voltage in the divider (the voltage of the base) is therefore stiff against
351 changes of the state of the circuit.

352 For this example we will use $R_1 = R_2 = 50 \text{ k}\Omega$, which for a supply
353 voltage $V_{CC} = 10 \text{ V}$ gives $V_b = 5 \text{ V}$, and consequently $V_e = 4.4 \text{ V}$. We
354 can program the quiescent collector current by using $R_e = 2.2 \text{ k}\Omega$ to
355 achieve the required $I_c \approx I_e = 2 \text{ mA}$. The transconductance is, as before,
356 $g_m = I_c / (25 \text{ mA}) = 0.08 \text{ }\Omega^{-1}$.

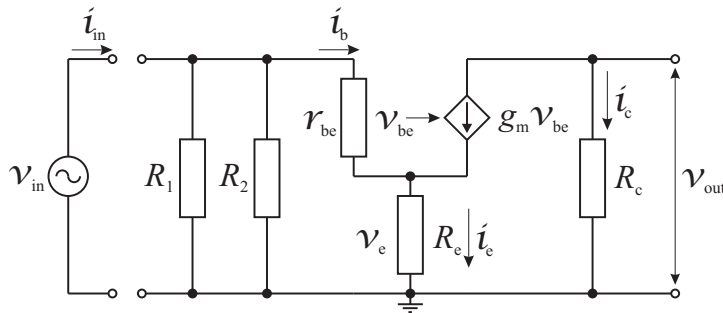357 We can now calculate the small signal gain using again the equivalent
small signal circuit (figure 22).



$$I_e = I_b + I_c = (\beta^{-1} + 1)I_c \approx I_c.$$

Figure 22: Small signal equivalent of the common-emitter amplifier circuit in fig. 21.

358 We write down the KVL for the input and the output loops, and the
359 KCL for the node where they come together.
360

$$v_{in} = v_{be} + v_e = v_{be} + i_e R_e,$$

$$v_{out} = i_c R_c = -g_m v_{be} R_c,$$

$$i_e = g_m v_{be} + \frac{v_{be}}{r_{be}}.$$

361 Inserting the last equation into the first gives

$$v_{in} = v_{be} + g_m v_{be} R_e + \frac{v_{be} R_e}{r_{be}}.$$

362 We can then use the second equation to eliminate v_{be} to get

$$v_{in} = -\left(\frac{1}{g_m R_c} + \frac{R_e}{R_c} + \frac{R_e}{g_m r_{be} R_c}\right) v_{out}.$$

363 The small signal gain can also be written as

$$G = \frac{v_{out}}{v_{in}} = -\frac{R_c}{\frac{1}{g_m} + R_e \left(1 + \frac{1}{g_m r_{be}}\right)}.$$

364 In the Ebers-Moll model $r_{be} = \beta / g_m$, so that

$$G = -\frac{R_c}{\frac{1}{g_m} + R_e \left(1 + \frac{1}{\beta}\right)}.$$

365 Remember that we chose $R_e = 2.2 \text{ k}\Omega$ to get $I_c = 2 \text{ mA}$, which resulted in
366 $g_m \approx 0.08 \text{ }\Omega^{-1}$, and therefore to good approximation

$$G \approx -\frac{R_c}{R_e}, \quad (10)$$

367 and the gain is no longer sensitive to device values like β or the bias
368 values. But this didn't come for free, the gain is now reduced.

Note that in these equations the resistors in the input voltage divider R_1 and R_2 are not present, they are only needed to define the working point.

This is an example how negative feedback can reduce non-linearity: The input to the circuit is the voltage of the base to ground. The input voltage to the transistor as a transconductance amplifier is V_{be} , which is the former voltage reduced by $R_e I_e$, proportional to the output current.

Now that we have a circuit which has satisfactory amplification properties, we can study its input and output impedances.

Let's first look at the input impedance. It is given by

$$R_{\text{in}} = \frac{v_{\text{in}}}{i_{\text{in}}}.$$

We start with

$$i_{\text{in}} = i_1 + i_2 + i_b = v_{\text{in}} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + \frac{v_{\text{be}}}{r_{\text{be}}},$$

and replace v_{be} using $v_{\text{out}} = -g_m v_{\text{be}} R_c$ and the gain $v_{\text{out}}/v_{\text{in}} = -R_c/R_e$,

and r_{be} using $r_{\text{be}} = \beta/g_m$, so that

$$i_{\text{in}} = v_{\text{in}} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{\beta R_e} \right),$$

and

$$R_{\text{in}} = \frac{v_{\text{in}}}{i_{\text{in}}} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{\beta R_e} \right)^{-1}.$$

So, R_{in} is simply the parallel combination of R_1 , R_2 and βR_e . β is about 100, and the last term therefore small. The input impedance is reasonably high and dominated by the resistors in the input voltage divider.

To find the output impedance we look for the Thevenin and Norton equivalent of the circuit in figure 22. We already know the output (open circuit) voltage $v_{\text{out}} = -(R_c/R_e)v_{\text{in}}$. We therefore need to find the short-circuit current of this circuit.

When the output is shorted, then R_c in figure 22 is shorted out, and the short-circuit current is given by the current from the current source in the small-signal transistor replacement

$$I_{\text{sc}} = -g_m v_{\text{be}}.$$

Furthermore we can use KVL and KCL

$$\begin{aligned} v_{\text{in}} + v_{\text{be}} + v_e &= 0 \\ i_b + g_m v_{\text{be}} &= i_e \end{aligned}$$

together with Ohm's law to find

$$I_{\text{sc}} = \frac{g_m v_{\text{in}}}{1 + \frac{R_e}{r_{\text{be}}} + g_m R_e},$$

and

$$R_{\text{out}} = \frac{v_{\text{out}}}{i_{\text{sc}}} = R_c + R_c \left(\frac{1}{\beta} + \frac{1}{g_m R_e} \right) \approx R_c.$$

If our amplifier should have reasonable gain this will be by all means a large resistance. It is a weakness of this circuit that it has a high output impedance and will not be able to drive low-impedance loads. Luckily there are other transistor circuits which can be used to achieve very low output impedances.

Reminder: To effectively couple a voltage from one device to another we need to keep the output impedance of the source low and the input impedance of the receiver high.


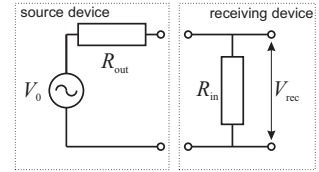


Figure 23: Input and output impedance of coupled devices.

This, and the preference to keep the load on the supply through the input voltage divider small, motivates us to make R_1 and R_2 large (but still small enough that the voltage divider is not disturbed by the current flowing into the transistor base).

394 *The common-collector amplifier or emitter follower*

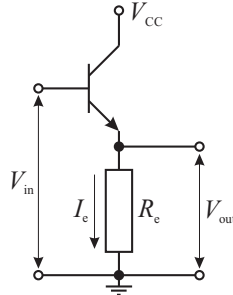395 Figure 24 shows a different transistor circuit, commonly known as emit-
396 ter follower, but it is also sometimes referred to as a common-collector
397 amplifier.



398 As long as $0.6\text{ V} \leq V_{\text{in}} \leq 9.4\text{ V}$ the transistor will be in the active region
399 with

$$I_e = \frac{V_{\text{in}} - 0.6\text{ V}}{R_e},$$

400 and $V_{\text{out}} = V_{\text{in}} - 0.6\text{ V}$. The output voltage follows the input voltage, which
401 explains the name.

402 If this circuit does not give us any voltage amplification, what else
403 could it be good for? Let's study this again with the small signal equiva-
404 lent (figure 25).

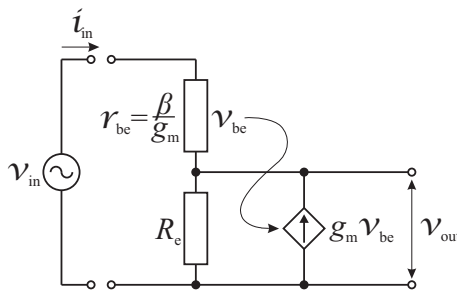


Figure 25: Small signal equivalent of the emitter follower.

405 First, we leave it to the students as an exercise to show that the small
406 signal gain is

$$G = \frac{v_{\text{out}}}{v_{\text{in}}} = \frac{1}{1 + \left(\frac{\beta}{\beta+1}\right) \frac{1}{g_m R_e}} \approx 1.$$

407 The small signal gain is close to 1, but slightly smaller.

408 Next, we can combine this with $v_{\text{in}} = v_e + v_{\text{be}}$ (KVL) and
409 $g_m v_{\text{be}} + i_{\text{in}} = v_{\text{out}}/R_e$ (KCL) to find the input impedance, which is

$$R_{\text{in}} = \frac{\beta}{g_m} + (\beta + 1)R_e.$$

410 $\beta/g_m = r_{\text{be}} \approx 1.5\text{ k}\Omega$ but if R_e is about $2\text{ k}\Omega$, which is a typical value, then
411 $R_{\text{in}} \approx 200\text{ k}\Omega$ for this circuit, which is reasonably high.

412 For the output impedance we calculate again the short-circuit current

$$i_{\text{sc}} = g_m v_{\text{be}} - i_e + i_b,$$

413 but $i_e = 0$ because R_e is shorted out. Similarly $v_{be} = v_{in}$ because of the
414 short, so

$$i_{sc} = v_{in} \left(g_m + \frac{g_m}{\beta} \right) = v_{in} g_m \left(\frac{\beta + 1}{\beta} \right),$$

415 and


$$R_{out} = \frac{v_{out}}{i_{sc}} = \frac{1}{\frac{1}{R_e} + g_m \left(\frac{\beta + 1}{\beta} \right)} \approx \frac{R_e}{1 + g_m R_e} \approx \frac{1}{g_m} = \frac{25 \text{ mV}}{I_c} = r_e.$$

416 The latter is called the ‘emitter resistance’ and is rather low.

417 The emitter follower is not a voltage amplifier but a current amplifier,
418 which is what makes the output impedance small. A common solu-
419 tion is to combine a voltage amplifier like a common emitter amplifier,
420 which provides the voltage gain, with a current amplifier like the emitter
421 follower, to lower the poor output impedance of the first stage in this
422 combination.

423 *The long-tailed pair*

424 As we have just seen the combination of two or more transistors can be
425 very useful. Another widely used combination of two transistors can be
426 used to eliminate distortions (thermal or due to non-linearities) without
427 a large reduction in gain: the long-tailed pair circuit (figure 26). Note
428 that this circuit has two inputs (V_a and V_b), and one output V_{out} . As we
429 will see this circuit actually amplifies the difference of the two input
430 voltages (or signals). Many of the distorting effects will apply to both
431 inputs the same way and will therefore not contribute to the amplified
432 output signal.

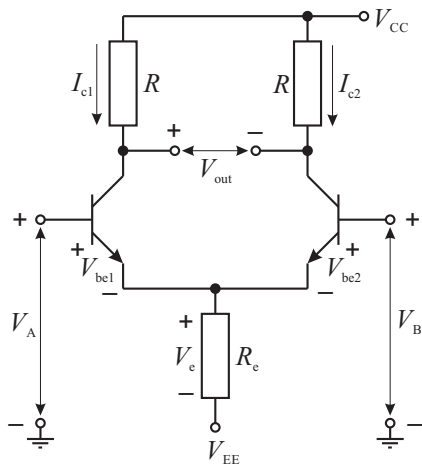

433 This circuit relies on the easy availability of matched transistors and
434 resistors, when they are manufactured on the same wafer. This applies in
435 particular for integrated circuits, where the whole circuit is implemented
436 on one small piece of silicon.

437 To understand the response of this circuit we will not use the small-
438 signal equivalent, but the Ebers-Moll equation, to have fewer approxima-
439 tions, however, the calculations become non-linear.

Generally, the resistance looking into the emitter of a transistor is small, whereas the resistance looking into the collector is high.

We call such an amplifier a differential amplifier. As we have seen the operational amplifier is an example for such an amplifier. In fact, usually the input stage of an op-amp is made up of a long-tailed pair.

Figure 26: The long tailed pair amplifier circuit.

Often only the output from one collector is taken (the two small signal collector voltages are symmetric and opposite). This is called a ‘single-ended’ output. The output is then referenced to ground and can be used as input to standard circuits like a common-emitter amplifier or an emitter follower. The collector resistor at the unconnected collector is then not required (but the transistor is, it needs to steer the currents).

‘Matched’ here means components with the same characteristics and key performance parameters.

Reminder: The Ebers-Moll equation is

$$I_c = I_s \left(e^{\frac{eV_{be}}{k_B T}} - 1 \right).$$

KCL and KVL, $P = VI$ and Ohm’s law (only for resistors) still work. Superposition does not work.

440 We start with KVL in the top loop of the circuit

$$V_{\text{out}} = (I_{c2} - I_{c1})R = I_s R \left(e^{\frac{eV_{\text{be2}}}{k_B T}} - e^{\frac{eV_{\text{be1}}}{k_B T}} \right),$$

441 where we did insert the Ebers-Moll equation for the second part. We can
442 then use KVL again to get

$$V_{\text{be1}} = V_A - V_e$$

$$V_{\text{be2}} = V_B - V_e$$

443 and

$$V_{\text{out}} = I_s R \left(e^{\frac{eV_B}{k_B T}} - e^{\frac{eV_A}{k_B T}} \right) e^{-\frac{eV_e}{k_B T}}.$$

444 Now we can imagine that the input voltages V_a and V_b consist of a part
445 which changes together and a part which changes differentially

$$V_a = V_{\text{com}} + \frac{\Delta V_{\text{in}}}{2}$$

$$V_b = V_{\text{com}} - \frac{\Delta V_{\text{in}}}{2}$$

V_{com} is referred to as the common mode voltage, whereas the differential input is called the normal mode.

446 without loss of generality. The output then becomes

$$V_{\text{out}} = -2I_s R e^{\frac{e}{k_B T}(V_{\text{com}} - V_e)} \sinh \frac{e \Delta V_{\text{in}}}{2k_B T}.$$

447 To understand the exponential in this expression we can use $V_{\text{com}} =$
448 $(V_A + V_B)/2 = (V_{\text{be1}} + V_{\text{be2}})/2 + V_e + V_{\text{EE}}$ (sum of the KVL for the two bottom
449 loops). The supply voltage V_{EE} is constant, and the diode drops V_{be1} and
450 V_{be2} too, to good approximation, so that $\delta V_{\text{cm}} \simeq \delta V_e$ and therefore the
451 exponential $e^{\frac{e}{k_B T}(V_{\text{com}} - V_e)}$ is a constant to first order, regardless of the
452 changes in common mode voltage on terminals A and B.

453 The output is therefore

$$V_{\text{out}} \propto -\sinh \frac{e \Delta V_{\text{in}}}{2k_B T},$$

454 which is very linear for small signals.

$\sinh x \approx x + \frac{x^3}{3!} + \dots$, no x^2 term.

455 *The current mirror*

456 By now you should be convinced that transistors are very powerful de-
457 vices, so it will not come as a surprise that one can also use transistors
458 to create excellent current sources. We will start this discussion with the
459 circuit in figure 27.

460 We leave it to the students to figure out what this circuit does. Is the
461 transistor in this circuit in the active region? What is I_c ?

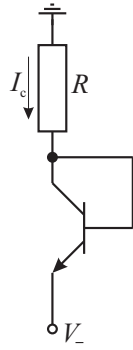


Figure 27: An interesting bias.

462 We can now use the base voltage defined in this circuit to bias one or
 463 more matched transistors.

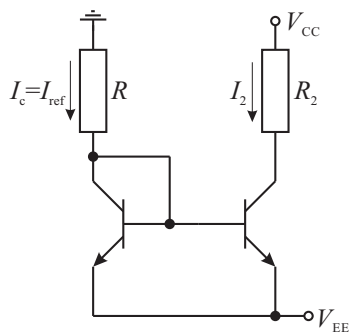


Figure 28: The current mirror.

464 What is I_2 in this circuit? As the base voltage corresponding to the
 465 current I_{ref} , which is programmed by the left transistor, is also the base
 466 voltage for the right transistor the current I_2 through this transistor will
 467 be the same as I_{ref} , independent of the value of R_2 . It should be clear why
 468 this circuit is called a 'current mirror'.

469 One of the exercises in the problem sheet will address these questions
 470 and guide you through a calculation of how the current mirror works.

Appendix A

Semiconductor principles

As you will see in the quantum mechanics course this year the electrons in an atom are in states of well-defined energy. As you will also see there is a general principle in quantum mechanics which prevents that a given state is occupied by more than one electron. As a consequence, when many atoms with their electrons come in close contact within a solid, their electron energy levels will spread slightly resulting in very closely spaced energy levels, which each can be occupied by a single electron. Because of the large number of electrons in the solid the spacing is so close that it cannot be resolved, and the energy levels are observed as a band.

The band structure of a solid defines its electrical conductivity. In an insulator there is an energy band called the 'valence' band which is full of electrons and a higher energy band called the 'conduction' band, which has no electrons. The electrons in the valence band are not free to move because of the Pauli exclusion principle: there are no free states available for the electron to move to. Therefore an insulator cannot conduct electrical current, hence its name. In a metal the conduction band is partially filled with electrons and therefore these electrons are free to move and metals have good electrical conductivity.

In a semiconductor the band gap between the valence and the conduction band is relatively small, small enough that thermal energies are sufficient to lift a small, but non-zero fraction of the electrons into the conduction band. At low energies all the electrons will be in the valence band and as the temperature increases more and more electrons will be lifted into the conduction band. As you will hear this year in the statistical mechanics course the probability for an electron within the solid to be lifted by an energy ΔE at a temperature T is given by the Boltzmann factor $e^{-\Delta E/(k_B T)}$, where k_B is the Boltzmann constant.

Commonly used semiconductor devices used in electronics are made of silicon or germanium. These are elements from the carbon group of the periodic table and as such have four electrons in the outermost shell.

A pure semiconductor of this type will arrange in a diamond cubic crystal structure with each of the outer shell electrons combining with an electron from a neighbouring atom to form a covalent bond. The four outer shell electrons of such an atom are all used up in four such bonds.

Because all its electrons are well integrated in this bond structure a pure semiconductor is a poor conductor. In terms of energies all elec-

This is known as the Pauli exclusion principle.

Imagine the M25 which is completely full of cars with no gaps. In this case no cars could move.

For example for silicon the band gap is 1.14 eV (1.83×10^{-19} J).

$$k_B = 1.38064852 \times 10^{-23} \text{ J/K}$$

Other semiconductors are used for more specialized functions, e.g. GaAs is used for semiconductor lasers and photodiodes.

510 trons are used to completely fill the valence band. However, the conduc-
 511 tivity can conveniently be altered by adding small amounts of elements
 512 from adjacent groups ('doping'). Doping with elements from the boron
 513 group results in p-type material (prevalence of holes) and doping with
 514 elements from the nitrogen group results in n-type material (prevalence
 515 of electrons). These prevalent charge carriers are weakly attached to their
 516 atoms and can easily make the jump into the valence band.

517 If a semiconductor has two regions of different doping a semiconduc-
 518 tor junction is created. A diode contains one junction, whereas a simple
 519 transistor contains two junctions (*npn* or *pnp*).

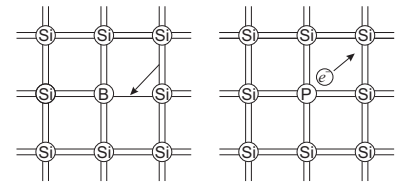


Figure A.1: The effect of placing a dopant into the silicon lattice. p-type doping (left) and n-type doping (right). For the figure the diamond cubic crystal structure has been flattened to 2D. Arrows indicate movement of electrons.

In the case of a hole it is actually the adjacent strongly bound electrons which are trying to fill the hole, but in doing so create a vacancy at their original location. Effectively this allows the hole to travel over large distances.

520 *Appendix B*

521 *Summary of approximate transistor circuit properties*

522 Table B.1 gives a summary of (approximate) key performance parameters for common transistor circuits for
 523 quick reference. For a derivation see the main text. These approximations should help you to quickly estimate
 524 certain performance parameters but for a serious circuit design more detailed models will be needed.

Table B.1: Key performance parameters for common transistor circuits. Approximate expressions for realistic transistors and resistor values are given where applicable.

Designation	circuit diagram	small signal gain	R_{in}	R_{out}	CMRR
Common-emitter amplifier		$-R_c / R_e$	$R_1 R_2$	R_c	
Emitter follower		1	βR_e	r_e	
Long-tailed pair		$-\frac{g_m R}{2}$			$g_m R_e$

525 *Appendix C*

526 *Circuit diagram symbols*

527 This appendix lists for reference the circuit diagram symbols used in this document.












	Resistor
	Capacitor
	Diode
	Transistor (<i>npn</i>)
	DC voltage source
	AC voltage source
	Controlled voltage source
	Current source
	Controlled current source
	Ground (0V)
	Differential amplifier (here: op-amp)

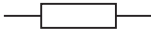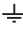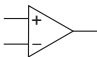Table C.1: Circuit diagram symbols.

528 *Appendix D*

529 *Open issues*

530 *Todd:*

- 531 • Appendix A – I'm not sure if it will be useful or not, how much work is
532 it to fill the table out the rest of the way? My inclination is to leave it in.

533 *Tony*

- 534 • The section on semiconductors is very terse. IMHO it needs to either
535 be expanded (maybe better) reduced to a very short statement saying
536 that in this course we will use a very simple model for a transistor and
537 the underlying physics of semiconductors will be covered in the third
538 year course. The electronics course manual gives a short introduction.

539

540 *Index*

- 541 AC circuit theory, 2
- 542 Amplifier
 - 543 Op-amps
 - 544 inverting amplifier, 3
 - 545 non-inverting amplifier, 3
 - 546 Transistor
 - 547 common-collector amplifier, 17
 - 548 common-emitter amplifier, 14
 - 549 emitter follower, 17
 - 550 long-tailed pair, 18
- 551 Common mode, 19
- 552 Common-collector amplifier, *see* Emitter follower
- 553 Common-emitter amplifier, 14
 - 554 input impedance, 16
 - 555 output impedance, 16
 - 556 setting the operating point, 14
 - 557 small signal gain, 15
- 558 Current mirror, 19
- 559 Current source, 2

- 560 Differential amplifier, 18
- 561 Diode, 7
 - 562 characteristics, 7
 - 563 finding operating point, 8
 - 564 knee voltage, 9
 - 565 small signal equivalent, 9
 - 566 small signal equivalent resistance, 8
- 567 Doping, 22

- 568 Early effect, 12
- 569 Ebers-Moll model, 11
- 570 Emitter follower, 17
 - 571 input impedance, 17
 - 572 output impedance, 17
 - 573 small signal gain, 17
- 574 Emitter resistance, 18

- 575 Impedance
 - 576 of capacitor, 3
 - 577 of inductor, 2
 - 578 of resistor, 2

- 579 Kirchhoff's laws, 1
 - 580 Kirchhoff's current law (KCL), 1
 - 581 Kirchhoff's voltage law (KVL), 1

- 582 Long-tailed pair, 18
 - 583 single-ended output, 18

- 584 Matched transistors, 18

- 585 Negative feedback
 - 586 in the common-emitter amplifier, 15
 - 587 with op-amps, 3
- 588 Network replacement theorems, 2
- 589 Norton equivalent, *see* Network replacement theorems

- 590

- 591 Op-amps
 - 592 ideal, 3

- 593 Passive sign convention, 1

- 594 Semiconductor junction, 22
- 595 Semiconductors, 7
- 596 Shockley diode equation, 7

- 597 Thevenin equivalent, *see* Network replacement theorems
- 598
- 599 Transconductance, 12
- 600 Transistor
 - 601 β , 10
 - 602 h_{FE} , 10
 - 603 active region, 10
 - 604 base, 10

605 collector, 10
606 emitter, 10
607 saturated region, 10
608 transconductance, 12

609 Virtual short, 3
610 Voltage source, 2