

Simple transmission line




naive view is that this is a wire with zero resistance so the signal travels perfectly with no distortion!

But how fast?

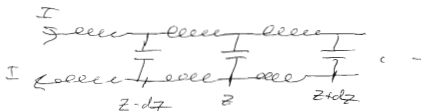3.11 ... Theory is all instantaneous and even with zero resistivity, as you learned last year & this.



Two pieces of metal in space have an inductance and a capacitance between them. Even if $R=0$.

So actually our simple line has an inductance per unit length and a capacitance per unit length.



①

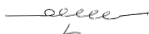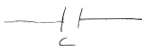- ① Passive sign convention! Labeling scheme
important to get transmission lines
undistorted




Simply stated, you define
voltage across two points
however you want.

then current is defined to
enter the + terminal

Reason

$$I_C = C \frac{dv_C}{dt}$$

with no
convention

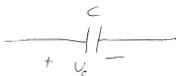

current must
be labeled
 $\rightarrow I_C$ flows from left
to right


works backwards too
voltage must be fixed.

given current

Reason

$$L \frac{dI_L}{dt} = V_L$$

using passive sign convention

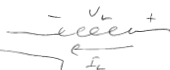


$\rightarrow$ voltage must
be
labeled this way.

(2)

Take with you to Board!

Look carefully at a section of the

Line

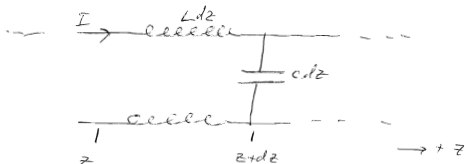

↑
start at location ' z '


and go in the positive ' z ' direction
to $z+dz$.

So the total inductance of our little
segment is Ldz

and the capacitance is Cdz


Now define the voltage between the
lines as ' V ' at location z .

Important!

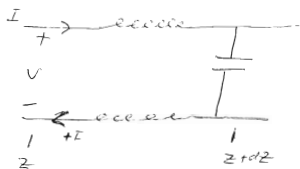

When we head
in the
 $+z$ direction
we need to
define V
as a positive
voltage increase

To match with our positive increase
in z

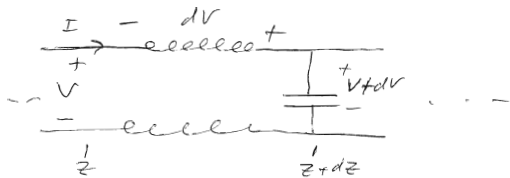


so across the capacitor
we set $V+dv$

But Now notice !!

The labeling we are forced to
obey because of our choice of $+z$
does not obey passive

sign convention for the inductor

we have

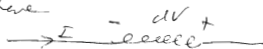

which is opposite.


so instead of $L dz \frac{dI}{dz} = dv$

we must use $\Rightarrow$

$$L dz \frac{dI}{dz} = -dv$$

so $-\frac{dV}{dz} = L \frac{dI}{dz}$ $L = \text{inductance/unit length}$

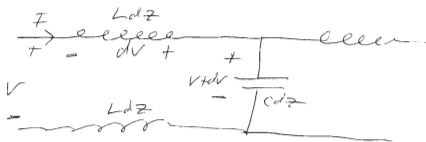Next problem we have identified
the current through the upper inductor
but not through the lower one




Pretty obvious from symmetry
that we had to have
 $-I$ in the lower branch,
and then the voltage drop is
the same,

but this gives us the channel to

simplify our model by treating
the lower branch as having zero
inductance and the upper one as having
all the inductance


we will call it $1/2 L$ anyway

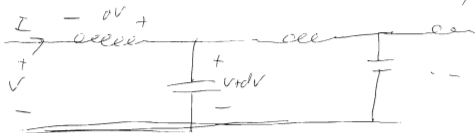


like a line over an infinite grid plane.

another proof $\rightarrow$

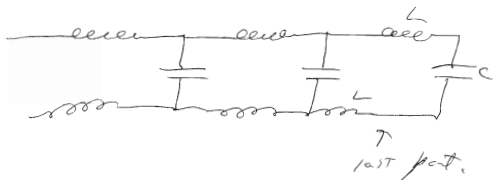ASK If want To see Resonance, if not skip this.



Combine impedances

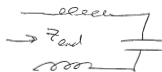


$$Z_{end} = j\omega 2L + \frac{1}{j\omega C} \Rightarrow \frac{j\omega 2L}{1} \parallel \frac{1}{j\omega C}$$



note that Z_{end} is in parallel with C


So this could always be modeled as

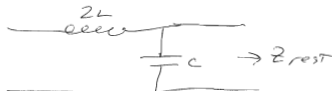

and since this is all general any way I'm going to keep $2L$ rather than carry around $2L$ everywhere

Another Point

I've used the following model

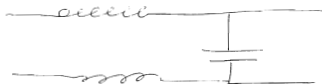

but this model has 2 times the number of inductors as capacitors.


So really, 2-for-1 and this isn't really right

and I used ' L ' the inductance per unit length on both inductors


But the per-unit inductance includes both when you actually calculate it.

So maybe I should have used ' $L/2$ ' instead of ' L '

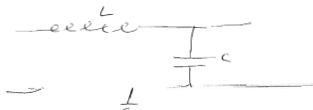or "fix" the model by doing what I am doing now.




(3)

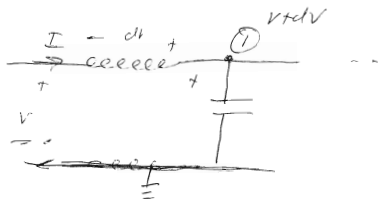

At node ① There is a current which is through the capacitor that joins I at location $z + dz$

Once again, our choice of positive z means that we must add the incremental current to I at $z + dz$

could to I to keep positive

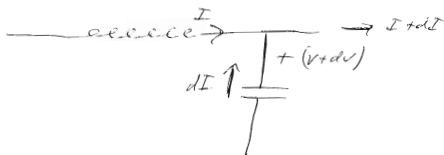

But notice that, across the capacitor, we once again have violated passive sign convention

$$\text{So} \quad -dI = \frac{dI}{dt} (V + dV)$$

Thus if $dV \approx \Delta V$
 $\frac{d}{dt}$ as $\frac{\Delta}{\Delta t}$

So $\frac{d}{dt} (V + dV) \approx \frac{\Delta V}{\Delta t} + \frac{\Delta V^2}{\Delta t}$

but ΔV^2 is too small to
 worry about so:

$$- \frac{dI}{dz} = C \frac{dV}{dt} \quad (A)$$

recall that

(B) $\left(\begin{aligned} - \frac{dV}{dz} &= L \frac{dI}{dt} \quad (B) \\ - \frac{d^2 V}{dz^2} &= L \frac{d}{dz} \left(\frac{dI}{dt} \right) \\ - \frac{d^2 V}{dz^2} &= L \frac{d}{dt} \left(\frac{dI}{dz} \right) \end{aligned} \right.$

now use (A)

$$- \frac{d^2 V}{dz^2} = -LC \frac{d^2 V}{dt^2}$$

so

$$\frac{d^2 V}{dz^2} = LC \frac{d^2 V}{dt^2}$$

wave equation with $v^2 = \frac{1}{LC}$

coaxial cable $C = \frac{2\pi\epsilon}{\ln(4a/b)}$ $L = \frac{\mu_0 \ln(4a/b)}{2\pi}$ so $v^2 = c^2$

④

From 1st year waves + normal modes

General Solution is

$$\textcircled{1} \quad V(z, t) = F(z - vt) + G(z + vt)$$

$$\text{let } u = z - vt \\ w = z + vt$$

$$\text{So } \frac{du}{dt} = -v \quad \frac{du}{dz} = 1 = \frac{dw}{dz} \\ \frac{dw}{dt} = v$$

using $\textcircled{1}$ let's take the time derivative

$$\frac{dV}{dt} = \frac{du}{dt} \frac{dF}{du} + \frac{dw}{dt} \frac{dG}{dw} \\ = -v \frac{dF}{du} + v \frac{dG}{dw}$$

But previously we concluded

$$\frac{dV}{dt} = -\frac{1}{c} \frac{dV}{dz}$$

$$\text{So } -\frac{1}{c} \frac{dV}{dz} = -v \frac{dF}{du} + v \frac{dG}{dw} \\ \frac{1}{cv} \frac{dV}{dz} = \frac{dF}{du} - \frac{dG}{dw} \quad v = \frac{1}{\sqrt{\epsilon\mu}}$$

$$\frac{\sqrt{\epsilon\mu}}{c} \frac{dV}{dz} = \frac{dz}{dz} \frac{dF}{du} - \frac{dz}{dz} \frac{dG}{dw}$$

$\uparrow \quad \quad \uparrow$
 multiply by one

(5)

$$\sqrt{\frac{L}{C}} \frac{dI}{dz} = \frac{dz}{dz} \frac{dF}{dz} - \frac{dz}{dz} \frac{dG}{dz}$$

$$\text{but } \frac{dz}{dz} = 1 = \frac{dz}{dz}$$


$$\sqrt{\frac{L}{C}} \frac{dI}{dz} = \frac{dF}{dz} - \frac{dG}{dz}$$

So we see that

$$Z_0 I = F(z-ct) - G(z+ct)$$

$$\text{with } Z_0 = \sqrt{\frac{L}{C}}$$

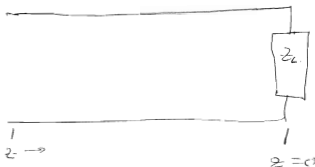~~So now a problem~~ Now is more practical problem



Transmission
line with
a given load

what happens when such a voltage or current wave encounters a terminating impedance?

need a solution we can work with

complex exponential !!

$$V(z, t) = A e^{(j\omega t - jkz)} + A' e^{(j\omega t + jkz)} \quad (6)$$

of course $v = \frac{\omega}{k} = \sqrt{\frac{1}{LC}}$

which is fine as long as we have $\frac{\omega}{k} = v \quad v^2 = \frac{1}{LC}$

This then does have the form of our General Solution $[F(z-vt) + G(z+vt)]$ and from previously we must have

$$Z_0 I(z, t) = A e^{(j\omega t - jkz)} - A' e^{(j\omega t + jkz)}$$

At $z=0$ we have impedance Z_L and the way we defined our + current and voltage sense means passive sign convention holds

$$\text{so } V = Z_L I \quad (\text{it must!})$$

$$\text{so } \frac{V(t)}{Z_0 I(t)} = \frac{Z_L}{Z_0} = \frac{A e^{j\omega t} + A' e^{j\omega t}}{A e^{j\omega t} - A' e^{j\omega t}}$$

and all the dependence drops out!

$$\frac{V}{Z_0 I} = \frac{Z_L}{Z_0} = \frac{A + A'}{A - A'}$$

we choose A so solve for ratio of

$$\frac{A'}{A} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$A \rightarrow$ incoming wave amplitude

$A' \rightarrow$ returning or "reflected" wave

~~16~~

If $Z_L = Z_0$

$$\frac{A'}{A} = 0$$

No returning wave!

$$Z_0 = \sqrt{\frac{L}{C}} \text{ is real}$$

and Z_L can be complex

but to get no return wave

$Z_L \Rightarrow \text{pure Resistance}$

If $Z_L = \infty$

$$\frac{A'}{A} = 1$$

reflected
voltage is in
same direction
reflection complete

$$Z_L = 0$$

$$\frac{A'}{A} = -1$$

again reflection
is complete
but reflected
wave is
of opposite sense.

Z_0 is like having a pure load
resistance at every point down the
line, when you get to the end, if
there is no match, the has to be
communicated to the source.

(7)

Power?

$$P = VI$$

$$= \frac{(Ae^{j\omega t - jkz} + A'e^{j\omega t + jkz})(Ae^{j\omega t - jkz} - A'e^{j\omega t + jkz})}{Z_0}$$

$$= \frac{1}{Z_0} [A^2 e^{j2\omega t - j2kz} - AA' e^{j2\omega t} + AA' e^{j2\omega t} - A'^2 e^{j2\omega t + j2kz}]$$

$$= \frac{1}{Z_0} [A^2 \exp(j2\omega t - j2kz) - A'^2 \exp(j2\omega t + j2kz)]$$

we see power also has components

traveling forward & backward

So when $A' = 0$ there is

no power reflecting down the line.

Careful! I used complex voltage

So really, to be rigorous,


would have needed to take the Real part of V & the Real part of I

but this illustrates the point completely,

Though the Average Power trick still works

$$P_{ave} = \frac{1}{2} (V_{rms})^2$$

What is impedance of a stub?

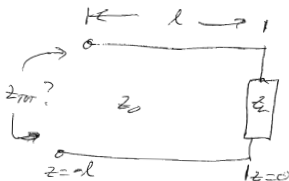

$$V = A e^{j(\omega t + \beta z)} + A' e^{j(\omega t - \beta z)}$$

$$Z_0 I = A e^{j(\omega t + \beta z)} - A' e^{j(\omega t - \beta z)}$$

$$Z_{TOT} = \frac{V}{I} = \frac{Z_0}{2} \frac{A e^{j\beta l} + A' e^{-j\beta l}}{A e^{j\beta l} - A' e^{-j\beta l}}$$

which is a bit of a mess in general,

but what if $\beta l = \frac{2\pi}{\lambda} l$

$$= \frac{\pi}{2}$$

in other words, what if $l = \frac{\lambda}{4}$?

Then $e^{j\beta l} = e^{j\pi/2} = j$
 $e^{-j\beta l} = e^{-j\pi/2} = -j$


$$Z_{TOT} = \frac{Z_0}{j(A-A')} = \frac{Z_0}{j(A+A')} = \frac{(A+A')}{A-A'} = \frac{Z_L}{Z_0}$$

$$= Z_0 \left(\frac{Z_0}{Z_L} \right)$$

$$= Z_0^2 / Z_L$$

(8)

So what?

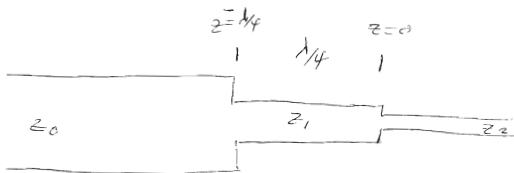

What does the point at $z = -\frac{1}{4}$ look like?

well z_1 looks like it is terminated with an impedance of z_2

so

$$\text{at } z = -\frac{1}{4}$$

$$Z_{\text{in}} = \frac{z_1^2}{z_2}$$


assume z_2 is fixed, & that we can

choose z_1 , if

$$z_0 = \frac{z_1^2}{z_2}$$


matched
impedance
if the
lines are
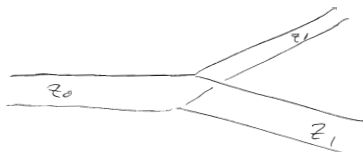
$$\left\{ \begin{array}{l} z_0 z_2 = z_1^2 \\ z_1 = \sqrt{z_0 z_2} \end{array} \right. \Rightarrow \text{no reflections down } z_0 !!$$



Sometimes, easier than you think,
 what would Z_1 have to be so there
 are no reflections back down
 Z_0 ?

Answer $Z_1 = 2Z_0$ acts like

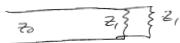

Two terminals Z_1 's in
 parallel


Note $\circ$ I was careful to

always use Z_0, Z_L etc.

remember, impedances can be complex or
 imaginary. Every formula still works!

(9)

General case with real terminated

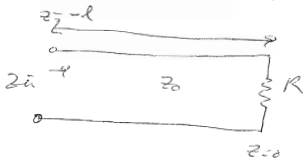

$$Z_{in} = \frac{V}{I} = Z_0 \frac{Ae^{jkl} + A'e^{-jkl}}{Ae^{jkl} - A'e^{-jkl}}$$

But if $Z_L = R$

$$\frac{A'}{A} = \frac{R - Z_0}{R + Z_0}$$

$$Z_{in} = Z_0 \left(\frac{e^{jkl} + \frac{R - Z_0}{R + Z_0} e^{-jkl}}{e^{jkl} + \frac{Z_0 - R}{R + Z_0} e^{-jkl}} \right)$$

$$= Z_0 \left[\frac{(R + Z_0)e^{jkl} + (R - Z_0)e^{-jkl}}{(R + Z_0)e^{jkl} + (Z_0 - R)e^{-jkl}} \right]$$

$$Z_{in} = Z_0 \frac{[2R \cos kl + j2Z_0 \sin kl]}{2R \sin kl + j2Z_0 \cos kl}$$

$$Z_{in} = Z_0 \frac{R \cos kl + jZ_0 \sin kl}{Z_0 \cos kl + jR \sin kl} = Z_0 \frac{R + jZ_0 \tan kl}{Z_0 + jR \tan kl}$$

$$Z_{in} = R \left(\frac{1 + j \frac{Z_0}{R} \tan kl}{1 + j \frac{R}{Z_0} \tan kl} \right)$$

Not c.e. But

has 15 only real

$$\text{when } \tau_{n,kl} = 0, \pi/2, \pi, 3\pi/2$$

$$= n\pi/2 \quad n=0, 1, 2,$$

$$\text{at } Rl = \frac{20l}{\lambda} = 0, \pi, 2\pi, 3\pi$$

$$= m\pi \quad m=0, 1, 2, 3$$

$$\tau_{n,kl} = 0 \quad \text{and } z_n = R$$

$$\text{at } kl = \pi/2, 3\pi/2, 5\pi/2$$

$$= (2m+1)\pi \quad m=0, 1, 2, 3$$

$$\tau_{n,kl} \rightarrow \infty$$

$$\text{and } z_n = R \left(\frac{z_{0,kl}}{R/z_0} \right) = \frac{z_0^2}{R}$$

as found previously

at every other point we get a

complex impedance which is

either ~~reactive~~ capacitive
or inductive

So this is how you can make
almost any kind of passive circuit
element you want in a transmission
line.

When does this apply?
(meaning all this theory)

Easy Rule of Thumb

if the frequency of use
is such that $\lambda \gtrsim \frac{l}{10}$

where l is the length of your
wires/traces on circuit board

you may need to consider impedance
matching in your system.

For a mobile phone;

~ 500

so it $\lambda \approx 0.5 \text{ km}$

≈ 500

assuming the speed of light


$f \approx 606 \text{ Hz}$

Since mobile phone $\sim 36 \text{ Hz}$ at
most you get away without this

Probably helps keep them cheap!

(11)


Final example If Time

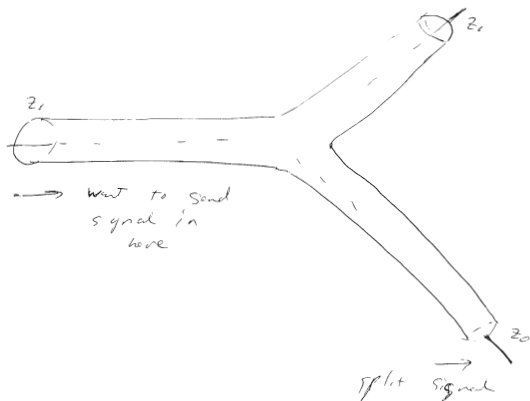

But we do not want any back reflections

Why?

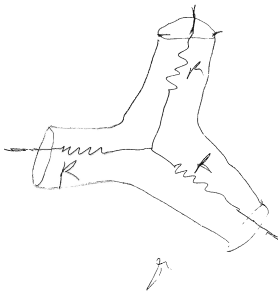because we do not want
 Sky 2 to know we
 have multiple sets connected.



connect

can break it up only
way we want



$$\text{Total} = R + \frac{(R+Z_0)(R+Z_0)}{2R+2Z_0}$$


want total to equal Z_0

$$Z_0 = R + \frac{(R+Z_0)^2}{2(R+Z_0)} \rightarrow \text{continue on board}$$

($R = Z_0/3$ answer)

Let's try for completeness
(off syllabus)

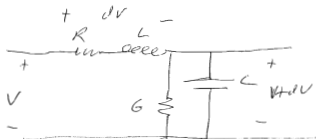Electric wires have resistance
dielectrics have losses



R - resistance/length

G - conductance/length.

Before we had

$$-\frac{dV}{dz} = L \frac{dI}{dt}$$

$$-\frac{dI}{dz} = C \frac{dV}{dt}$$

Now we have

$$-\frac{dV}{dz} = RI + L \frac{dI}{dt}$$

$$-\frac{dI}{dz} = GV + C \frac{dV}{dt}$$

Using same procedure as before
we get after algebra & calculus

$$\frac{d^2 V}{dz^2} = RGV + (RL + LC) \frac{dV}{dt} + LC \frac{d^2 V}{dt^2}$$

This is a damped traveling wave
of form

$$e^{-\alpha z} e^{i(\omega t - kz)}$$